

Circuit Analysis Techniques



Lecture 6

Thevenin Theorem

Lecture delivered by:



Topics

- Thevnin's Theorem
- Computing Thevenin Equivalent
- Networks to Illustrate Thevenin Theorem



Objectives

At the end of this lecture, student will be able to:

- State and implement Thevenin's theorem on any complicate linear bilateral network




Thevenin's Theorem

- **Thevenin's Theorem** states that “Any circuit with sources (dependent or independent) and resistors can be replaced by an equivalent circuit containing a single voltage source and a single resistor”.
- Thevenin's theorem implies that we can replace arbitrarily complicated networks with simple networks for purposes of analysis.





Independent Sources (Thevenin)

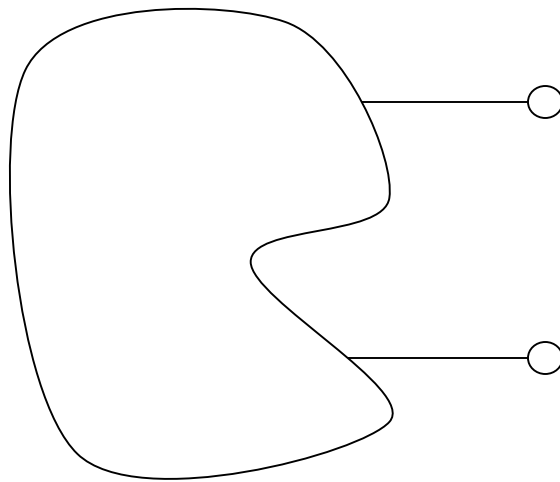- Any network with two open terminals can be replaced by a **single voltage source (V_{TH})** and a **series resistance (R_{TH})** connected to the open terminals.
- A component can be removed to produce the open terminals.



Circuit with
independent sources

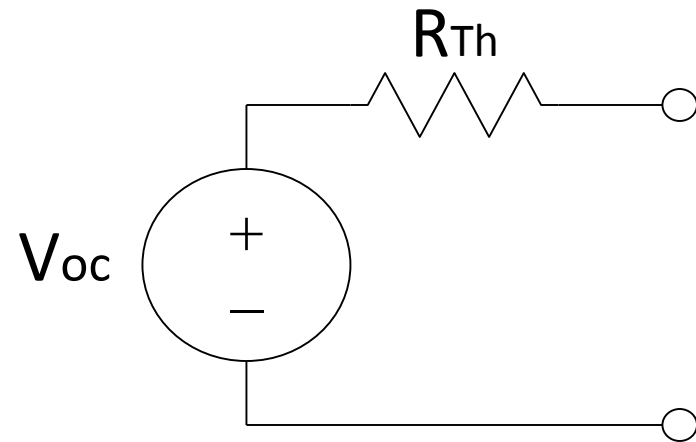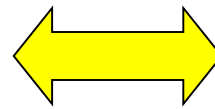

Thevenin equivalent
circuit

Computing Thevenin Equivalent

- Basic steps to determining Thevenin equivalent are

- Find v_{Th}

V_{TH} is determined by calculating the voltage between open terminals **A** and **B**.


- Find R_{Th}

R_{TH} is determined by shorting the voltage source and calculating the circuit's total resistance as seen from open terminals **A** and **B**.




Networks to Illustrate Thevenin Theorem


(a)

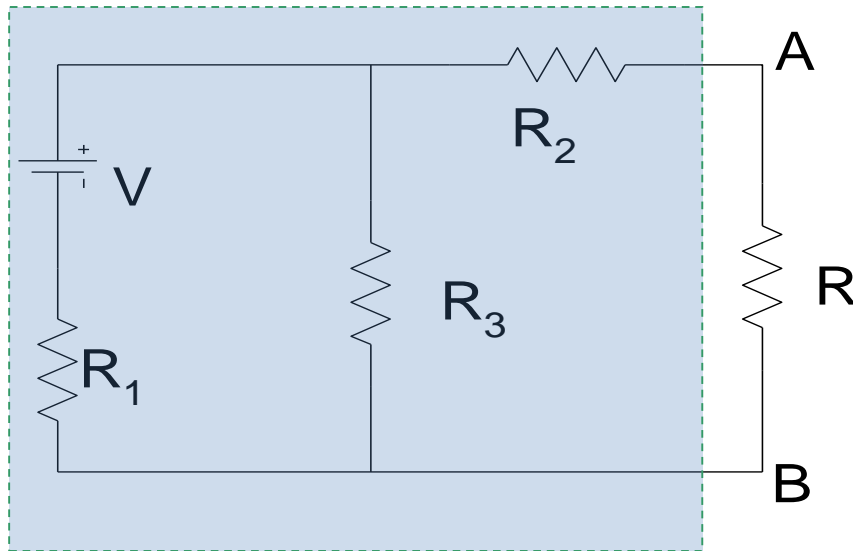


(b)

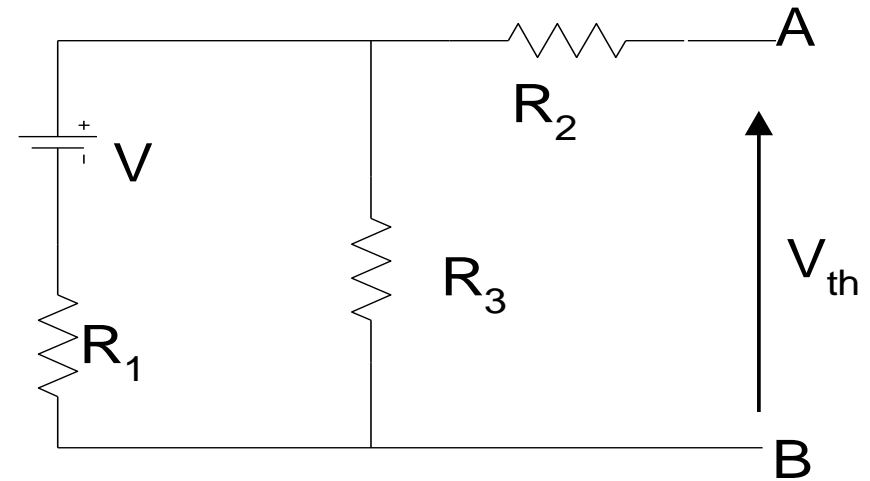

(c)

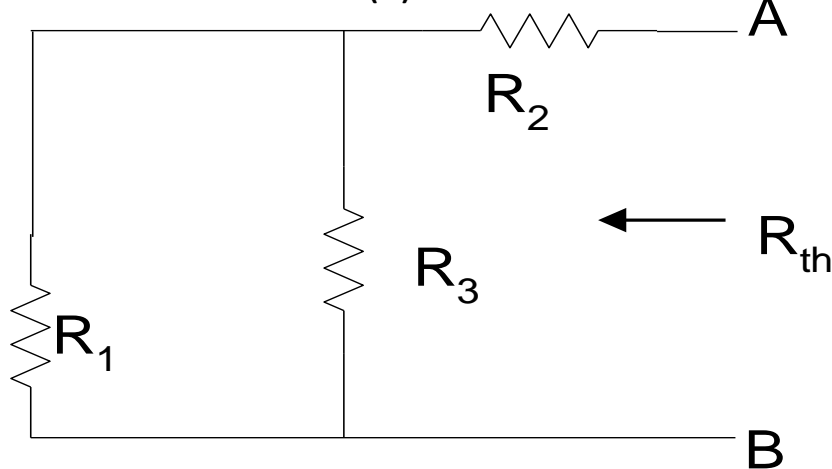

(d)

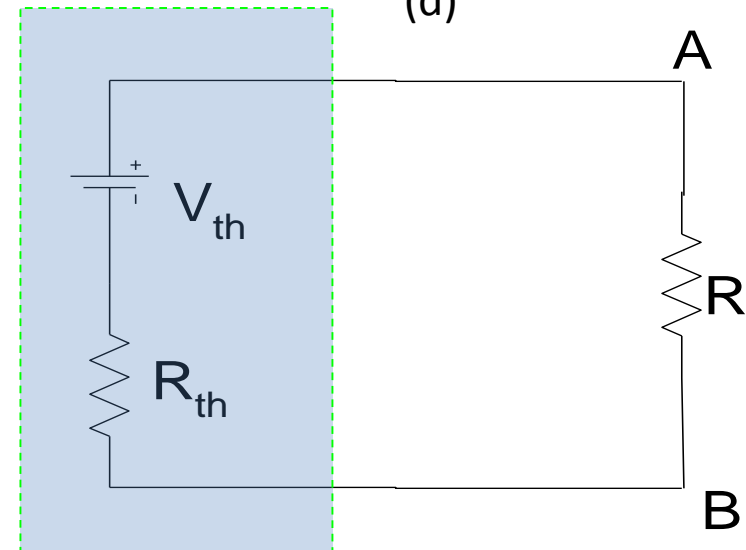

Computing Thevenin Equivalent

Refer to network (b), in R_2 there is not complete circuit, thus no current, thus current in R_3

And p.d across R_3 is

$$I_{R3} = \frac{V}{R_1 + R_3} \quad (1)$$

$$V_{R3} = \frac{VR_3}{R_1 + R_3} \quad (2)$$

Since no current in R_2 , thus

$$V_{th} = \frac{VR_3}{R_1 + R_3} \quad (3)$$

Refer to network (c) the resistance at AB

$$R_{th} = R_2 + \frac{R_1 R_3}{R_1 + R_3} \quad (4)$$

Thus current in R (refer network (d))

$$I = \frac{V_{th}}{R_{th} + R} \quad (5)$$



Thevenin's Theorem

Example 1

Calculate the current through R_3



Solution

With R_3 disconnected as in figure below

$$I_1 = \frac{6 - 4}{R_1 + R_2} = \frac{2}{2 + 3} = 0.4A$$

p.d across CD is $E_1 - I_1 R_1$


$$V = 6 - (0.4 \times 2) = 5.2V$$

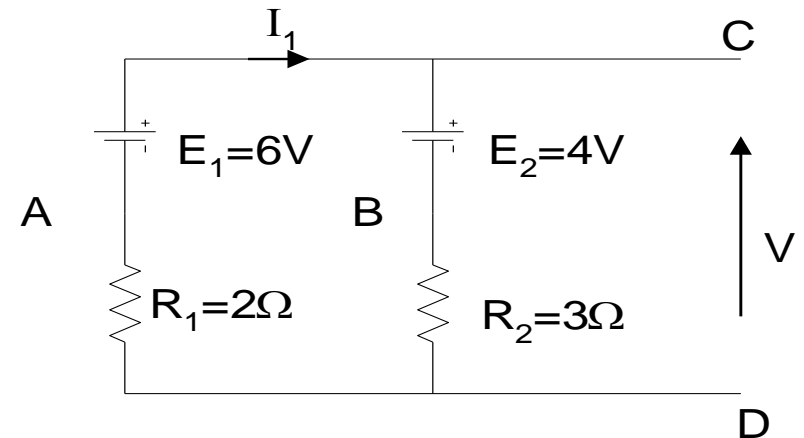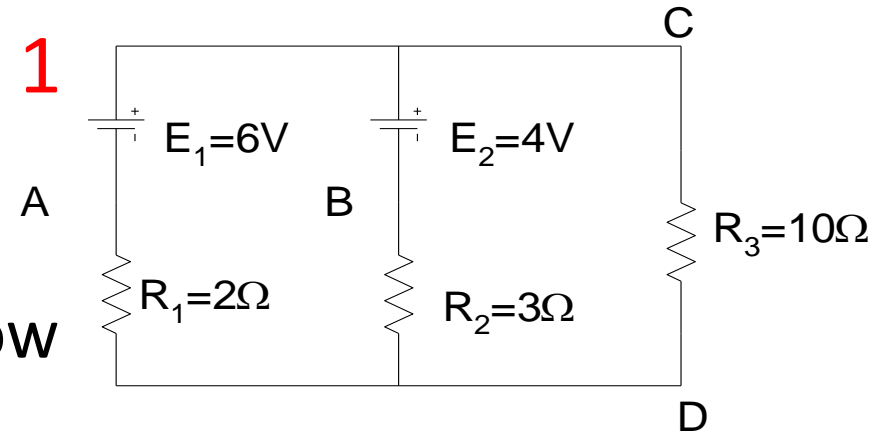

Continued..


To determine the internal resistance we remove the e.m.f s
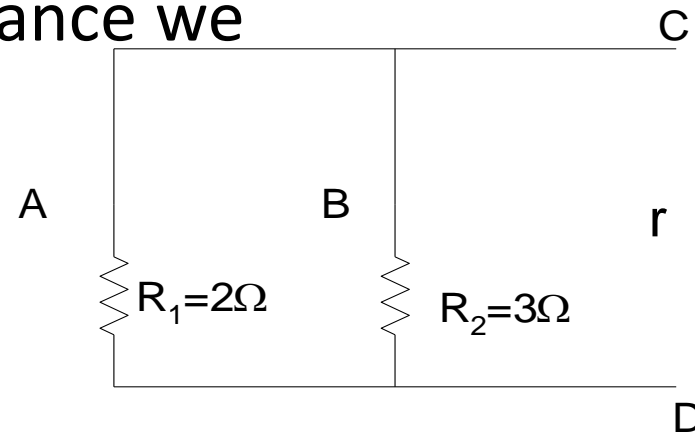
$$r = \frac{2 \times 3}{2 + 3} = 1.2 \Omega$$



Replace the network with $V=5.2V$ and $r=1.2$, then the at terminal CD, R_3 , thus the current

$$I = \frac{5.2}{1.2 + 10} = 0.46A$$

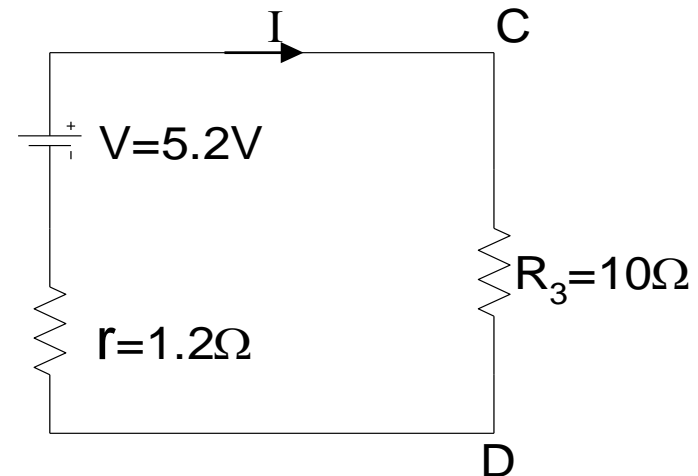


Thevenin's Theorem

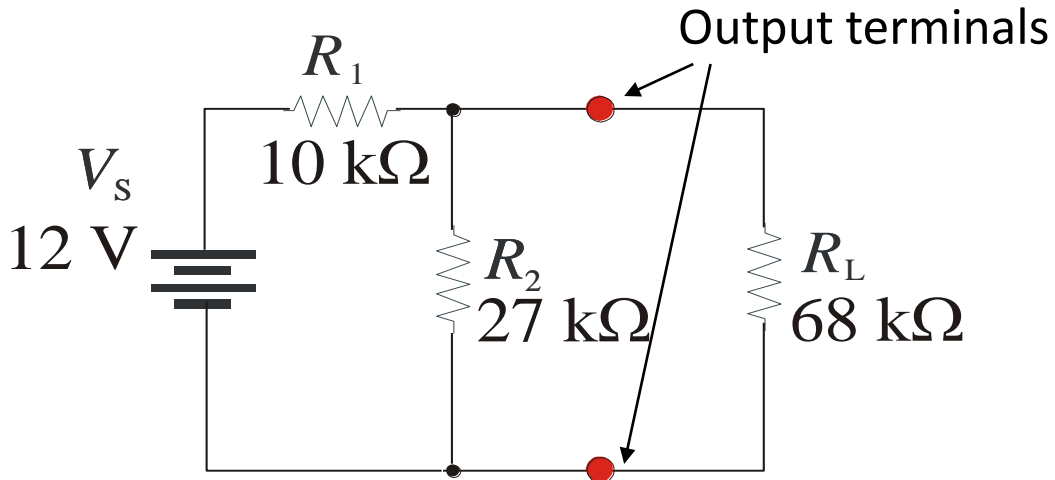Example 2

What is the Thevenin voltage for the circuit? **8.76 V**

What is the Thevenin resistance for the circuit? **7.30 k Ω**



Remember, the load resistor has no effect on the Thevenin parameters.

Summary

- Thevenin's Theorem states that “Any circuit with sources (dependent or independent) and resistors can be replaced by an equivalent circuit containing a single voltage source and a single resistor”.

