

# Circuit Analysis Techniques



# Lecture 15

## Tutorial

Lecture delivered by:



# Objectives

At the end of this lecture, student will be able to:


- Solve problems on Star-delta conversion
- Solve problems on Superposition theorem
- Solve problems on circuit analysis



# Star/ Delta Transformation
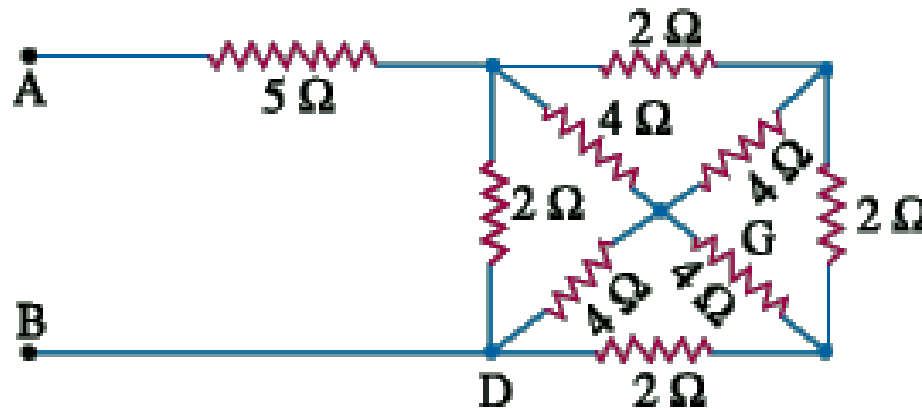
## Problem 10:


Use  $\Delta$ -Y conversion to find the resistance between the terminals 'AB' of the circuit shown in figure.



# Problems
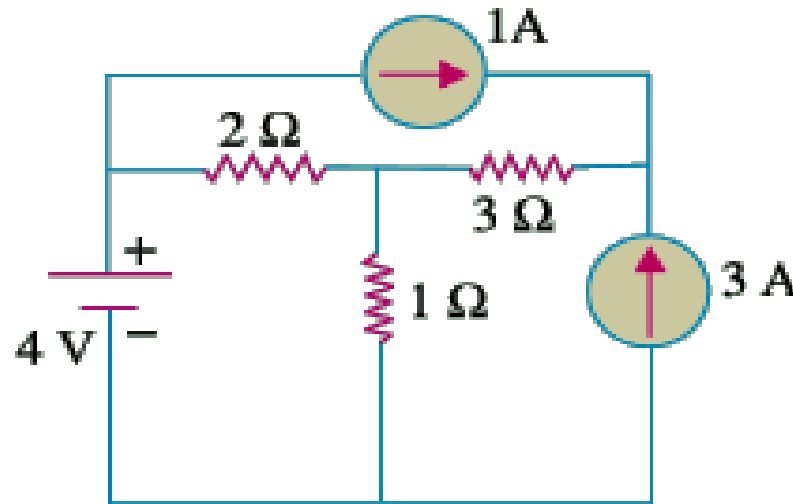
## Problem 11:


In the circuit of Fig. find current through  $1\text{-}\Omega$  resistor using both THEVENIN's theorem and SUPERPOSITION theorem



## Problem 12

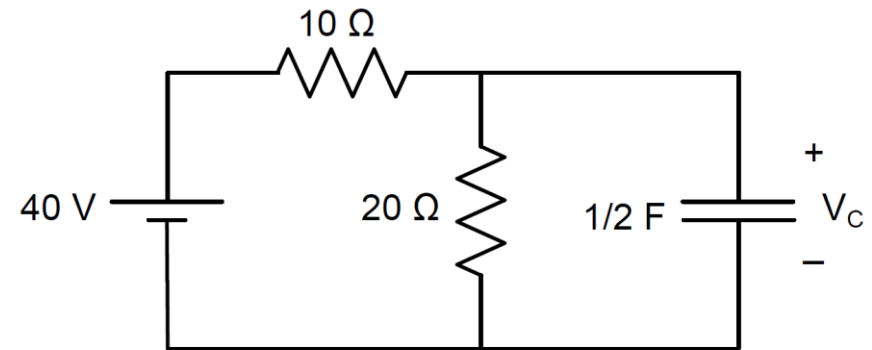
# Problems

In the circuit in Fig,  $V_C = 20$  V at some time  $t_1$ . Then  $\frac{dV_C}{dt}$  at the same time is


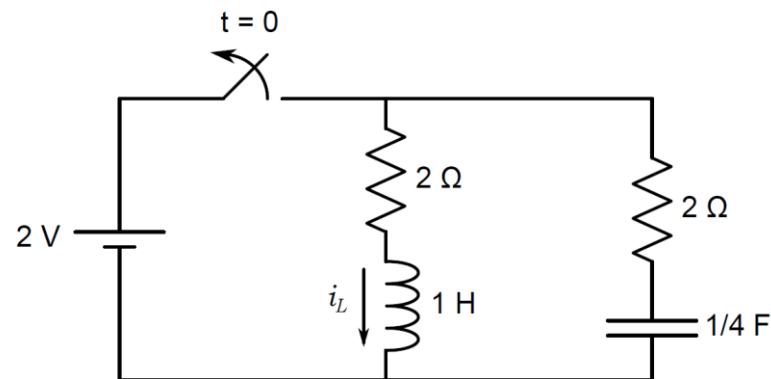
## Problem 13


In Fig.5 the switch was initially in closed position for a long time and is opened at time  $t = 0$ . Then the expression for current through the inductor  $i_L$  is given by



# Problems
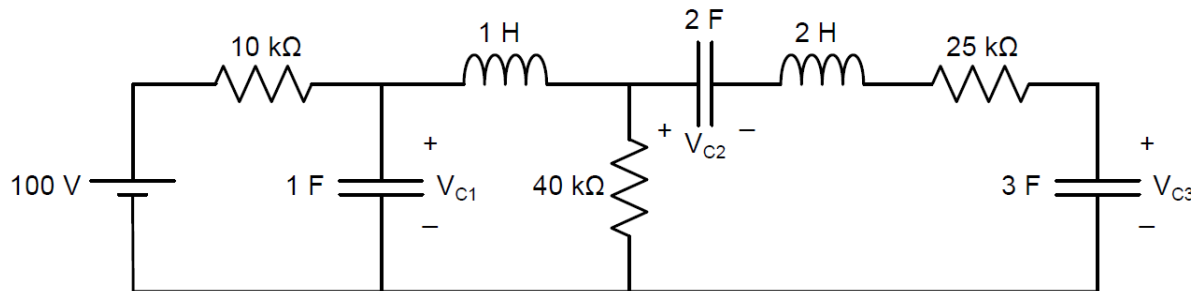
## Problem 14

In Fig find capacitor voltages  $V_{C1}$ ,  $V_{C2}$  and  $V_{C3}$  under steady state are respectively



Demonstration Using MATLAB

# Summary

- Understand and be able to use Star-delta conversion
- Understand and be able to use Superposition theorem
- Understand and be able to use Circuit analysis Techniques

