

# Lecture-32

## Ideal Transformer

Lecture delivered by:



# Topics

- EMF Induced in Transformer
- Transformer Rating
- Ideal Transformers
- Ideal Transformer under No-Load
- Practical Transformer





# Objectives

At the end of this lecture, student will be able to:

- Derive the EMF equation of Transformer and use it in calculations
- Identify the transformer ratings based on its name plate details
- Describe the properties of Ideal transformer
- Differentiate the Ideal and practical transformers
- Solve for primary voltage, secondary voltage, primary current and number of turns in the secondary given various transformer values



# EMF Induced in Transformer

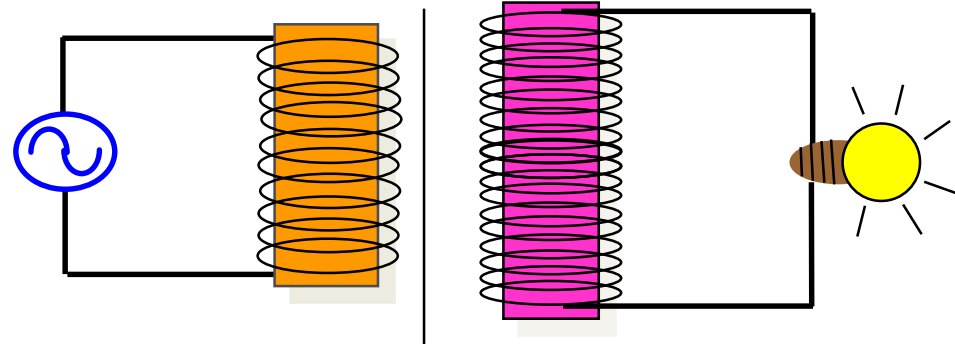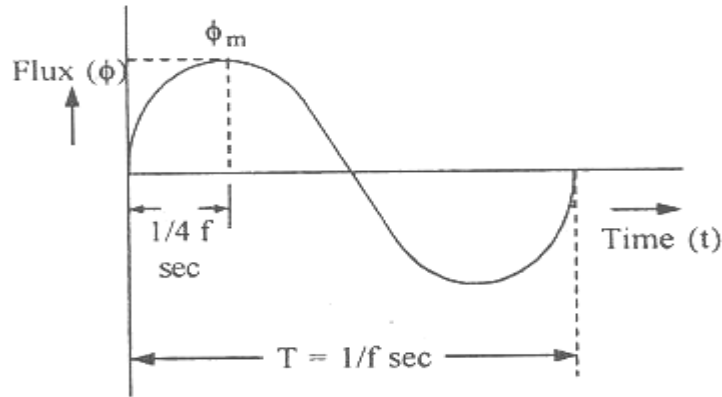

Flux  $\phi$  is produced which is given by an equation

$$\Phi = N_p i_p / S \quad \text{.....(1)}$$

where  $S$  is the reluctance



# EMF Induced in Transformer Cont..,

According to Faraday law of electromagnetic induction

$$v_p = N_p \frac{d\phi}{dt} \quad \text{.....(2)}$$

Substitute  $\phi = N_p i_p / S$  into the above equation , then

$$v_p = \frac{N_p^2}{S} \times \frac{d}{dt} (i_p) \quad \text{.....(3)}$$



# EMF Induced in Transformer Cont.,

If  $i_p$  is sinusoidal, the flux produced also sinusoidal, i.e

$$\Phi = \Phi_m \sin 2\pi ft \quad \text{.....(4)}$$

therefore 
$$v_p = N_p \frac{d(\Phi_m \sin 2\pi ft)}{dt}$$

$$v_p = N_p 2\pi f \Phi_m \cos 2\pi ft = N_p 2\pi f \Phi_m \sin (2\pi ft + \pi/2) \quad \text{.....(5)}$$

$$\text{The peak value} = V_{pm} = N_p 2\pi f \Phi_m \quad \text{.....(6)}$$

and  $v_p$  is leading the flux by  $\pi/2$ .

**The rms value** 
$$V_p = \frac{V_{pm}}{\sqrt{2}} = 0.707 \times N_p 2\pi f \Phi_m = 4.44 N_p f \Phi_m \quad \text{.....(7)}$$



# EMF Induced in Transformer Cont..,

From (2) and (8) we get

$$\frac{V_s}{V_p} = \frac{N_s}{N_p} \quad \text{.....(9)}$$

$$N_p I_p = N_s I_s$$

rearrange  $\frac{I_p}{I_s} = \frac{N_s}{N_p}$



# Transformer Rating

- If a transformer carries the **10kVA, 1100/110volts** information on its name-plate. **What are the meanings of these ratings?**
  - **Voltage ratio** indicates that the transformer has two windings, the high-voltage winding is rated for 1100 Volts and low-voltage winding for 110 volts.
  - The kVA rating means that each winding is designed for 10 kVA.  
**current rating** for the high-voltage winding =  $10000/1100 = 9.09\text{A}$   
**Current rating** for low voltage winding =  $10000/110 = 90.9\text{ A}$





# Problem

## Worked Example No.1

A 250 kVA, 11000V/400V, 50Hz single –phase transformer has 80 turns on the secondary. Calculate

- (a) The appropriate values of the primary and secondary currents;
- (b) The approximate number of primary turns;
- (c) the maximum value of the flux.

(a) Full-load primary current 
$$I_p = \frac{P}{V_p} = \frac{250 \times 10^3}{11000} = 22.7 \text{ A}$$

Full-load secondary current 
$$I_s = \frac{P}{V_s} = \frac{250 \times 10^3}{400} = 625 \text{ A}$$



# Problem

(b) Number of primary turns

recall  $\frac{V_s}{V_p} = \frac{N_s}{N_p}$

$$\longrightarrow N_p = \frac{N_s}{V_s} \times V_p = \frac{80}{400} \times 11000 = 2200$$

(c) Maximum flux

recall  $E = 4.44 N f \Phi_m$

$$\Phi_m = \frac{E_s}{4.44 N_s f} = \frac{400}{4.44 \times 80 \times 50} = 22.5 \text{ mWb}$$




# Ideal Transformers


- Ideal Transformer is a unity coupled, lossless transformer in which the primary and secondary coils have infinite self inductances.

Transformer is ideal if:

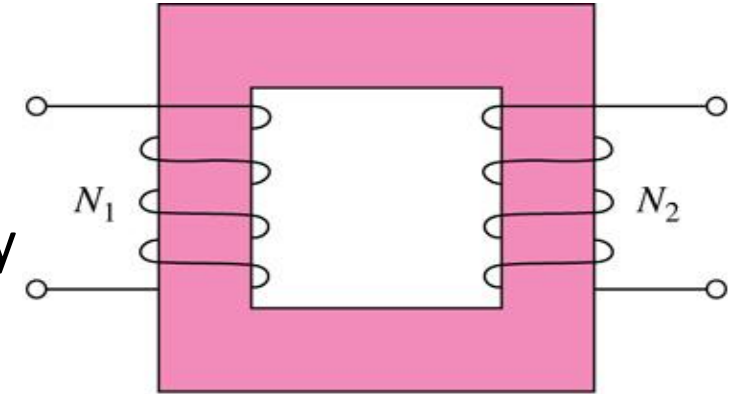- 1) Large reactance coils;  $L_1, L_2, M \rightarrow \infty$
- 2) Unity Coupling  $k=1$ .
- 3) Coils are lossless ( $R_1=R_2=0$ )



Ideal transformer

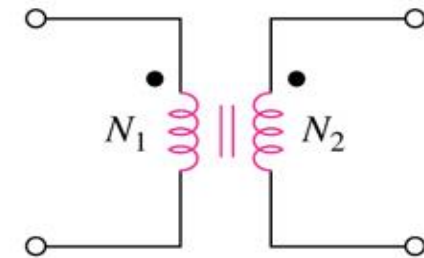

Circuit symbol for the Ideal transformer



# Variables of an Ideal Transformer

- Input and Output voltages and currents of an ideal transformer are related only by the turns ratio.


$$V_1 = j\omega L_1 I_1 + j\omega M I_2 \quad I_1 = \frac{V_1 - j\omega M I_2}{j\omega L_1}$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2 \quad V_2 = j\omega L_2 I_2 + \frac{M V_1}{L_1} - \frac{j\omega M^2 I_2}{L_1}$$

Perfect Coupling  $k = 1$ , Thus we have  $M = \sqrt{L_1 L_2}$  Substitute

$$V_2 = j\omega L_2 I_2 + \frac{\sqrt{L_1 L_2} V_1}{L_1} - \frac{j\omega L_1 L_2 I_2}{L_1} = \sqrt{\frac{L_2}{L_1}} V_1 = n V_1 = \frac{N_2}{N_1} V_1$$
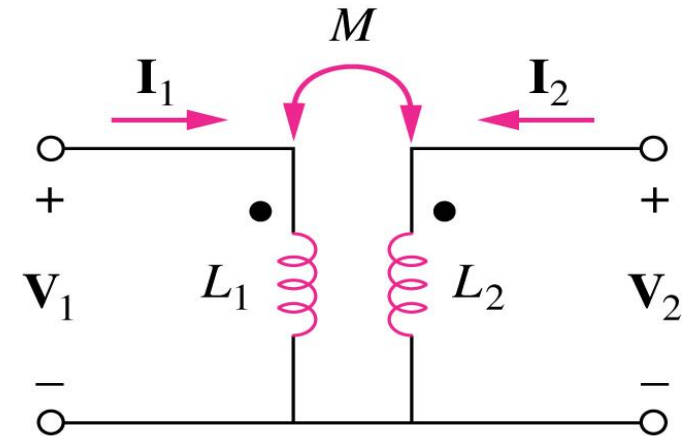
$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n = \text{Turns Ratio}$$




# Turns Ratio of an Ideal Transformer

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n = \text{Turns Ratio}$$

- A Ideal Transformer is called:
  - 1) Step-up transformer if  $n > 1$ .
  - 2) Step-down transformer if  $n < 1$ .
  - 3) Isolation transformer if  $n=1$ .



# Ideal Transformer with No Load

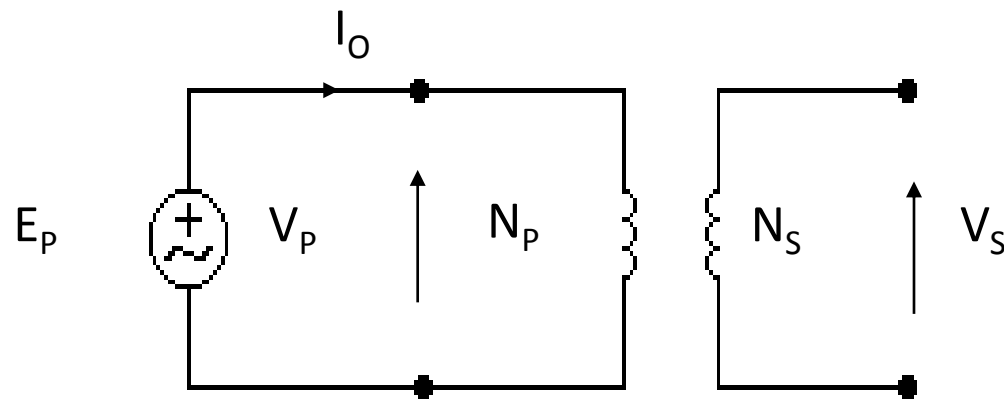

$I_o$  is the no load current when the secondary is open circuit.



# Ideal Transformer with No Load Cont...

$V_p$  = emf of supply to the primary coil


$E_p$  = emf induced in the primary coil

$V_s$  = emf induced in the secondary coil

$I_{om}$  = magnetizing current

$I_{o1}$  = current to compensate the losses due to hysteresis and eddy current.

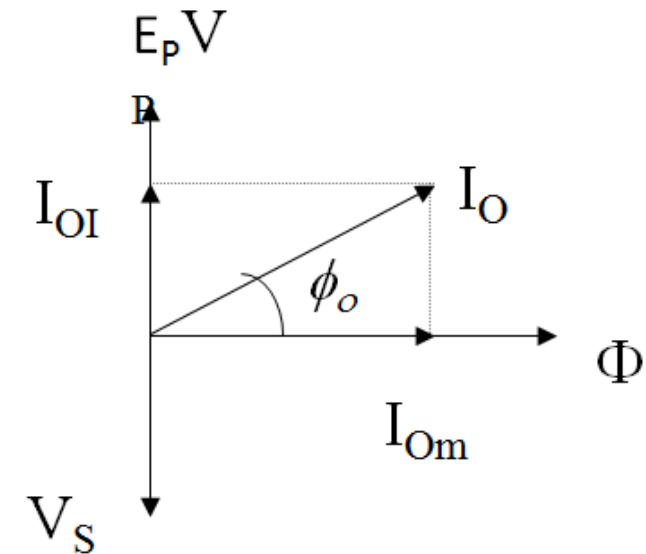$I_o$  = the no load current and given by



Phasor diagram for  
no load transformer

$$I_o = \sqrt{I_{om}^2 + I_{o1}^2}$$


Power factor  $\cos \phi_o = \frac{I_{o1}}{I_o}$


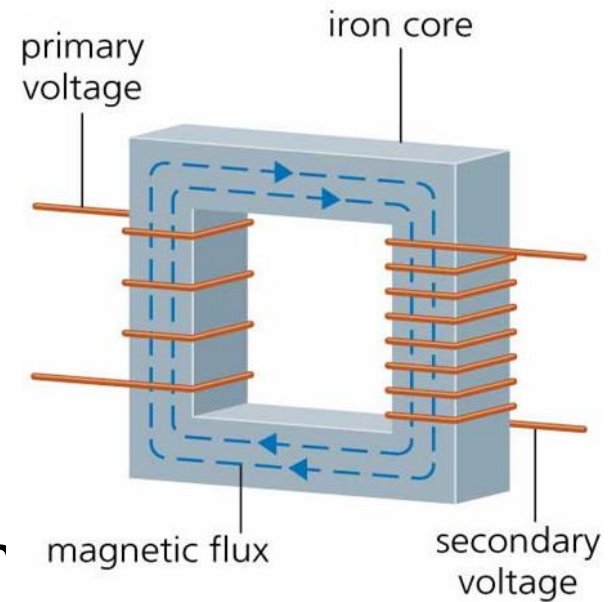
# Practical Transformer

Practical transformer has

- Copper resistance
- Leakage flux
- Finite core permeability (i.e., finite  $\mu_r$ )
- Core loss



**Note:** Practically no transformer is ideal. Knowledge of ideal transformer helps us to develop the concept of behavior of practical transformer






# Problem

## Worked Example No.2

The diagram shows a transformer. Calculate the voltage across the secondary coil of this transformer.

## Solution

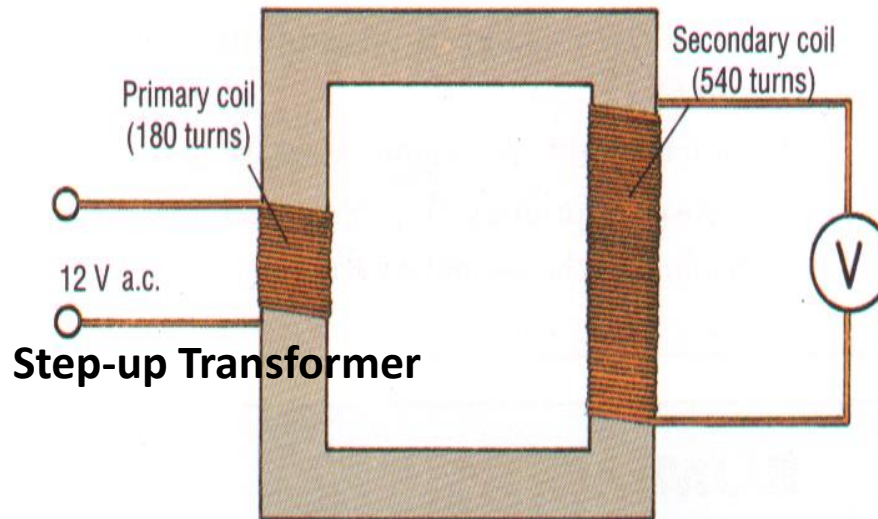

$$\frac{V_P}{V_S} = \frac{N_P}{N_S}$$

Substituting

$$\frac{12}{V_S} = \frac{180}{540}$$

Crossmultiplying

$$180 \cdot V_S = 12 \times 540$$

$$\therefore V_S = \frac{12 \times 540}{180}$$

$$\therefore V_S = 36 \text{ V}$$



# Problem


## Worked Example No. 3

A transformer which has 1380 turns in its primary coil is to be used to convert the mains voltage of 230 V to operate a 6 V bulb. How many turns should the secondary coil of this transformer have?

## Solution

$$V_P = 230 \text{ V}$$

$$N_P = 1380$$

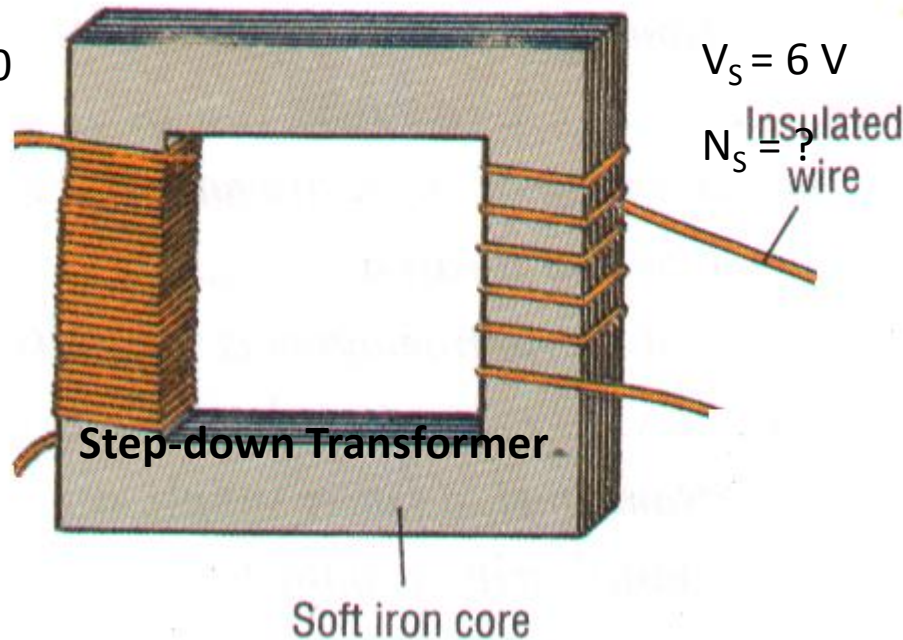

$$\frac{V_P}{V_S} = \frac{N_P}{N_S}$$

Substituting

$$\frac{230}{6} = \frac{1380}{N_S}$$

Crossmultiplying

$$2300 \cdot N_S = 6 \times 13800$$

$$\therefore N_S = \frac{6 \times 1380}{230}$$

$$\therefore N_S = 36 \text{ turns}$$



# Summary

- EMF equation of Transformer is  $E = 4.44 N f \Phi_m$
- Losses are zero in an ideal transformer
- An ideal transformer divides a sinusoidal input voltage by a factor of  $a$  and multiplies a sinusoidal input current by  $a$  to obtain secondary voltage and current.
- If a transformer increases the voltage, the current decreases and vice versa.

