

# Lecture-33

## Circuit model of a Transformer

Lecture delivered by:



# Topics

- Ideal Transformer under On Load
- Circuit Model of Transformer under No-Load condition
- Circuit Model of Transformer under Load condition




# Objectives

At the end of this lecture, student will be able to:


- State the meaning of a "no-load condition" and "on-load condition" relative to a transformer
- Describe the operation of ideal transformer under on-load condition
- Construct a transformer on-load phasor diagram for different loads
- Derive the equivalent resistance and reactance referred to the primary and secondary side of a transformer



# Ideal Transformer On Load

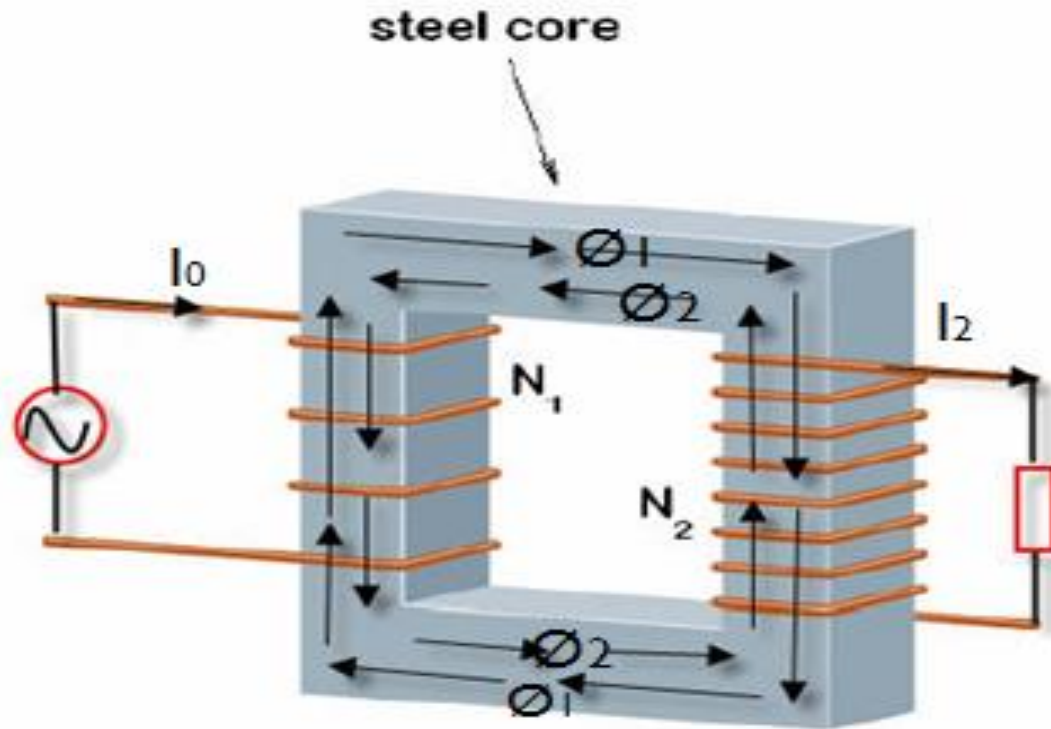

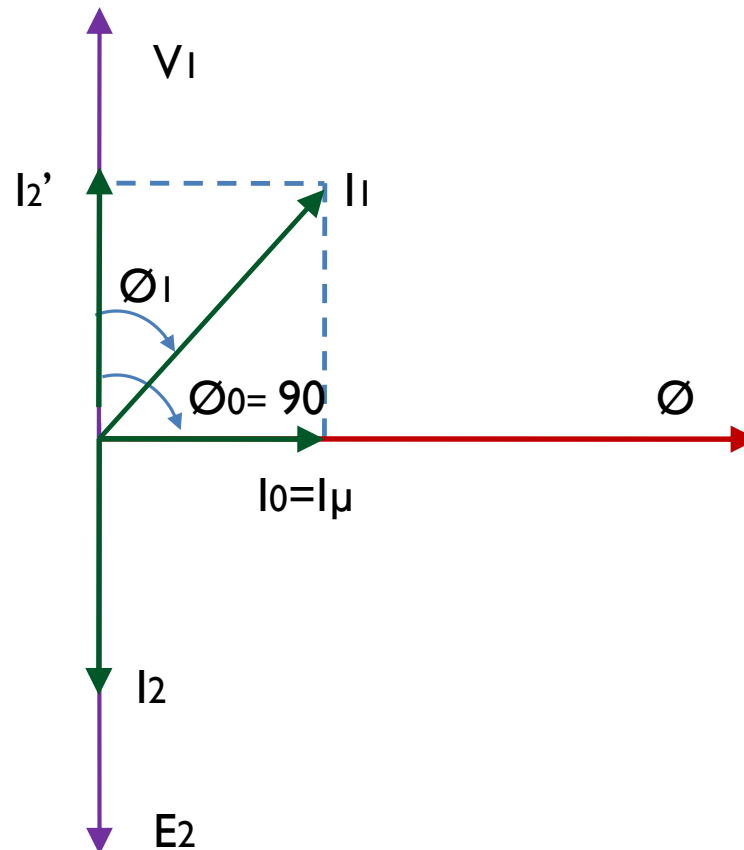
# Phasor Diagram of Ideal Transformer For Resistive Load :



Phasor diagram for resistive load



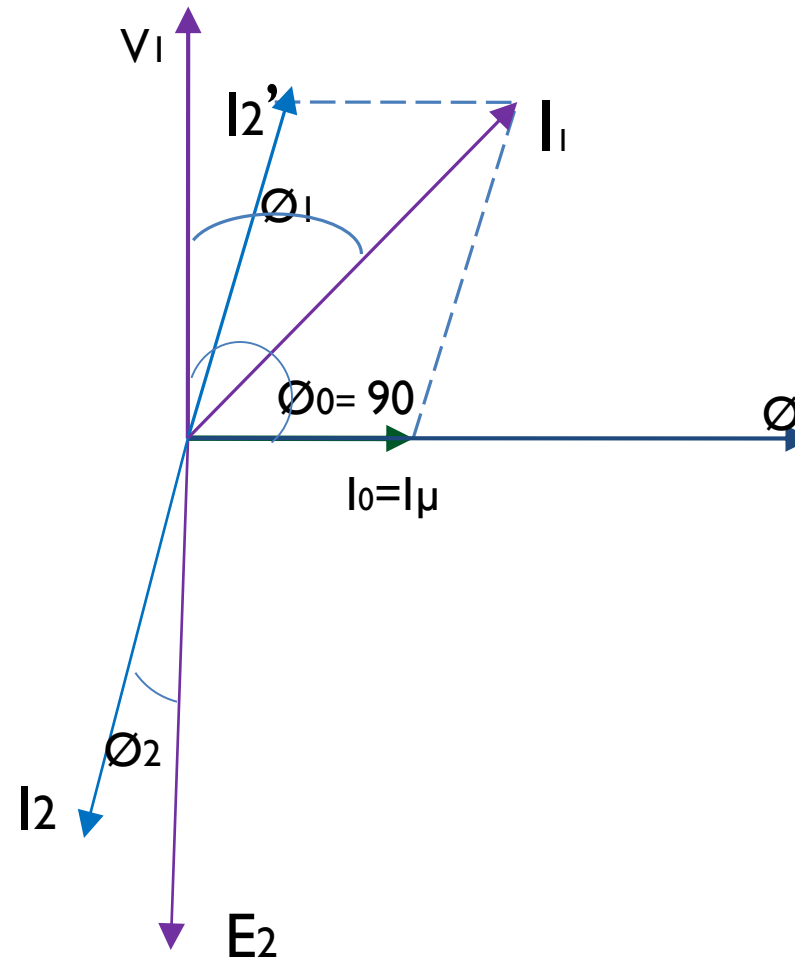
# Phasor Diagram of Ideal transformer for inductive load



Phasor diagram for inductive load


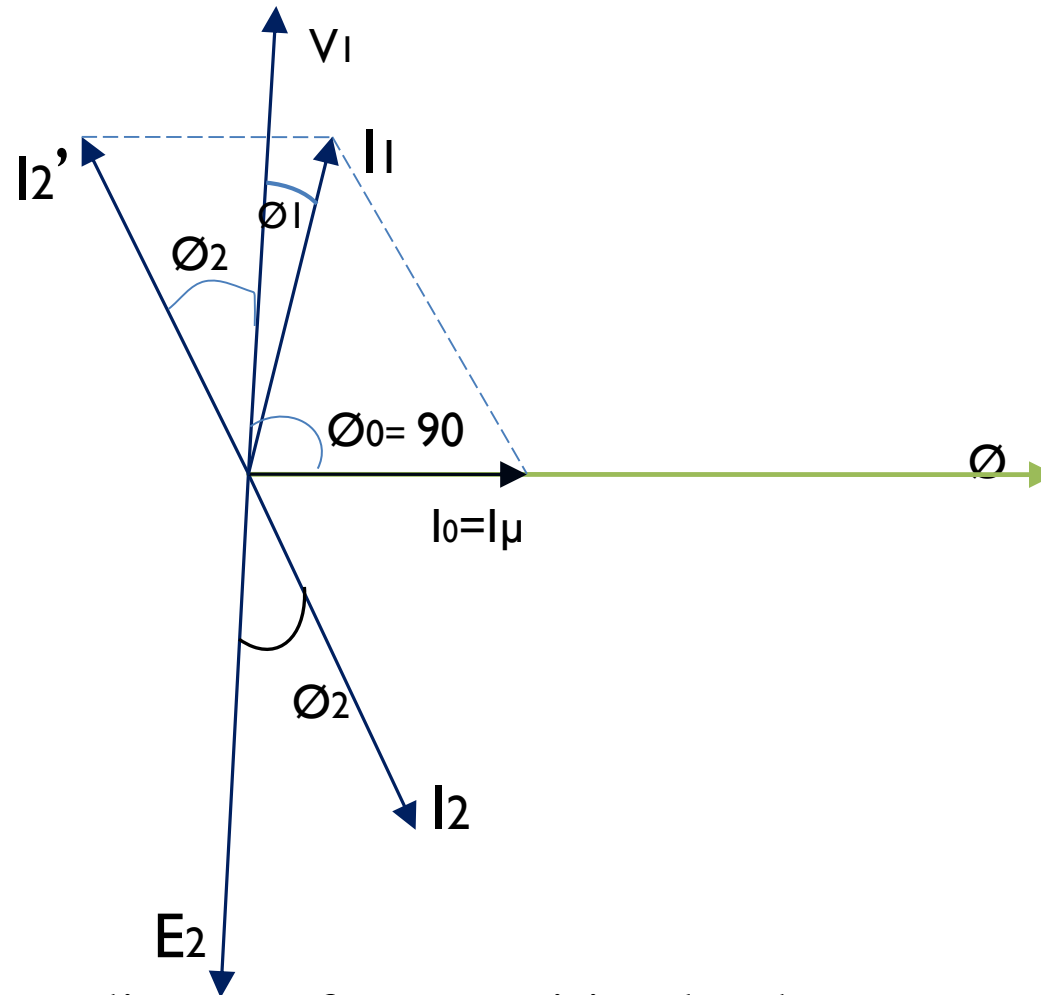
# Phasor Diagram of Ideal transformer for Capacitive load




Phasor diagram for capacitive load



# Equivalent Circuit of Transformer

## No Load Equivalent Circuit

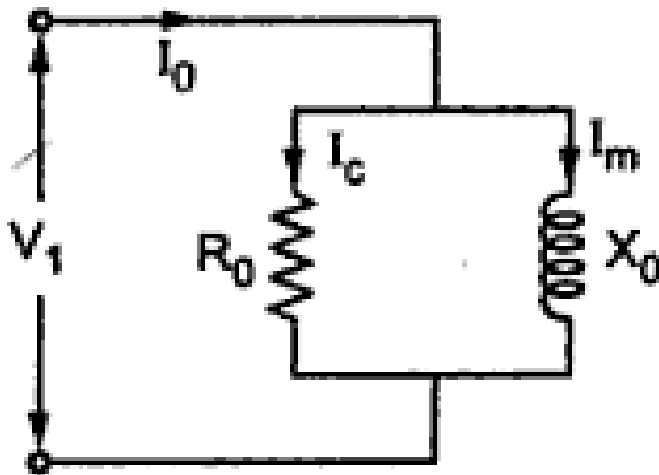

$$R_0 = \frac{V_1}{I_c}$$

$$X_0 = \frac{V_1}{I_m}$$


$$I_m = I_0 \sin \phi_0 = \text{Magnetising component}$$

$$I_c = I_0 \cos \phi_0 = \text{Active component}$$





# Equivalent Circuit with Load

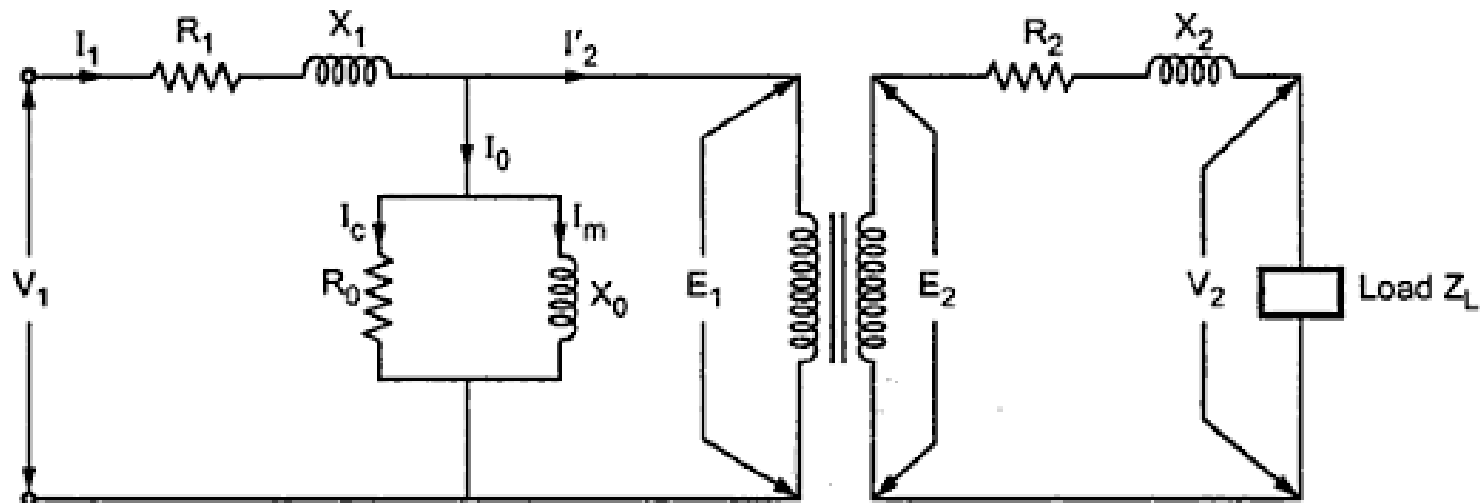

# Equivalent Circuit with Load Cont..

$$I_2^2 R_2 = I_1^2 R_2^1$$

$$\therefore R_2^1 = \frac{I_2^2}{I_1^2} R_2$$

$$R_2^1 = \frac{R_2}{K^2} \quad \text{where} \quad K = \frac{I_1}{I_2}$$

The  $R_2^1$  is called the secondary resistance referred to primary.




# Equivalent Circuit Referred to Primary Side

## Transferring Secondary Side Parameters to Primary Side



$$R'_2 = \frac{R_2}{K^2}, \quad X'_2 = \frac{X_2}{K^2}, \quad Z'_2 = \frac{Z_2}{K^2}$$

While  $E'_2 = \frac{E_2}{K}, \quad I'_2 = KI_2$

where  $K = \frac{N_2}{N_1}$

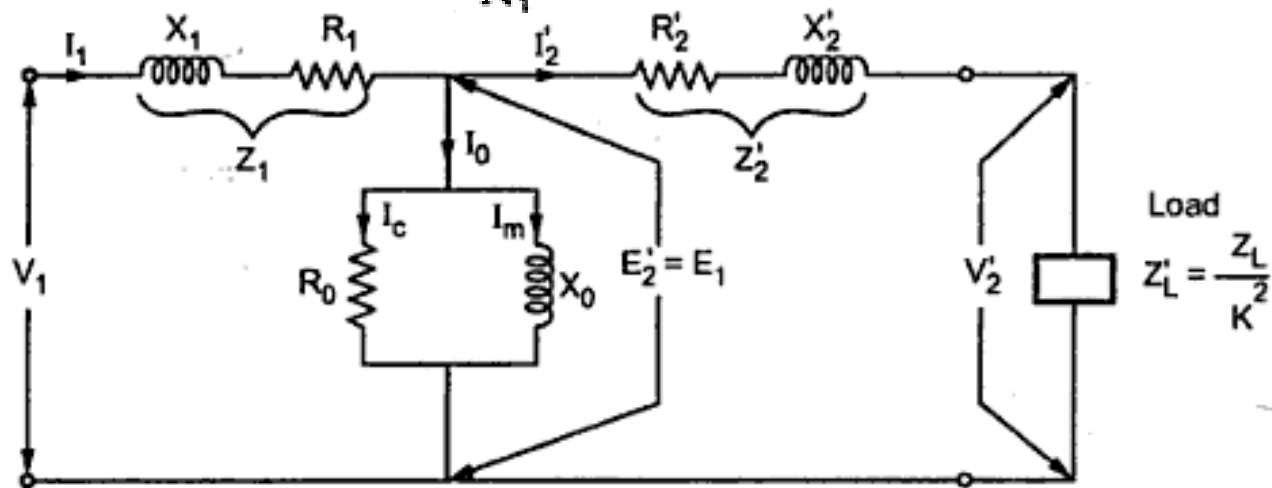

# Problem

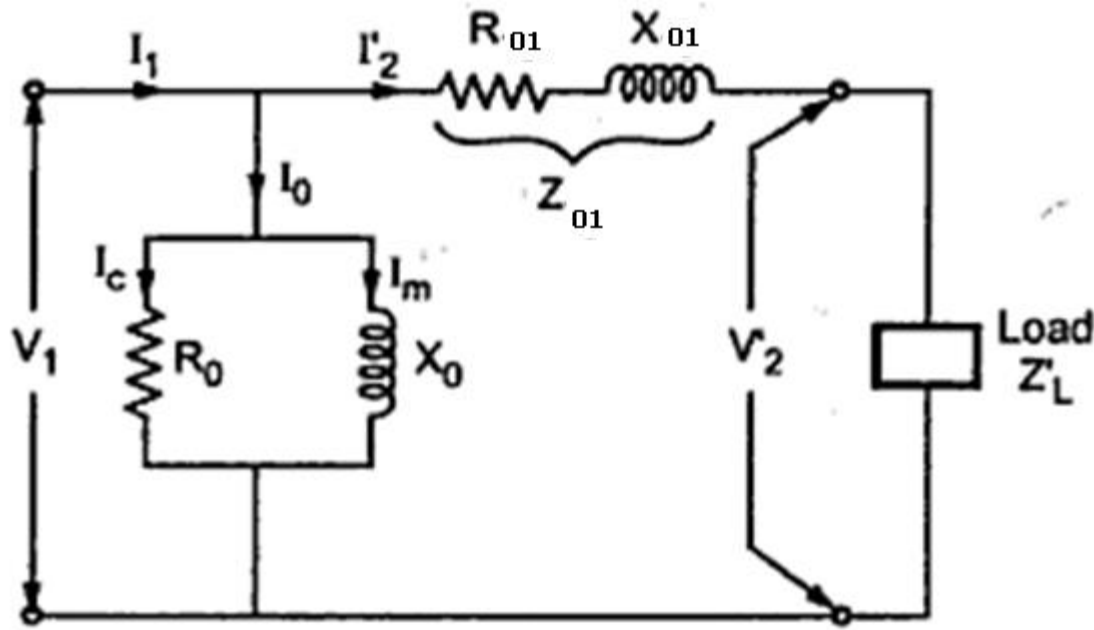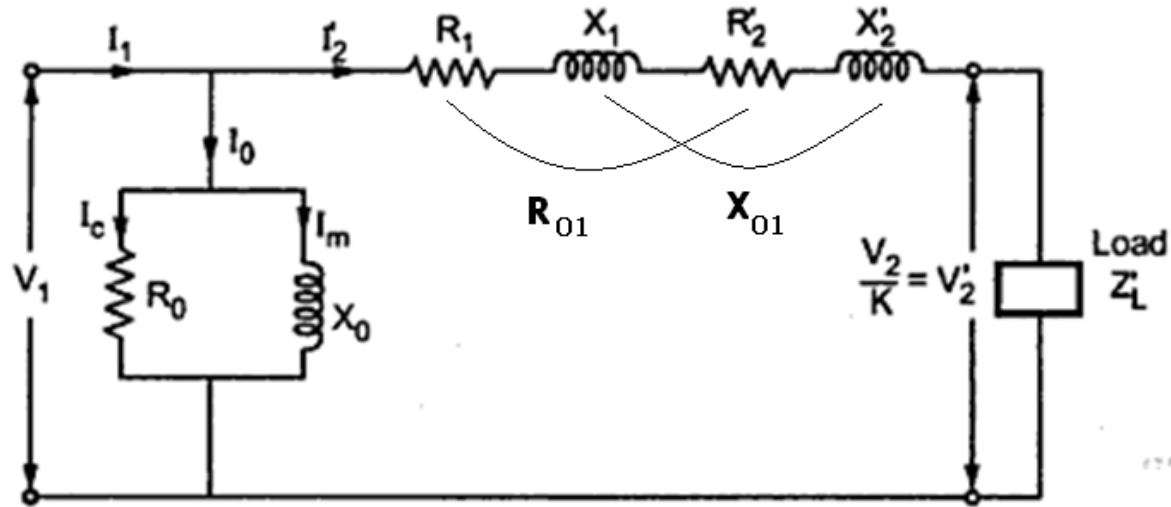

where

$$R_{01} = R_1 + R_2' = R_1 + \frac{R_2}{K^2}$$

$$X_{01} = X_1 + X_2' = X_1 + \frac{X_2}{K^2}$$

$$Z_{01} = R_{01} + j X_{01}$$




# Equivalent Circuit Referred to Secondary Side

## Transferring Primary Side Parameters to Secondary Side


$$R'_1 = K^2 R_1, \quad X'_1 = K^2 X_1, \quad Z'_1 = K^2 Z_1$$

$$E'_1 = K E_1, \quad I'_1 = \frac{I_1}{K}, \quad I'_0 = \frac{I_0}{K}$$

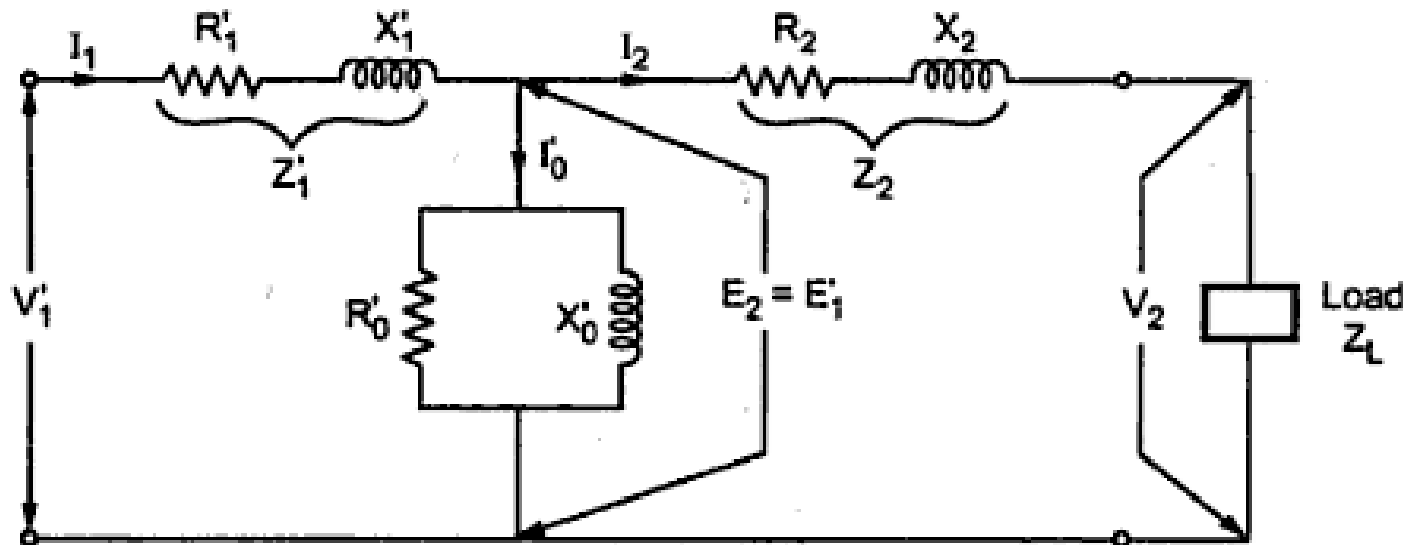Similarly exciting circuit parameters are also transferred to secondary as  $R'_0$  and  $X'_0$



# Approximate Equivalent Circuit

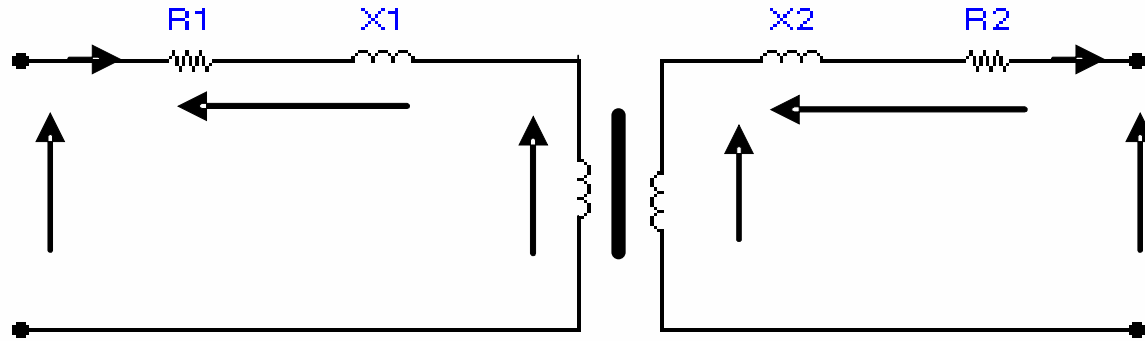

$$I_1^2 R_{2'} = I_2^2 R_2$$

$$R_{2'} = R_2 \left( \frac{I_2}{I_1} \right)^2 \approx R_2 \left( \frac{V_1}{V_2} \right)^2$$

Similarly

$$X_{2'} = X_2 \left( \frac{N_1}{N_2} \right)^2 \approx X_2 \left( \frac{V_1}{V_2} \right)^2$$



# Equivalent Circuit

$$R_e = R_1 + R_2' = R_1 + R_2 \left( \frac{V_1}{V_2} \right)^2$$

$$X_e = X_1 + X_2' = X_1 + X_2 \left( \frac{V_1}{V_2} \right)^2$$



then  $Z_e = \sqrt{R_e^2 + X_e^2}$

where  $R_e = Z_e \cos \phi_e$

$$X_e = Z_e \sin \phi_e$$

and

$$\tan \phi_e = \frac{X_e}{R_e}$$

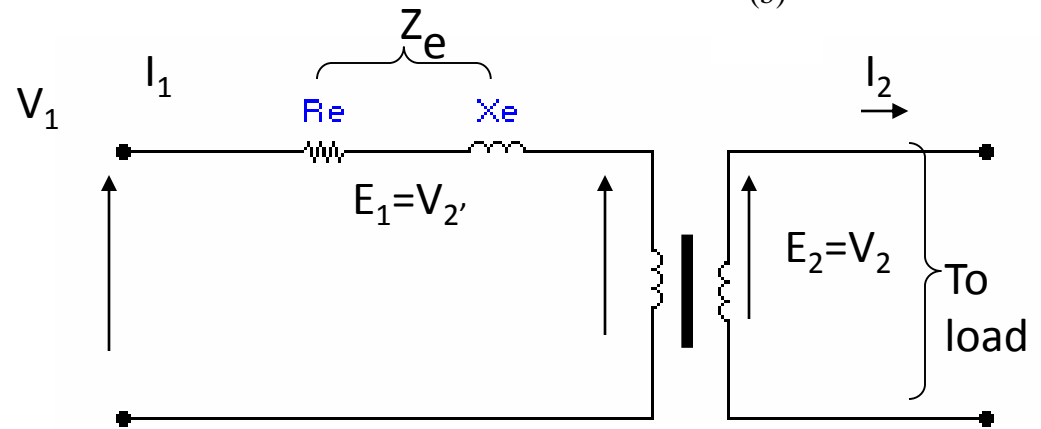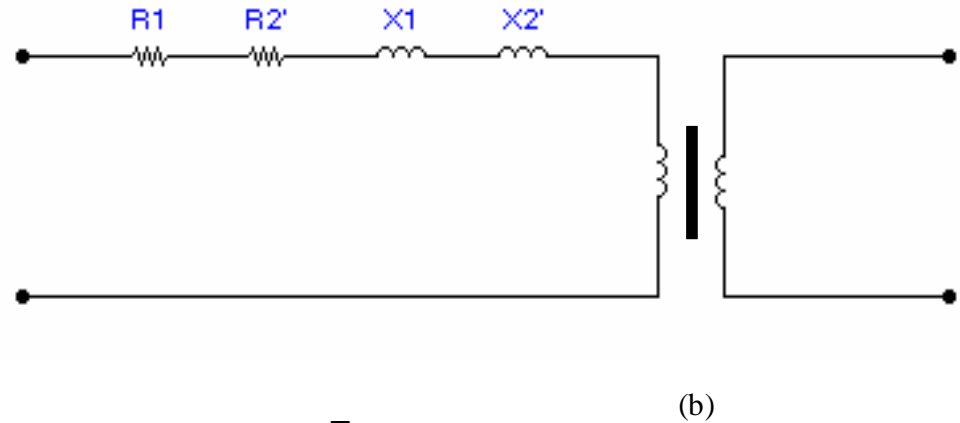

transformer simplified circuit



# Example

•A single-phase transformer has 1000 turns on the primary and 200 turns on the secondary. The no load current is 3A at a power factor 0.2 lagging when secondary current is 280A at a power factor of 0.8 lagging. Calculate the primary current and the power factor. Assume the voltage drop in the windings to be negligible.

Solution:

$$\frac{I_p}{I_s} = \frac{N_s}{N_p}$$

$$I_p = \frac{N_s}{N_p} \times I_s = \frac{200}{1000} \times 280 = 56A$$





# Problem

$$\cos \phi_{2'} = 0.8 \quad \therefore \sin \phi_{2'} = 0.6$$

$$\cos \phi_o = 0.2 \quad \therefore \sin \phi_o = 0.98$$

Solve for horizontal and vertical components


$$\begin{aligned} I_1 \cos \phi_1 &= I_{2'} \cos \phi_{2'} + I_o \cos \phi_o \\ &= (56 \times 0.8) + (3 \times 0.2) = 45.4 A \end{aligned}$$

$$\begin{aligned} I_1 \sin \phi_1 &= I_{2'} \sin \phi_{2'} + I_o \sin \phi_o \\ &= (56 \times 0.6) + (3 \times 0.98) = 36.54 A \end{aligned}$$

$$I_1 = \sqrt{(45.4)^2 + (36.54)^2} = 58.3 A$$

$$\tan \phi_1 = \frac{36.54}{45.4} = 0.805 \quad \longrightarrow \quad \phi_1 = 38^\circ 50'$$

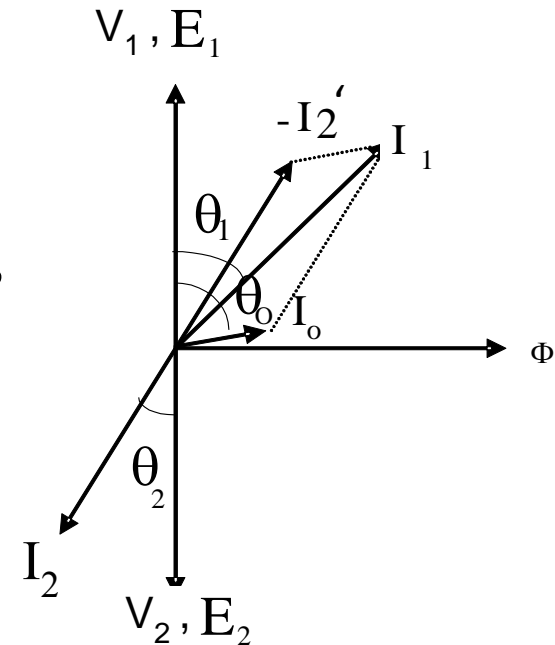Power factor  $\cos \phi_1 = \cos 38^\circ 50' = 0.78 \text{ lagging}$



# Summary

- Operation of ideal transformer under on-load condition
- Phasor diagrams of the transformer at different loads
- Development of equivalent circuit of a transformer referred to primary side
- Development of equivalent circuit of a transformer referred to secondary side

