

Circuit Analysis Techniques



Lecture 10

Tutorial

Lecture delivered by:



Objectives

At the end of this lecture, student will be able to:


- Solve problems on Thevenin's Theorem
- Solve problems on Superposition Theorem



Thevenin's Theorem

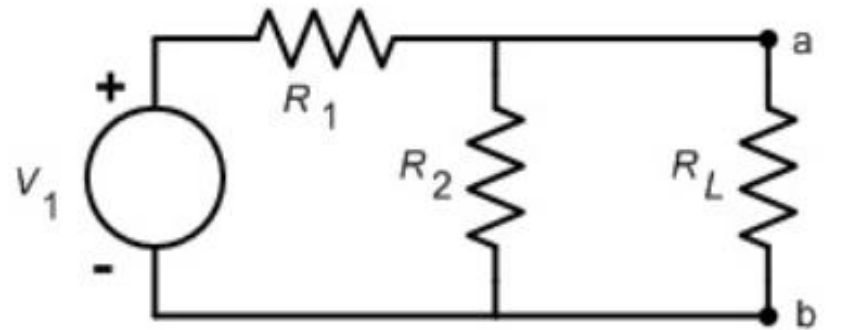Problem 5:

Obtain the load current through R_L using Thevenin's theorem.




$$V_1 = 42 \text{ V}, \quad R_1 = 3 \, \Omega, \quad R_2 = 6 \, \Omega, \quad R_L = 12 \, \Omega$$

Thevenin's Theorem

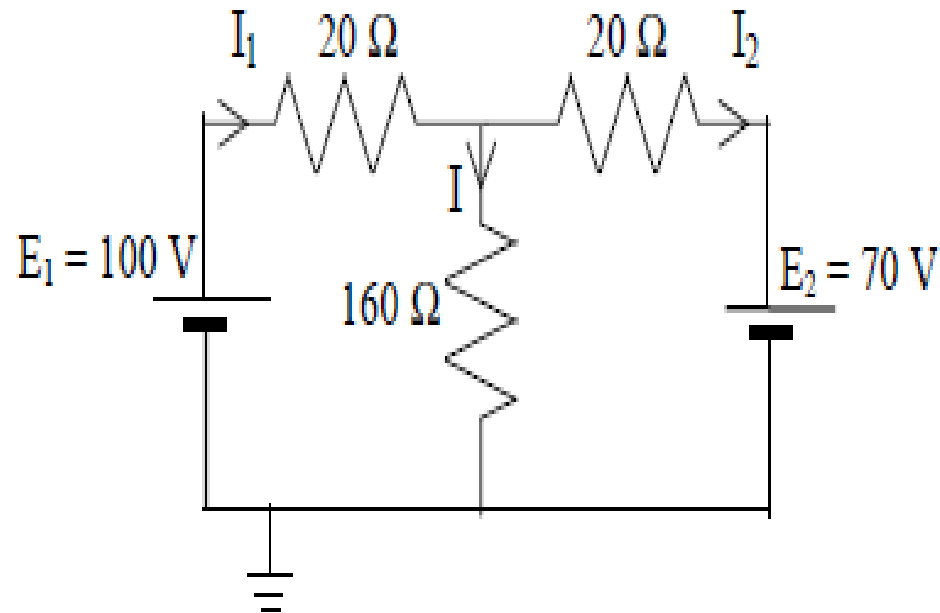Example 6:


Obtain the load current I using Thevenin's theorem.



Thevenin's Theorem

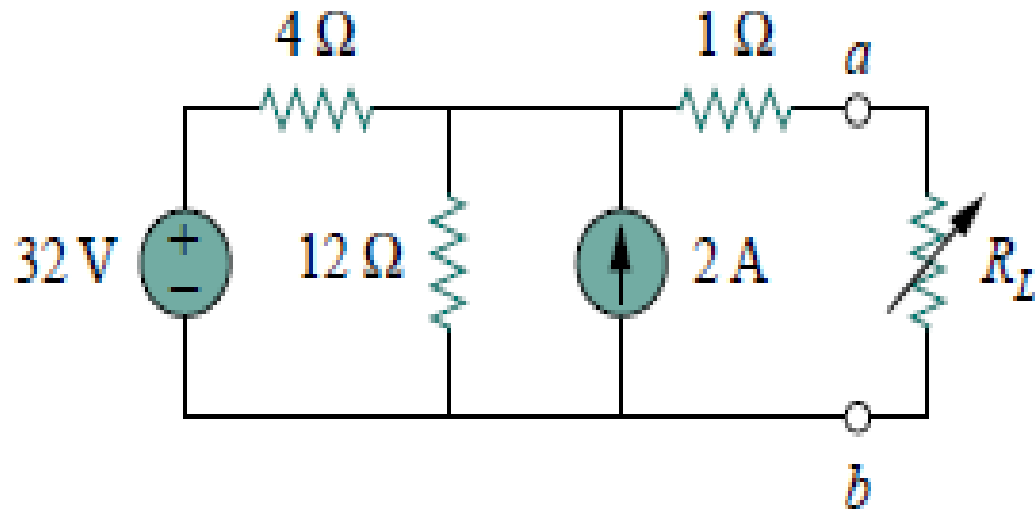Problem 7:


Find the load current through $R_L = 6, 16$ and 36Ω using Thevenin's theorem for the given circuit.



Norton's Theorem

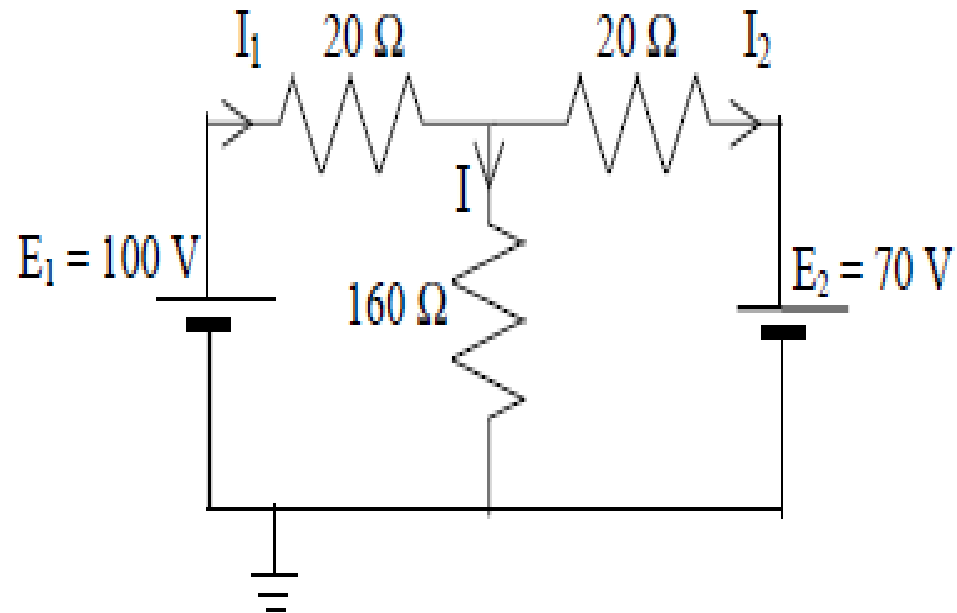Problem 8:

Obtain the load current I using Norton's theorem.



Summary

- Understand and be able to use Thevenin's theorem
- Understand and be able to use Norton's theorem

