

# Circuit Analysis Techniques



# Lecture 9

## Tutorial

Lecture delivered by:



# Objectives

At the end of this lecture, student will be able to:


- Solve problems on Superposition Theorem



# Superposition Theorem
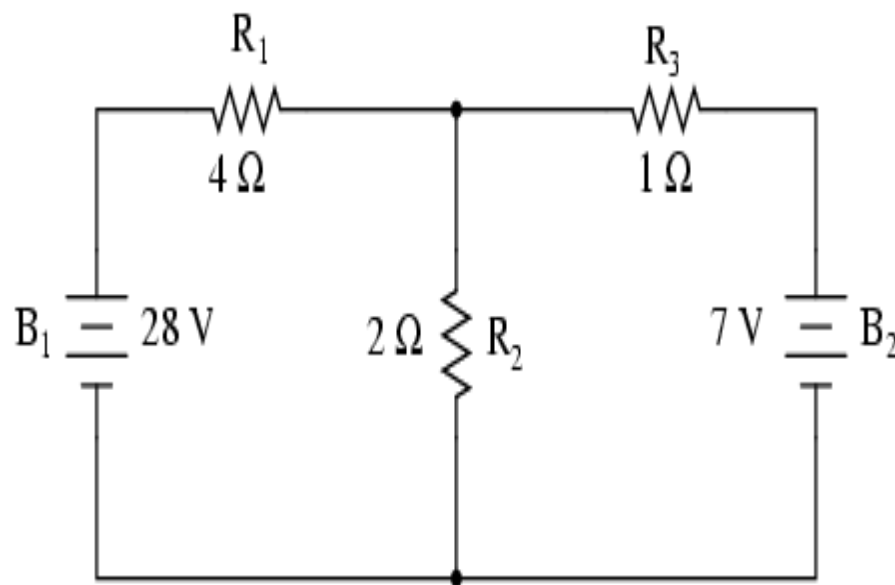
## Problem 1:


Calculate the current flowing through  $2\ \Omega$  resistor in the given circuit by applying Superposition theorem.



# Superposition Theorem
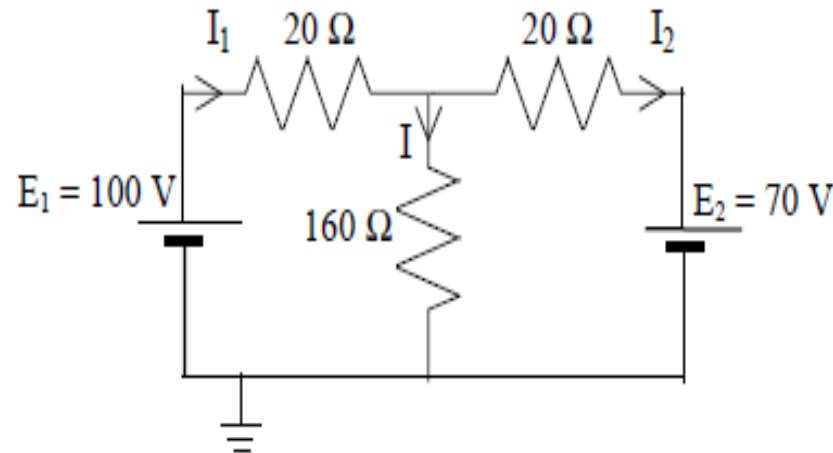
## Example 2:


Calculate the current flowing through  $2\ \Omega$  resistor in the given circuit by applying Superposition theorem.



# Superposition Theorem
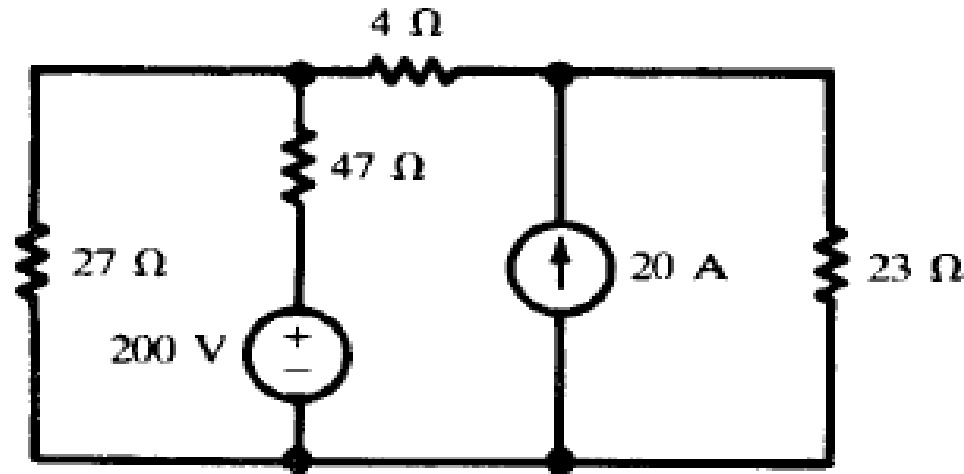
## Problem 3:


Calculate the current flowing through  $23\ \Omega$  resistor in the given circuit by applying Superposition theorem.



# Superposition Theorem
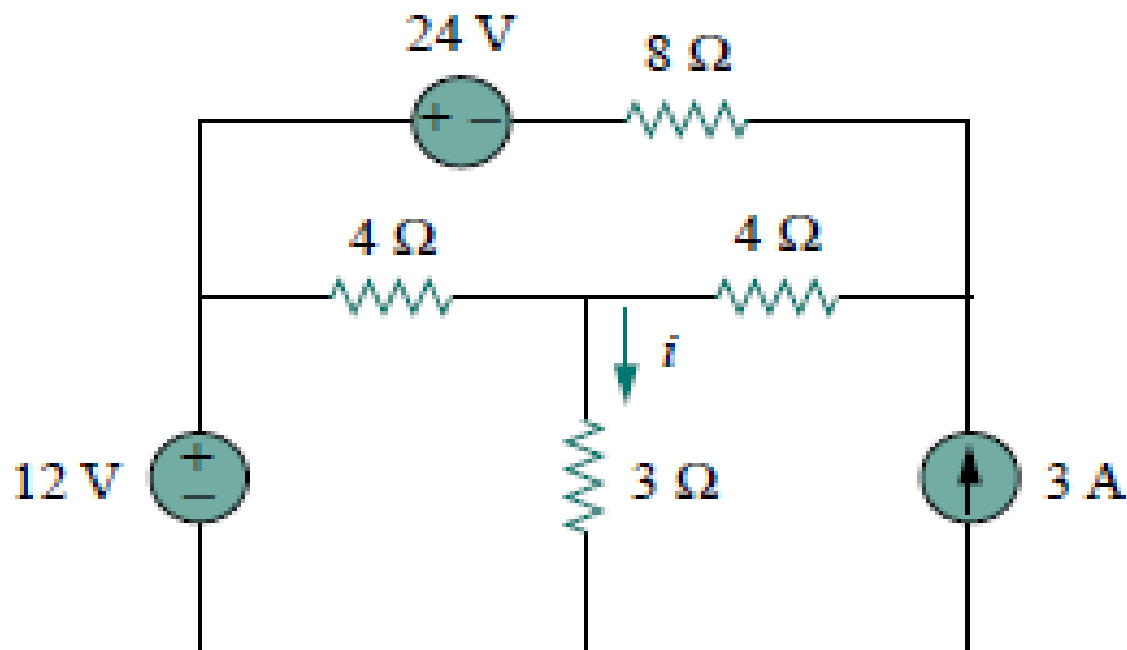
## Problem 4:

Calculate the current flowing through  $3\ \Omega$  resistor in the given circuit by applying Superposition theorem.



# Summary

- Understand and be able to use superposition theorem.

