

Lecture No. 47

DC Generator (Types & Characteristics)

Lecture delivered by



Objectives

At the end of this lecture, student will be able to:

- Derive an expression for induced E.M.F.
- Classify DC Generators based upon methods of excitation
- Discuss Open Circuit and Load characteristics of DC Generators
- Explain the losses associated with DC machines



E.M.F. Generated in An Armature Winding

Z = number of armature conductors,

ϕ = useful flux per pole, in webers

p = number of **pairs of poles**

and n = armature speed in rev/s

- The e.m.f. generated by the armature is equal to the e.m.f. generated by one of the parallel paths.



E.m.f. generated in an armature winding

- Each conductor passes $2p$ poles per revolution and thus cuts $2p\phi$ webers of magnetic flux per revolution.

$$= 2p\phi n \quad \text{Wb}$$

so the average e.m.f. E generated per conductor is given by:

$$E = 2p\phi n \quad \text{Volts}$$

(since 1 volt = 1 Weber per second)



E.m.f. generated in an armature winding

- c = number of parallel paths through the winding between positive and negative brushes

$c = 2$ for a wave winding

$c = 2p$ for a lap winding

- The number of conductors in series in each path Z/c
- The total e.m.f. between brushes
= (average e.m.f./conductor)(number of conductors in series per path)

$$= 2p\phi n * Z/c$$

$$\text{i.e., generated e.m.f.}, E = \frac{2p\Phi n Z}{c} \text{ volts}$$



E.m.f. generated in an armature winding

- Since Z , p and c are constant for a given machine, then $E \propto \phi_n$. However

$2\pi n$ is the angular velocity ω in radians per second, hence the generated e.m.f. is proportional to ϕ and ω , i.e.,

$$\text{generated e.m.f.}, E \propto \phi \omega$$



Problem

- **Problem 1.** An 8-pole, wave-connected armature has 600 conductors and is driven at 625 rev/min. If the flux per pole is 20 mWb, determine the generated e.m.f.

Solⁿ $Z = 600, c = 2$ (for a wave winding), $p = 4$ pairs

$$n = \frac{625}{60} \text{ rev / s}, \quad \Phi = 20 \times 10^{-3} \text{ Wb}$$

$$\text{Generated e.m.f.}, E = \frac{2p\Phi nZ}{c}$$

$$= \frac{2(4)(20 \times 10^{-3}) \left(\frac{625}{60} \right) (600)}{2} = 500 \text{ volts}$$




DC Generator

- DC generators are classified according to the method of their field excitation. These groupings are
 - **Separately-excited generators**
 - **Self-excited generators**
 - (a) shunt
 - (b) series, and
 - (c) compound wound generators



Types of DC generator

- Separately-excited generator -

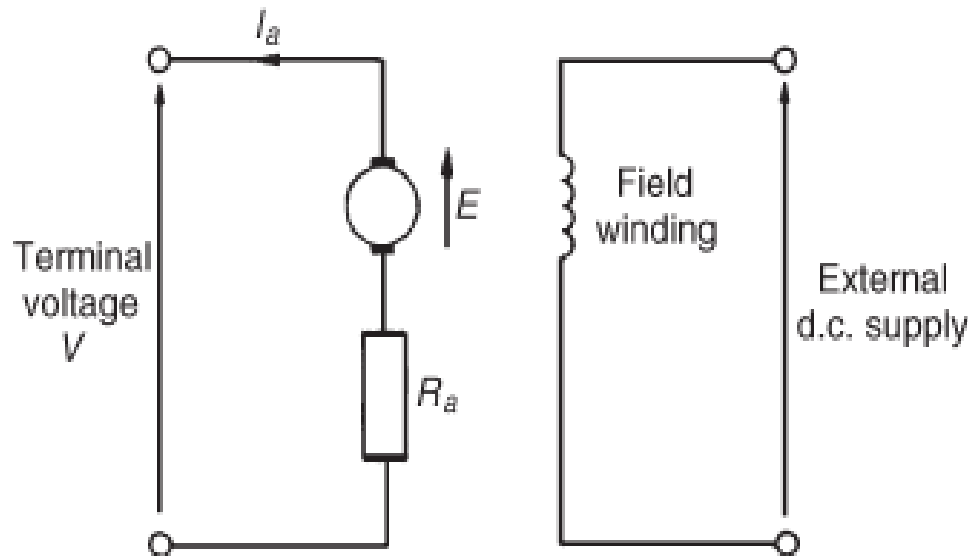

terminal voltage,

$$V = E - I_a R_a$$



Problem

- **Problem 7.** Determine the terminal voltage of a generator which develops an e.m.f. of 200 V and has an armature current of 30 A on load. Assume the armature resistance is 0.30

- **Solⁿ** $V = E - I_a R_a = 200 - (30)(0.30) = 200 - 9 = \mathbf{191 \text{ volts}}$



- **Problem 8.** A generator is connected to a 60Ω load and a current of 8 A flows. If the armature resistance is 1Ω determine (a) the terminal voltage, and (b) the generated e.m.f.

(a) Terminal voltage, $V = I_a R_L = (8)(60) = \mathbf{480 \text{ volts}}$

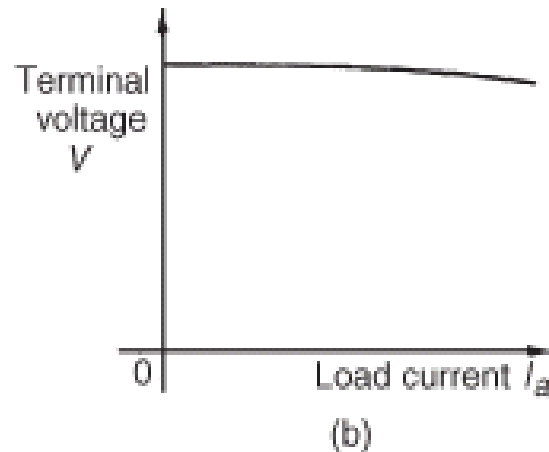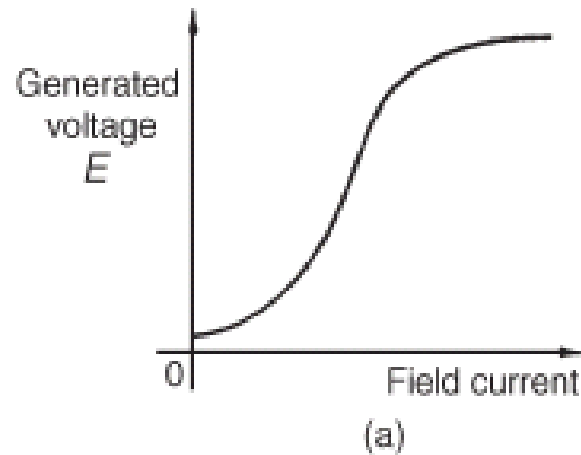(b) Generated e.m.f., $E = V + I_a R_a$

$$= 480 + (8)(1) = 480 + 8 = \mathbf{488}$$

Separately-excited Generator Characteristics




a) Open circuit characteristics

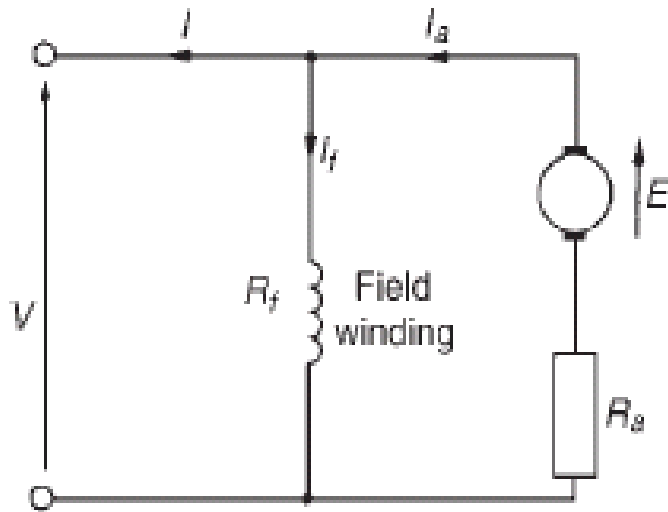b) Load characteristics



Shunt-wound generator

- In a shunt wound generator the field winding is connected in parallel with the armature as shown in Figure. The field winding has a relatively high resistance and therefore the current carried is only a fraction of the armature current



For the circuit shown :

$$\text{terminal voltage } V = E - I_a R_a$$

$$\text{or generated e.m.f., } E = V + I_a R_a$$

$$I_a = I_f + I, \text{ from kirchhoff 's current law,}$$

where I_a = armature current

$$I_f = \text{field current} \left(\frac{V}{R_f} \right)$$


and I = load current



Problem

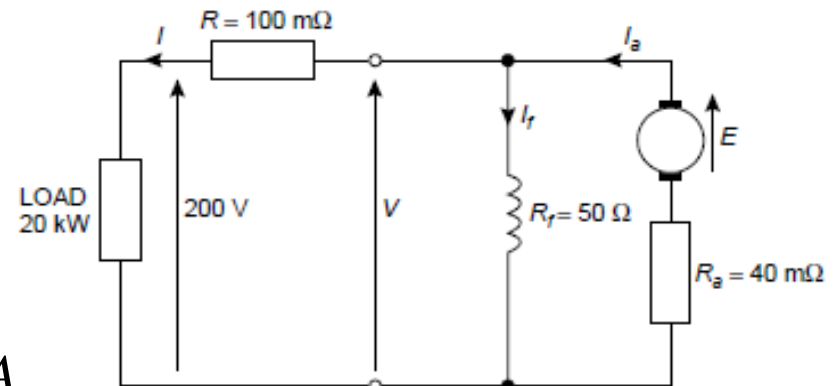- Problem 10.** A shunt generator supplies a 20 kW load at 200 V through cables of resistance, $R = 100 \text{ m}\Omega$. If the field winding resistance, $R_f = 50 \Omega$ and the armature resistance, $R_a = 40 \text{ m}\Omega$, determine (a) the terminal voltage, and (b) the e.m.f. generated in the armature

Solⁿ : -The circuit is as shown in Figure (a)



$$\text{Load current, } I = \frac{20000 \text{ watts}}{200 \text{ volts}} = 100 \text{ A}$$



Problem

$$\text{Volt drop in the cables to the load} = IR = (100)(100 \times 10^{-3}) \\ = 10V$$

$$\text{Hence terminal voltage, } V = 200 + 10 = 210 \text{ volts}$$

$$(b) \text{ Armature current } I_a = I_f + I$$


$$\text{Field current, } I_f = \frac{V}{R_f} = \frac{210}{50} = 4.2A$$

$$\text{Hence } I_a = I_f + I = 4.2 + 100 = 104.2A \\ = 210 + (104.2)(40 \times 10^{-3}) \\ = 214.17 \text{ volts}$$




Shunt Generator Characteristics

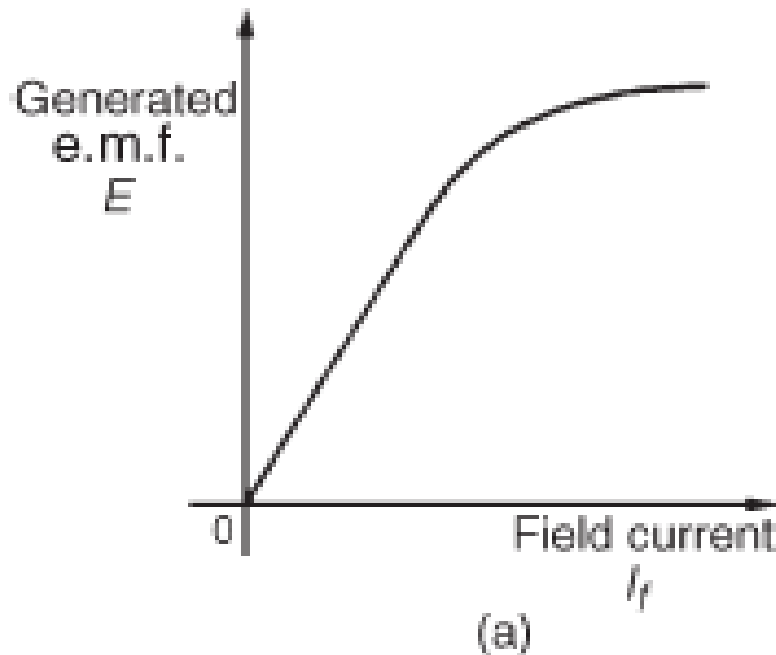- The generated e.m.f., E , is proportional to ϕ , hence at constant speed, since $\omega = 2\phi n$,
- E / ϕ Also the flux ϕ is proportional to field current I_f until magnetic saturation of the iron circuit of the generator occurs.




Shunt-wound Generator Characteristics

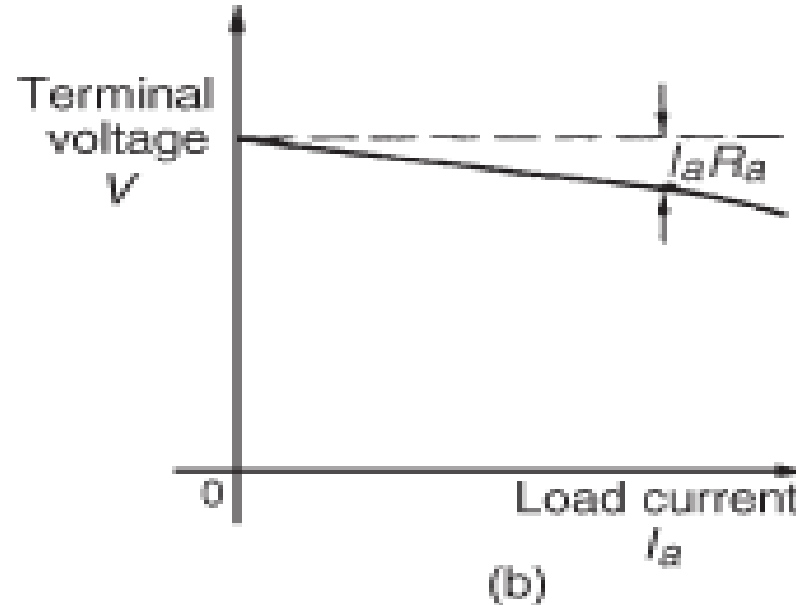- As the load current on a generator having constant field current and running at constant speed increases, the armature volt drop, $I_a R_a$ increases




Series-wound Generator

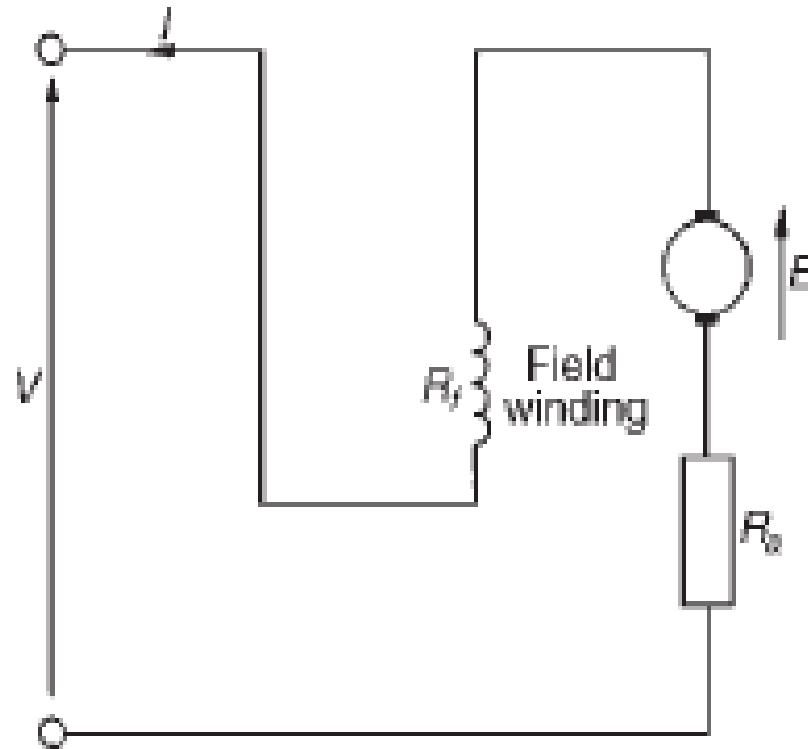


Series-wound Generator

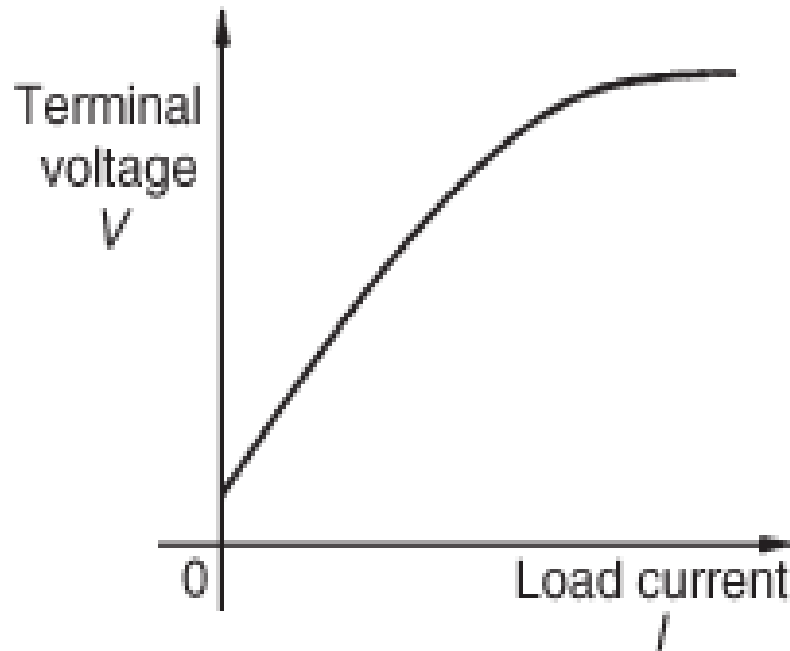- The values of field resistance and armature resistance in a series wound machine are small, hence the terminal voltage V is very nearly equal to E .




Compound-wound Generator

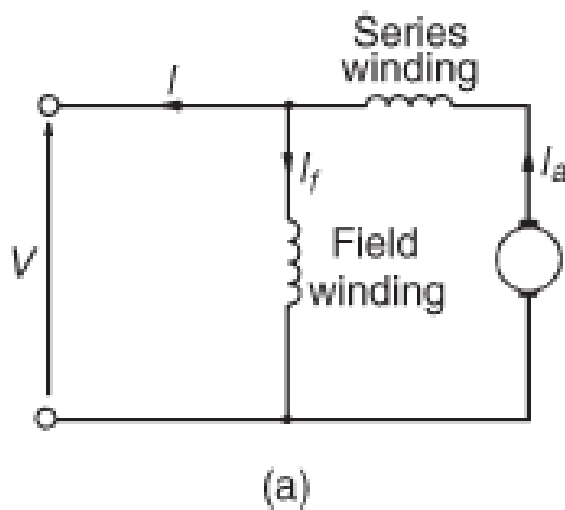- Compound-wound generator consists both shunt and series windings



Long Shunt

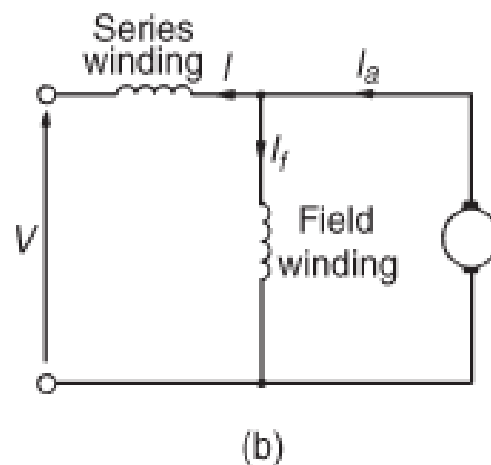


Short Shunt



Problem

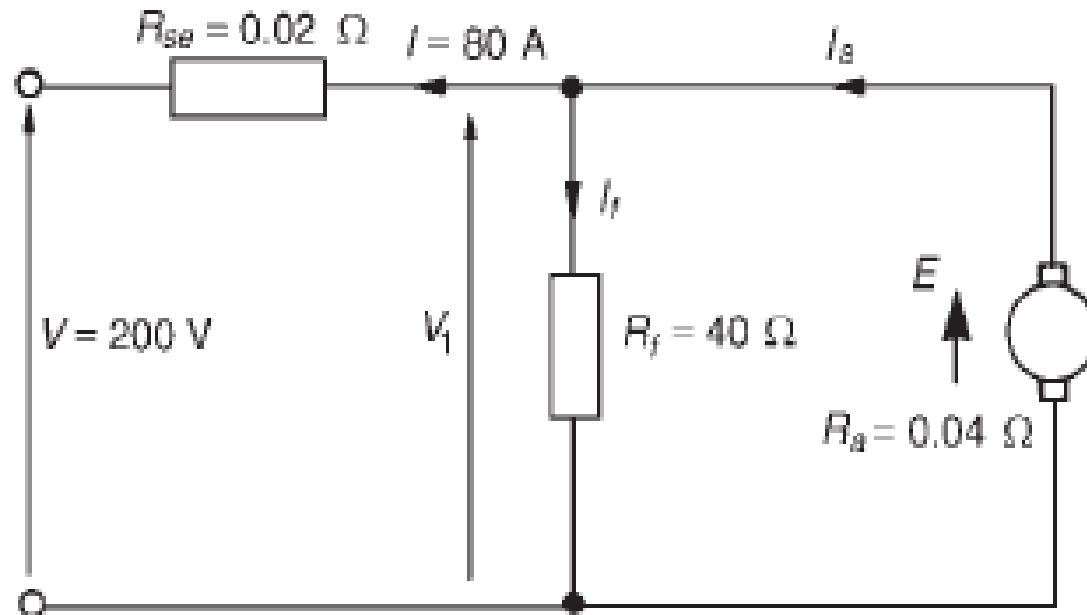- Problem 11. A short-shunt compound generator supplies 80 A at 200 V. If the field resistance, $R_f = 40$, the series resistance, $R_{se} = 0.02$ and the armature resistance, $R_a = 0.04\Omega$, determine the e.m.f. generated.



Problem

Solⁿ

$$\text{Volt drop in series winding} = IR_{se} = (80)(0.02) = 1.6 \text{ V}$$

$$\begin{aligned}\text{P.d. across the field winding} &= \text{p.d. across armature} \\ &= V_1 = 200 + 1.6 = 201.6 \text{ V}\end{aligned}$$


$$\text{Field current } I_f = \frac{V_1}{R_f} = \frac{201.6}{40} = 5.04 \text{ A}$$

$$\text{Armature current, } I_a = I + I_f = 80 + 5.04 = 85.04 \text{ A}$$

$$\begin{aligned}\text{Generated e.m.f., } E &= V_1 + I_a R_a \\ &= 201.6 + (85.04)(0.04) \\ &= 205 \text{ volts}\end{aligned}$$



D.C. Machine Losses

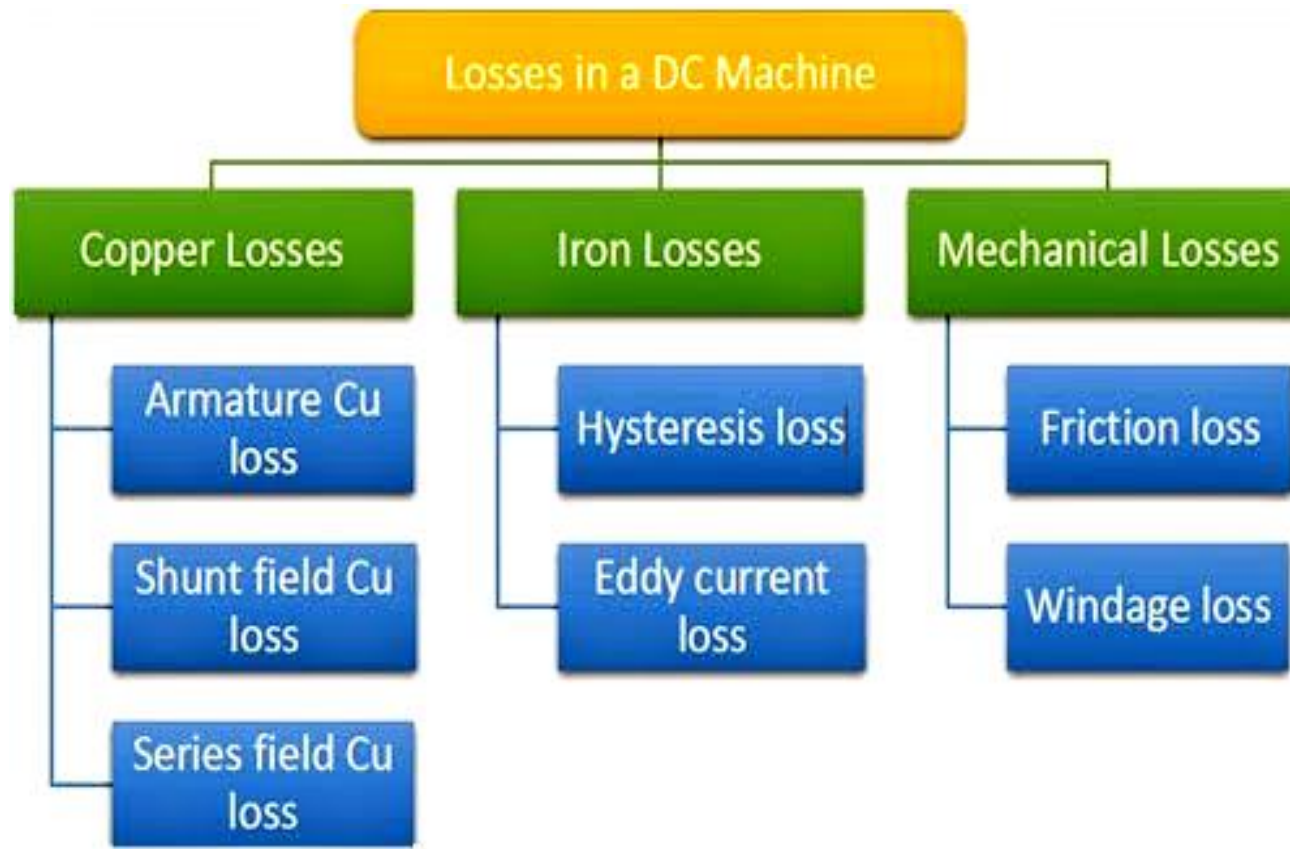

Efficiency of a D.C. Generator

efficiency, $\eta =$

$$\text{efficiency, } \eta = \left(\frac{\text{output power}}{\text{input power}} \right) \times 100\%$$

- Armature copper loss- $I_a^2 R_a$
- Field copper loss- $I_f V$



Efficiency of a D.C. Generator

- the total losses is given by

$$I_a^2 R_a + I_f V + C \quad (I_a^2 R_a + I_f V \text{ is, in fact, the 'copper loss'})$$

Total input power = $VI + I_a^2 R_a + I_f V + C$. Hence

$$\text{efficiency, } \eta = \frac{\text{output}}{\text{input}} = \left(\frac{VI}{VI + I_a^2 R_a + I_f V + C} \right) \times 100\%$$

- The efficiency of a generator is a maximum when the load is such that:


$$I_a^2 R_a = VI_f + C$$

i.e., when the variable loss = the constant loss



Problem

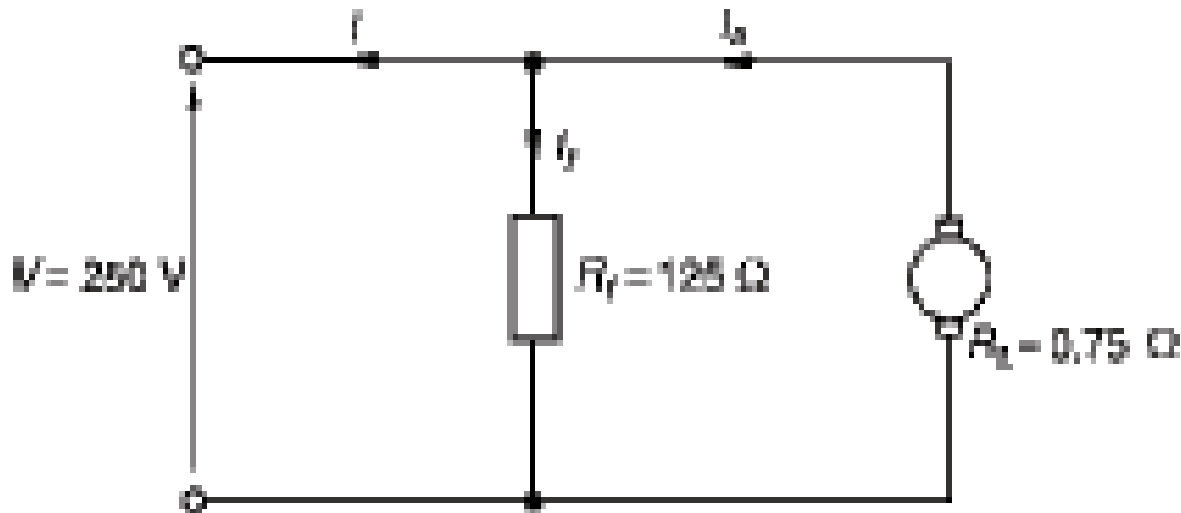- Problem 12.** A 10 kW shunt generator having an armature circuit resistance of 0.75Ω and a field resistance of 125Ω , generates a terminal voltage of 250 V at full load. Determine the efficiency of the generator at full load, assuming the iron, friction and windage losses amount to 600 W.



Problem

Solⁿ

$$\text{Output power} = 10\,000 \text{ W} = VI$$

$$\text{from which, load current } I = \frac{10\,000}{V} = \frac{10\,000}{250} = 40 \text{ A}$$

$$\text{Field current, } I_f = \frac{V}{R_f} = \frac{250}{125} = 2 \text{ A}$$

$$\text{Armature current, } I_a = I_f + I = 2 + 40 = 42 \text{ A}$$

$$\begin{aligned} \text{Efficiency, } \eta &= \left(\frac{VI}{VI + I_a^2 R_a + I_f V + C} \right) \times 100\% \\ &= \left(\frac{VI}{10\,000 + (42)^2 (0.75) + (2)(250) + 600} \right) \times 100\% \\ &= 80.50\% \end{aligned}$$



Problem

Problem 13. The armature of a d.c. machine has a resistance of 0.25 and is connected to a 300 V supply. Calculate the e.m.f. generated when it is running: (a) as a generator giving 100 A, and (b) as a motor taking 80 A.

(a) As a generator, generated e.m.f.,

$$\begin{aligned} E &= V + I_a R_a, \\ &= 300 + (100)(0.25) \\ &= 300 + 25 = 325 \text{ volts} \end{aligned}$$

(b) As a motor, generated e.m.f. (or back e.m.f.),

$$\begin{aligned} E &= V - I_a R_a, \\ &= 300 - (80)(0.25) = 280 \text{ volts} \end{aligned}$$



Summary

- Induced emf in a DC machine is proportional to speed and flux per pole
- OCC of Shunt Generator is similar to B-H curve
- As the load increases on a shunt generator its terminal voltage decreases
- Efficiency of a DC machine is maximum when variable loss is equal to constant loss

