

# Lecture-40

## Equivalent Circuit of 3 - phase Induction Motor

Lecture delivered by:



# Topics

- Equivalent Circuit of three phase Induction Motor
- Torque-speed characteristics



# Objectives


At the end of this lecture, student will be able to:

- Develop the equivalent circuit of 3 - phase Induction Motor
- Describe the torque-speed characteristics of 3 - phase Induction Motor
- Derive the Torque equation of 3 - phase Induction Motor
- Describe the power flow of 3 - phase Induction Motor


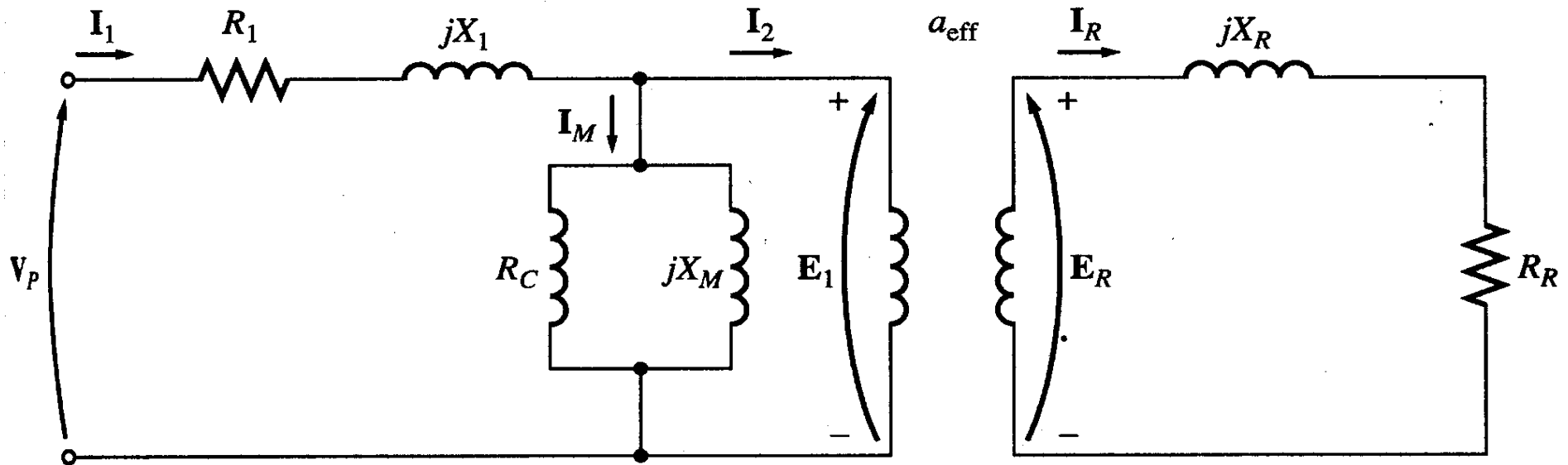
# Equivalent Circuit

- The induction motor is similar to the transformer with the exception that its secondary windings are free to rotate.



# Equivalent Circuit

- When the rotor is locked (or blocked), i.e.  $s = 1$ , the largest voltage and rotor frequency are induced in the rotor, **Why?**
- On the other side, if the rotor rotates at synchronous speed, i.e.  $s = 0$ , the induced voltage and frequency in the rotor will be equal to zero,

**Why?**

$$E_R = sE_{R0}$$

- Where  $E_{R0}$  is the largest value of the rotor's induced voltage obtained at  $s = 1$  (locked rotor)



# Equivalent Circuit

- The same is true for the frequency, i.e.

$$f_r = s f_e$$

- It is known that

$$X = \omega L = 2 \pi f L$$

- So, as the frequency of the induced voltage in the rotor changes, the reactance of the rotor circuit also changes


Where  $X_{r0}$  is the rotor reactance  
at the supply frequency  
(at blocked rotor)

$$\begin{aligned} X_r &= \omega_r L_r = 2\pi f_r L_r \\ &= 2\pi s f_e L_r \\ &= s X_{r0} \end{aligned}$$


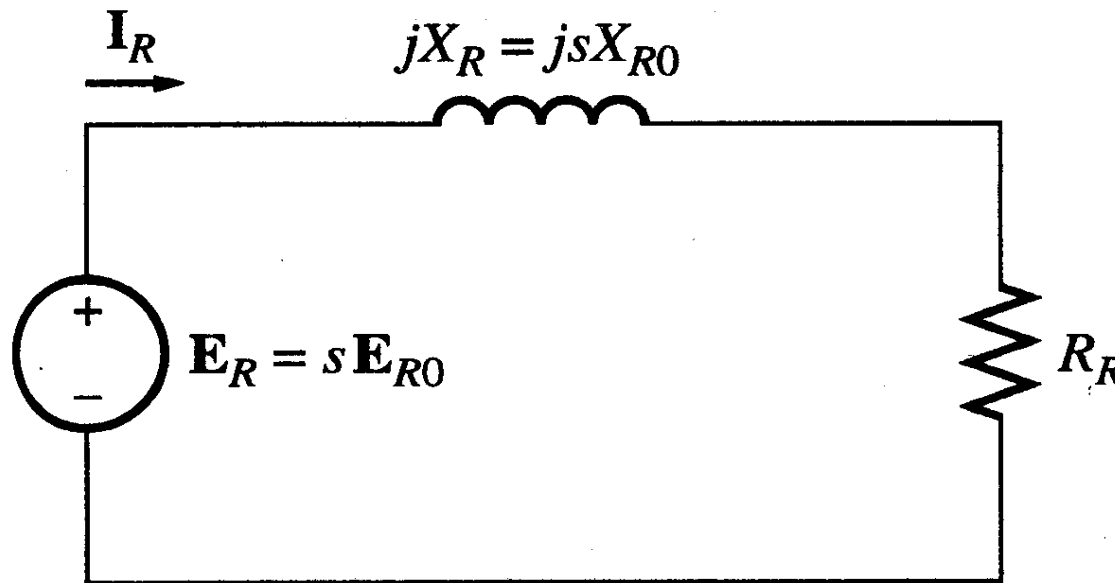
# Equivalent Circuit

- Then, we can draw the rotor equivalent circuit as follows



Where  $E_R$  is the induced voltage in the rotor and  $R_R$  is the rotor resistance



# Equivalent Circuit

- Now we can calculate the rotor current as

$$I_R = \frac{E_R}{(R_R + jX_R)}$$
$$= \frac{sE_{R0}}{(R_R + jsX_{R0})}$$

- Dividing both the numerator and denominator by  $s$  so nothing changes we get

$$I_R = \frac{E_{R0}}{\left(\frac{R_R}{s} + jX_{R0}\right)}$$


Where  $E_{R0}$  is the induced voltage and  $X_{R0}$  is the rotor reactance at blocked rotor condition ( $s = 1$ )




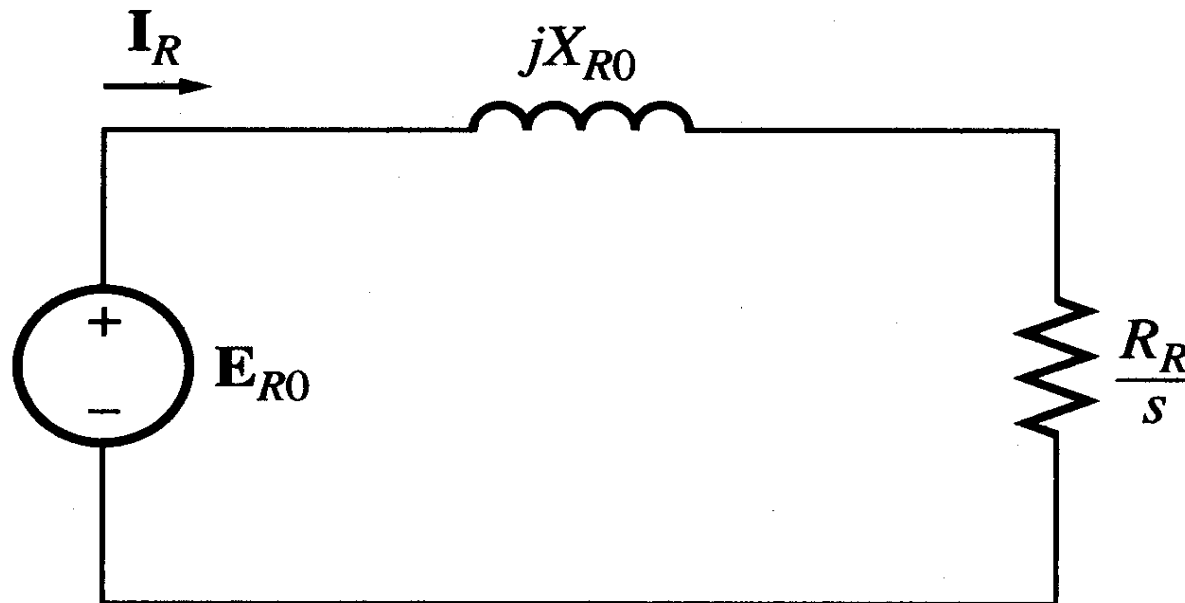
# Equivalent Circuit

- Now we can have the rotor equivalent circuit



# Equivalent Circuit

- Now as we managed to solve the induced voltage and different frequency problems, we can combine the stator and rotor circuits in one equivalent circuit

Where


$$X_2 = a_{eff}^2 X_{R0}$$

$$R_2 = a_{eff}^2 R_R$$

$$I_2 = \frac{I_R}{a_{eff}}$$


$$E_1 = a_{eff} E_{R0}$$

$$a_{eff} = \frac{N_S}{N_R}$$

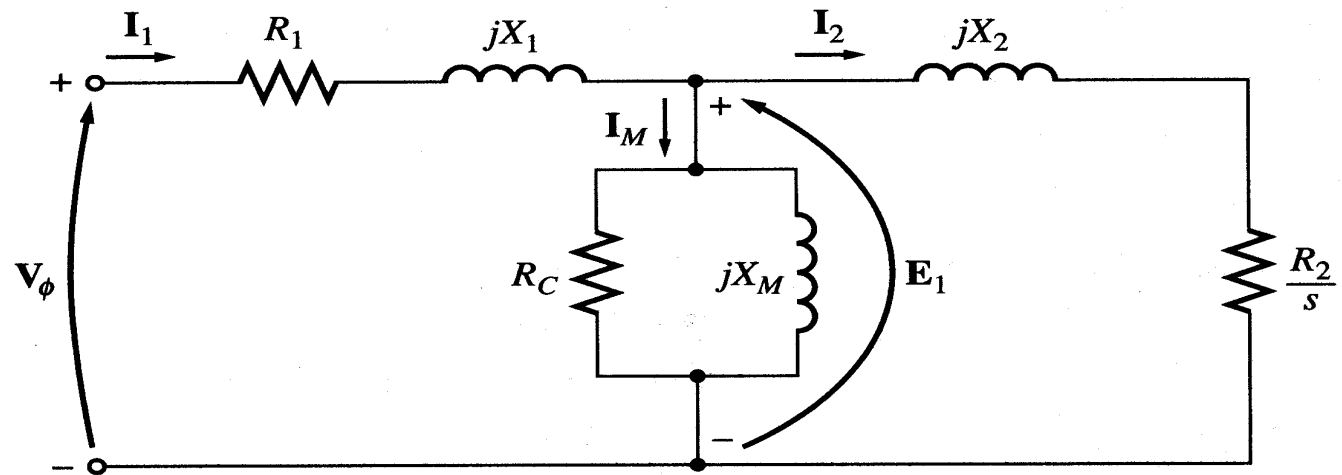

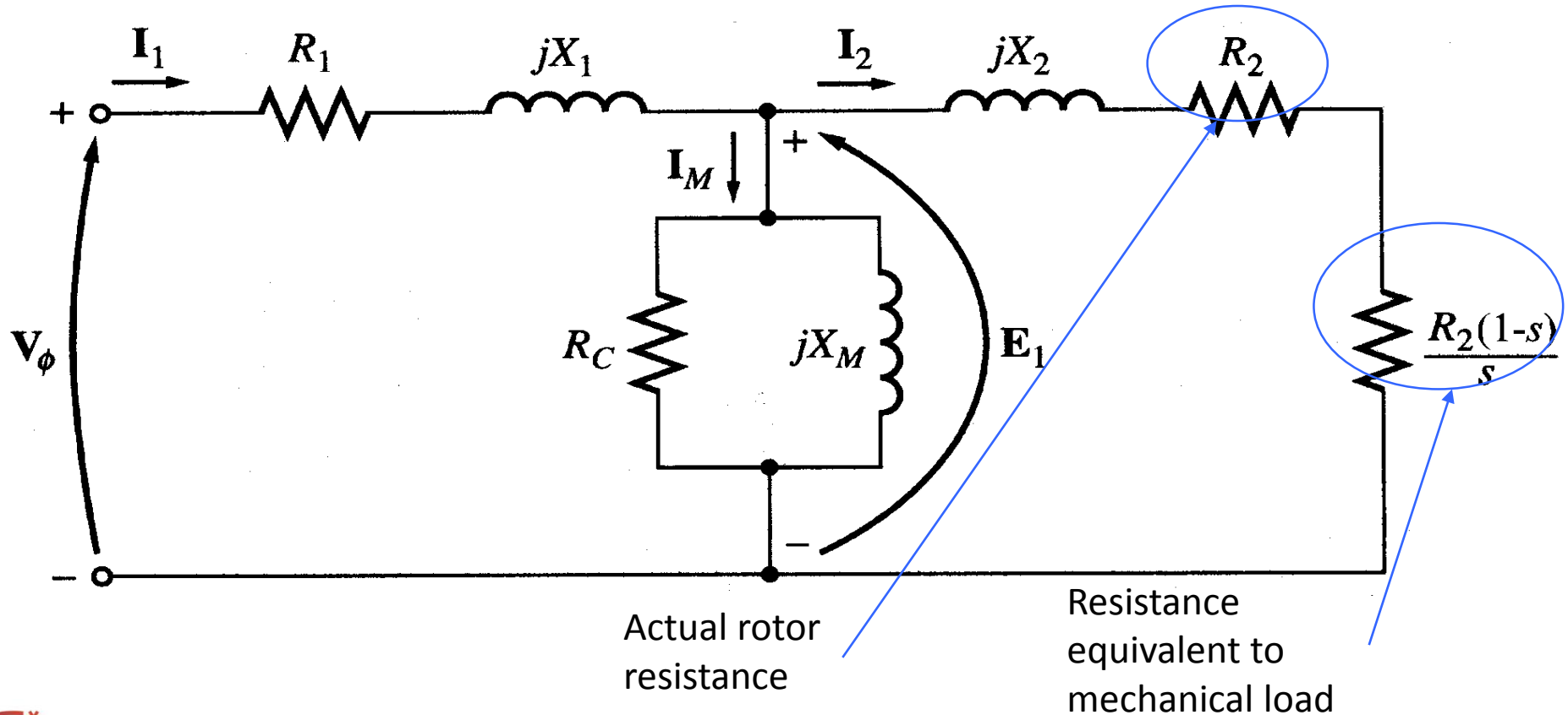
# Equivalent Circuit

- We can rearrange the equivalent circuit as follows



# Torque-speed characteristics

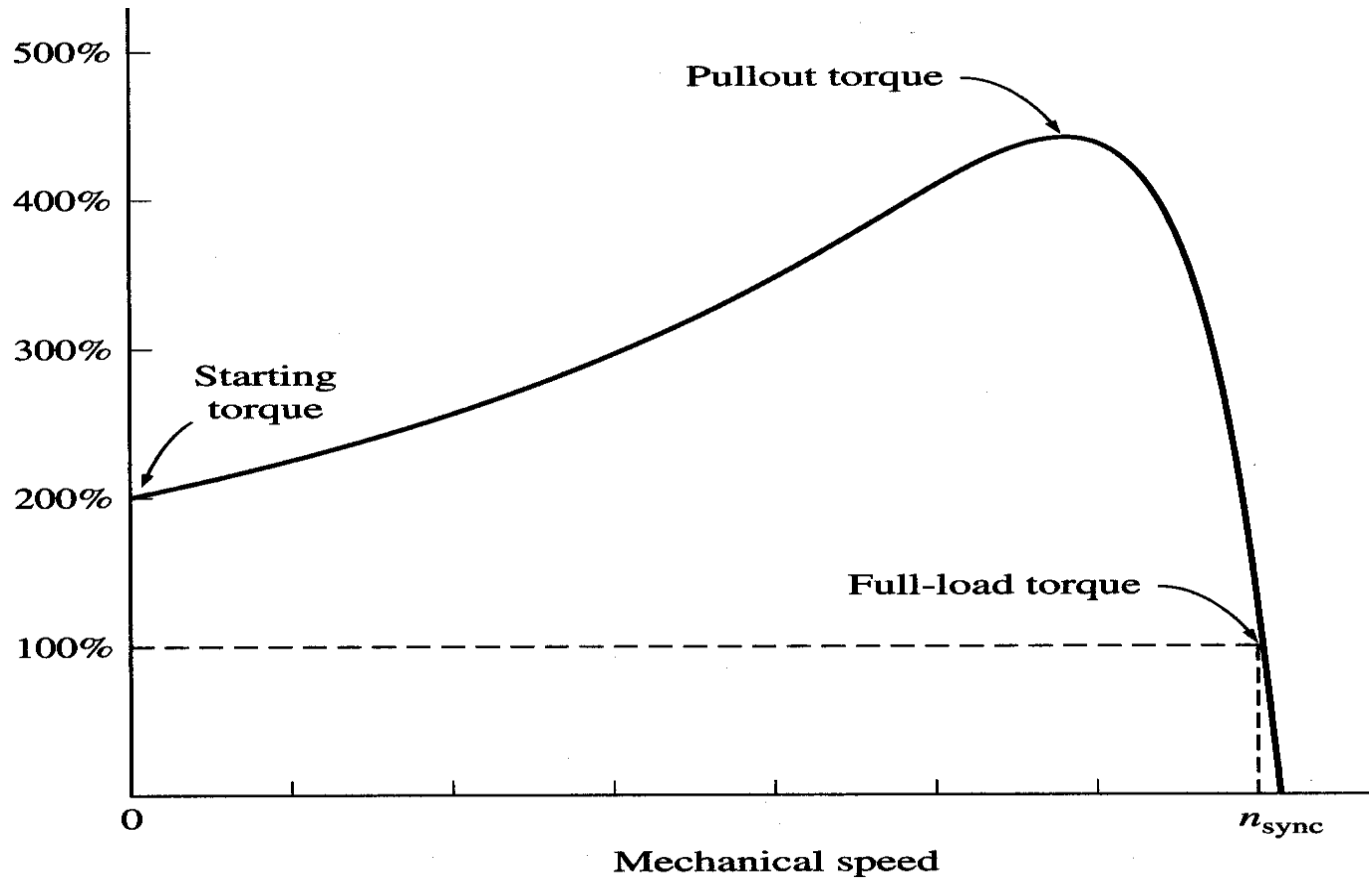

Typical torque-speed characteristics of induction motor



# Torque-speed characteristics

1. Induced torque is **zero** at **synchronous speed**. Discussed earlier.
2. Curve is **nearly linear** between **no-load** and **full load**. In this range, the rotor current, torque increase linearly with the slip.
3. Maximum possible torque is called as ***pullout torque*** and is **2 to 3 times the rated full-load torque**.



# Torque-speed characteristics

4. **Starting torque** of the motor is slightly higher than its full-load torque, so the motor will start carrying any load it can supply at full load.
5. The **torque** of the motor for a given slip varies as the **square of the applied voltage**.
6. If the rotor is **driven faster than synchronous speed** it will **run as a generator**, converting mechanical power to electric power.



# Torque-Equation

- Torque, can be derived from power equation in term of mechanical power or electrical power.

$$\text{Power, } P = \omega T, \text{ where } \omega = \frac{2\pi n}{60} (\text{rad} / \text{s})$$

$$\text{Hence, } T = \frac{60P}{2\pi n}$$

*Thus,*

$$\text{Mechanical Torque, } T_m = \frac{60P_m}{2\pi n_r}$$

$$\text{Output Torque, } T_o = \frac{60P_o}{2\pi n_r}$$



# Torque-Equation

- Note that, Mechanical torque can be written in terms of circuit parameters. This is determined by using **approximation method**

$$P_m = 3I_R'^2 \frac{R_R'}{s} (1-s) \text{ and } P_m = \omega_r T_m$$

$$\therefore T_m = \frac{P_m}{\omega_r} = \left[ \frac{3I_R'^2 \frac{R_R'}{s} (1-s)}{\omega_r} \right]$$


...

...

...

$$\therefore T_m = \left[ \frac{3(V_{RM\phi})^2}{2\pi n_s} \right] \left[ \frac{sR_R'}{(R_R')^2 + (sX_R')^2} \right]$$

Hence, Plot  $T_m$  vs  $s$

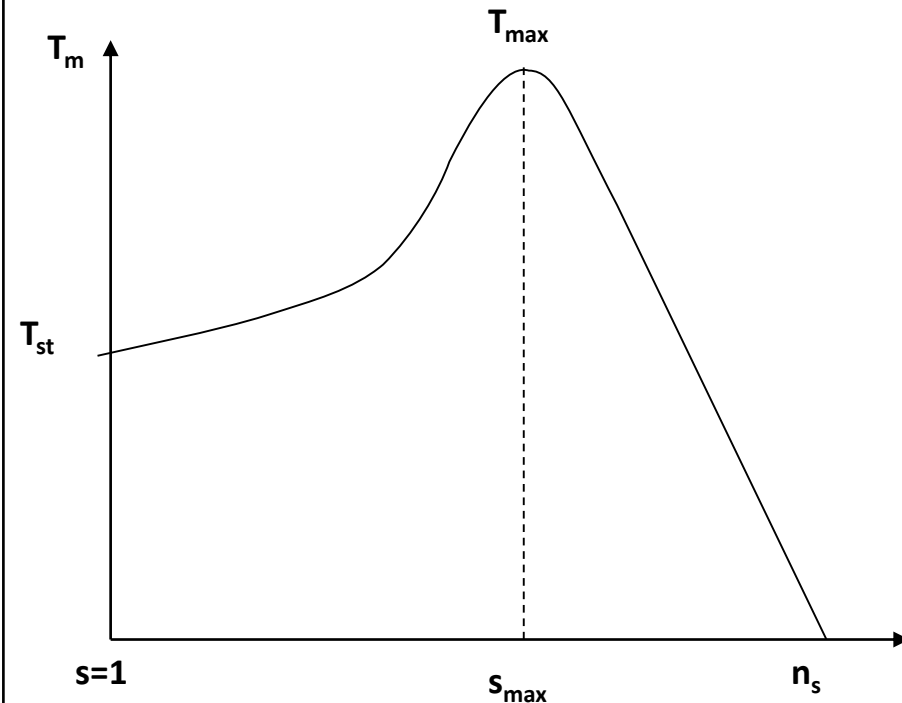

$s_{max}$  is the slip for  $T_{max}$  to occur





# Torque-Equation

*Starting Torque,  $s = 1$*


$$\therefore T_{st} = \left[ \frac{3(V_{s\phi})^2}{2\pi \left( \frac{n_s}{60} \right)} \right] \left[ \frac{R_R'}{(R_s + R_R')^2 + (X_s + X_R')^2} \right]$$

$$s_{\max} = \pm \left[ \frac{R_R'}{\sqrt{(R_s)^2 + (X_R')^2}} \right]$$

$$T_{\max} = \left[ \frac{3(V_{s\phi})^2}{2 \left[ 2\pi \left( \frac{n_s}{60} \right) \right]} \right] \left[ \frac{1}{R_s + \sqrt{(R_s)^2 + (X_s + X_R')^2}} \right]$$



# Power Flow of Induction Motor

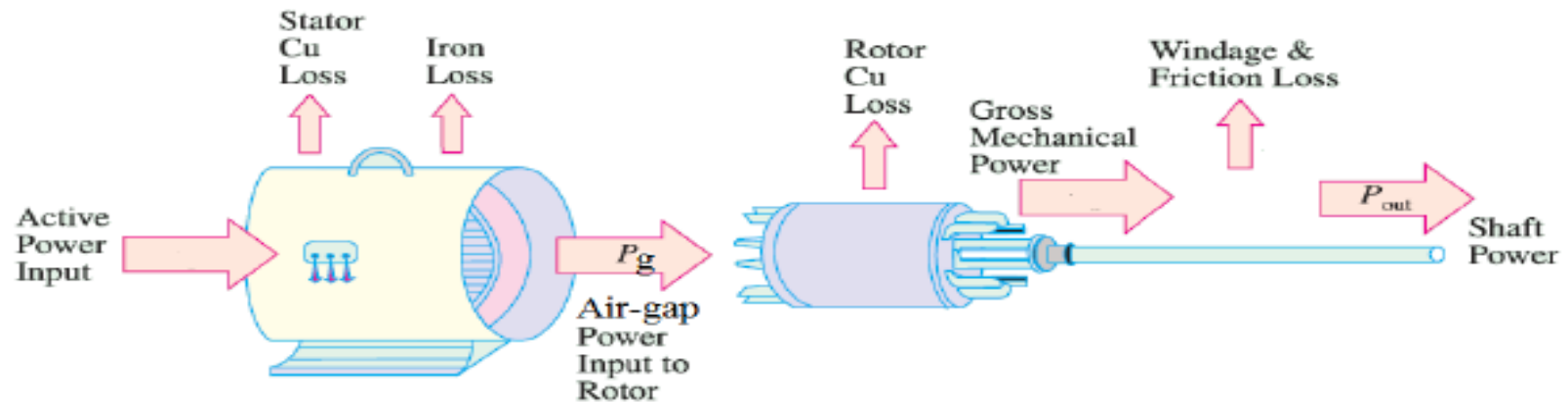

# Summary

- Equivalent Circuit of three phase Induction Motor is developed.
- Behavior of Torque-speed characteristics are analyzed.
- Power Flow of Induction Motor

