

Circuit Analysis Techniques



Lecture 5

Tutorial

Lecture delivered by:



Objectives

At the end of this lecture, student will be able to:


- Solve problems on KCL, KVL, Mesh and Nodal analysis
- Compute equivalent resistance in electrical circuits



Problems


Problem 8

For the network shown in Fig, find V_s which makes $I_0 = 7.5$ mA.

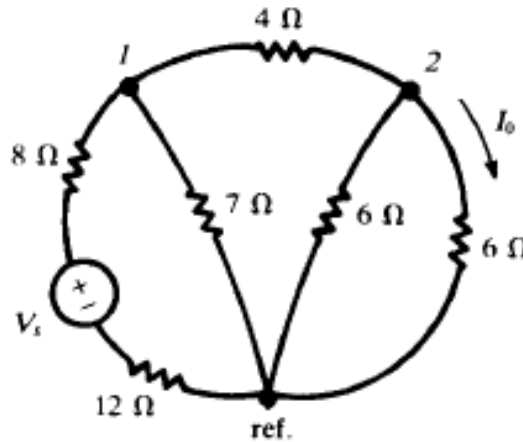

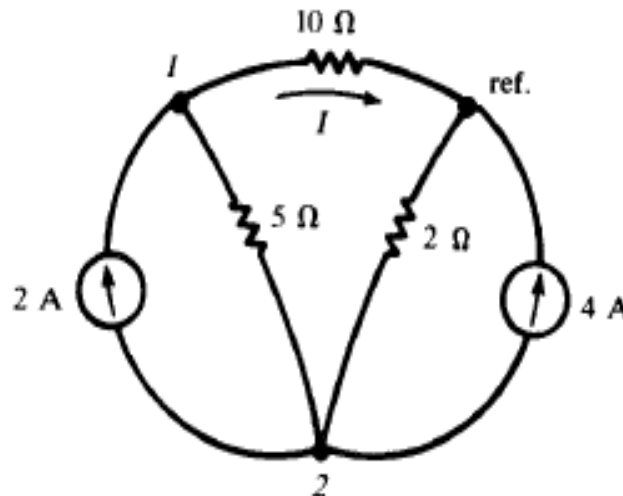Problem 9


In the network shown, find the current in the $10\ \Omega$ resistor.



Problems


Problem 10

Find the voltage V_{ab} in the network shown in Fig.

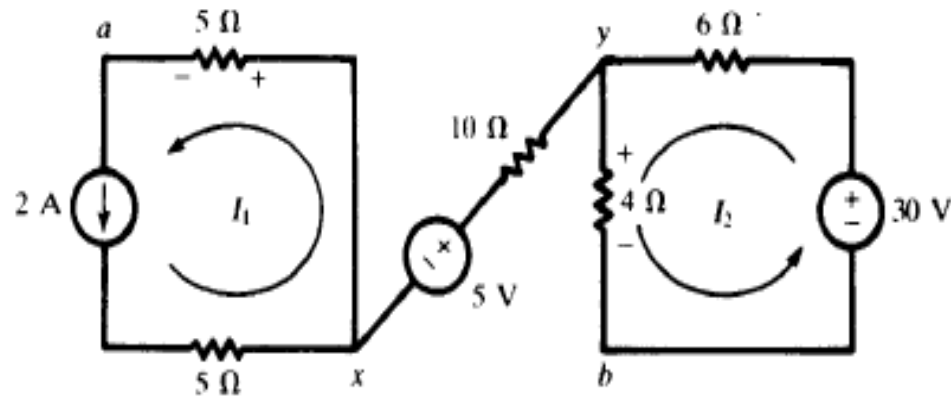

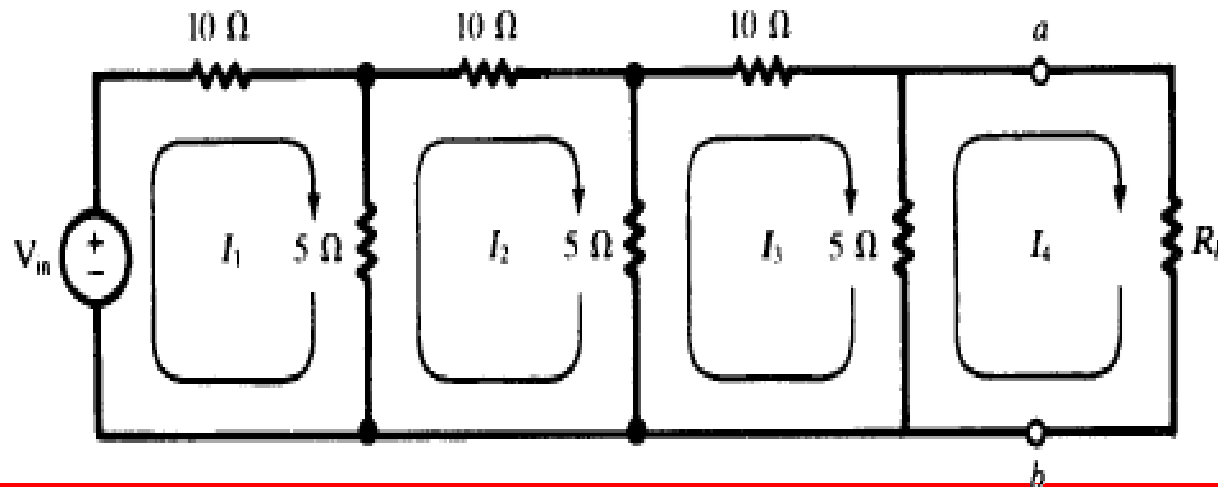Problem 11


In the ladder network of Fig, obtain the transfer resistance as expressed by the ratio of V_{in} to I_4 .



Problems


Problem 12

Find the maximum power that can be delivered to the resistor of circuit shown in figure

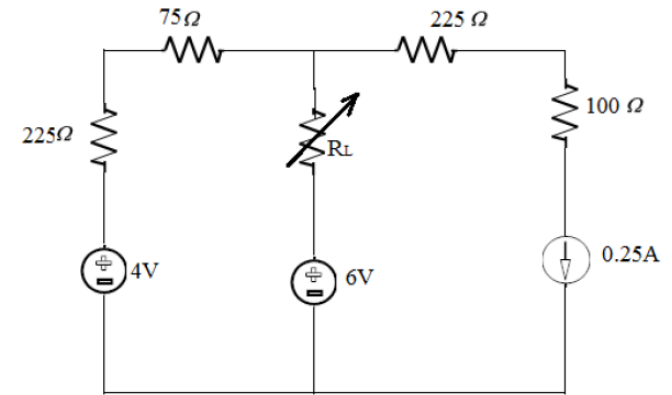

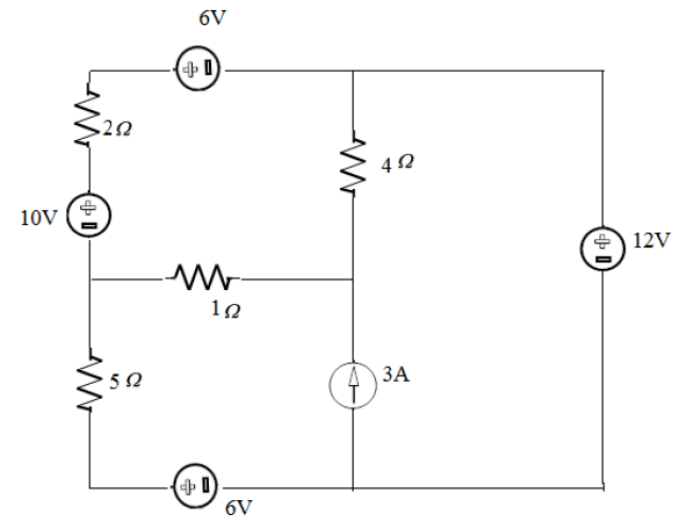Problem 13


Find the power supplied by the $3A$ current source to the circuit shown in figure. Use either mesh analysis or nodal analysis



Problems


Problem 14

Find $I_L(0)$ and $V_C(0)$ for the circuit shown in figure

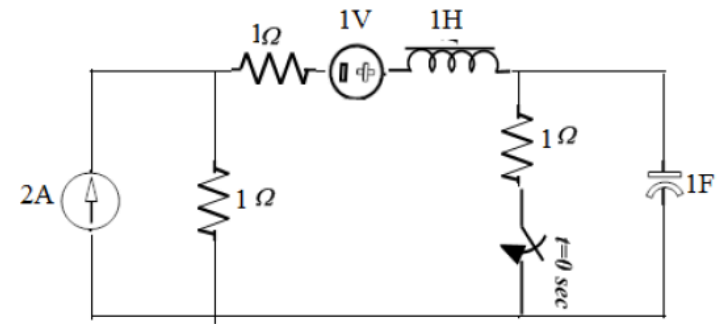

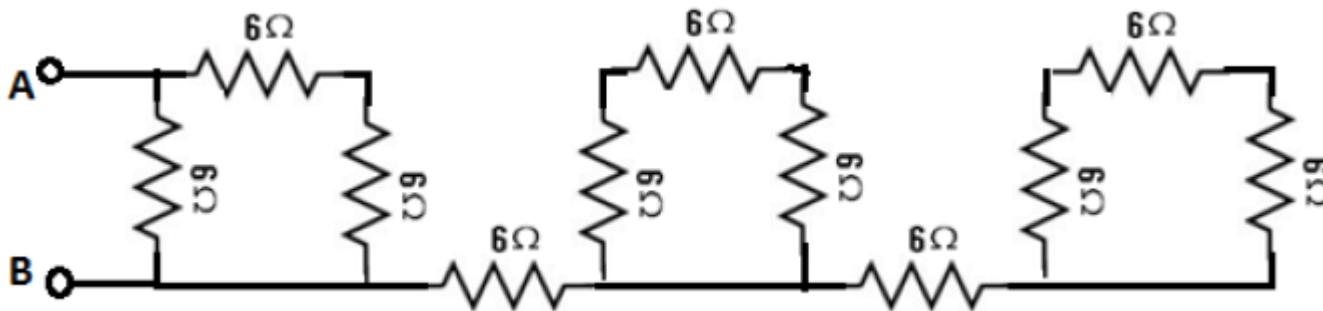Problem 15

Find the equivalent Resistance across A and B



Summary

- Problems are solved on KCL
- Problems are solved on KVL
- Problems are solved on mesh and node analysis
- Arrive at equivalent resistance

