

# Lecture-36

## OC and SC Test

Lecture delivered by:



# Topics

- Determination of Parameters of Circuit Model of Transformer (O.C and S.C Test)
- Voltage Regulation
- Transformer Efficiency



# Objectives

At the end of this lecture, student will be able to:

- Explain the need of Open Circuit (OC) and Short Circuit (SC) tests
- Conduct Open Circuit (OC) and Short Circuit (SC) tests
- Compute parameters of equivalent circuit and voltage regulation from the tests results



# Tests conducted on a transformer

- Open Circuit test
- Short Circuit test
- Sumpner's or Back-to-Back test
- Polarity test

In this lecture we will discuss the OC and SC tests only.




# Open circuit and Short circuit tests

Purpose of conducting these tests are:

- i. To determine the parameters of the equivalent circuit
- ii. To pre-determine the voltage regulation and efficiency at any given load.



# Open-circuit Test

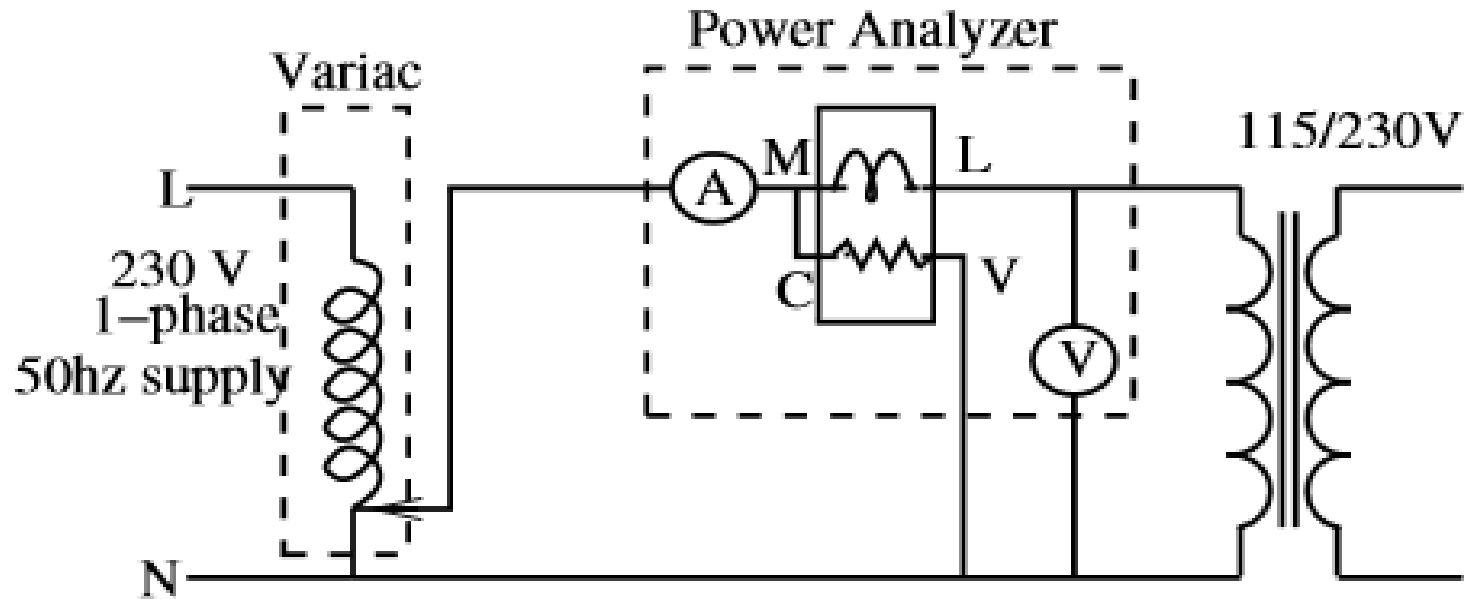

- O.C Test is usually conducted on L.V side
- O.C Test is used to find
  - (i) No load loss or core loss
  - (ii) No load current  $I_o$  which is helpful in finding  $G_o$ (or  $R_o$ ) and  $B_o$  (or  $X_o$ )



# Open-circuit Test Cont...

$$\begin{aligned}\text{Core loss} &= W_{oc} \\ &= V_0 I_0 \cos \phi_0\end{aligned}$$

$$\cos \phi_0 = \frac{W_{oc}}{V_0 I_0}$$

$$I_c \text{ or } I_w = I_0 \cos \phi_0$$

$$I_m \text{ or } I_\mu = I_0 \sin \phi_0 = \sqrt{I_0^2 - I_w^2}$$

$$I_0 = V_0 Y_0; \quad \therefore Y_0 = \frac{I_0}{V_0}$$

$$W_{oc} = V_0^2 G_0;$$

$$\therefore \text{conductance} \quad G_0 = \frac{W_{oc}}{V_0^2}$$

$$\& \text{ susceptance} \quad B_0 = \sqrt{Y_0^2 - G_0^2}$$

$$R_o = \frac{V_o}{I_w}$$


$$X_o = \frac{V_o}{I_\mu}$$

$$G_o = \frac{I_w}{V_o}$$

$$B_o = \frac{I_\mu}{V_o}$$



# Short-circuit Test

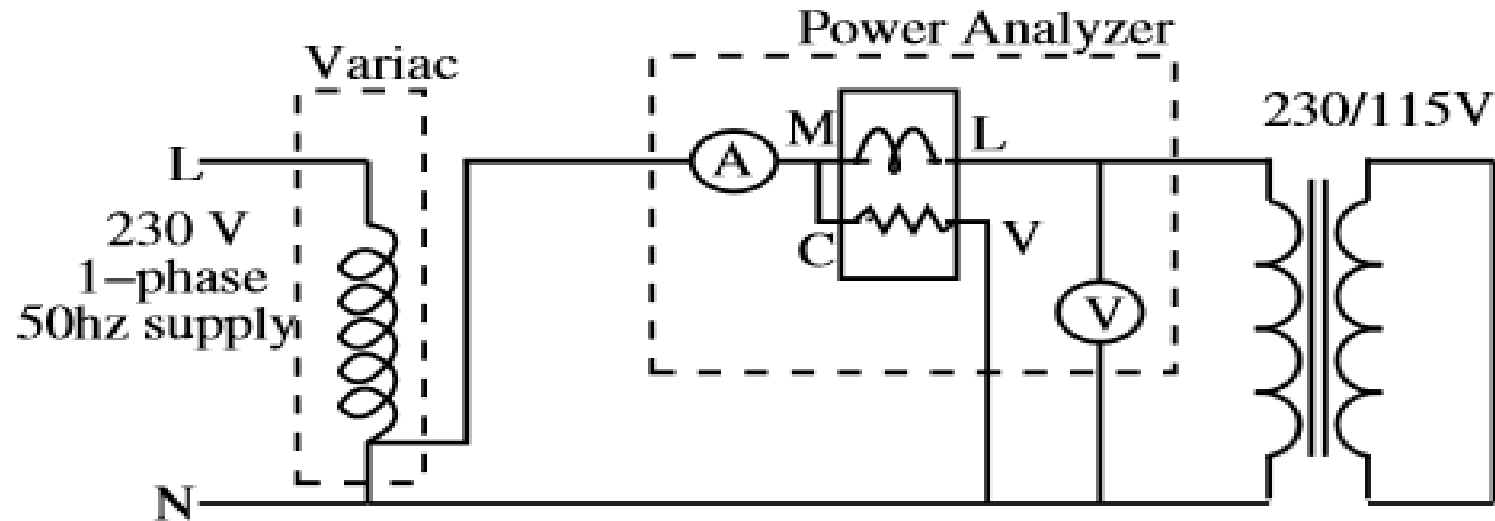


- S.C Test is usually conducted on H.V side
- S.C Test is used to find
  - (i) Full load copper loss – to pre determine the efficiency
  - (ii)  $Z_{01}$  or  $Z_{02}$ ;  $X_{01}$  or  $X_{02}$ ;  $R_{01}$  or  $R_{02}$  - to predetermine the voltage regulation





# Short-circuit Test Cont..

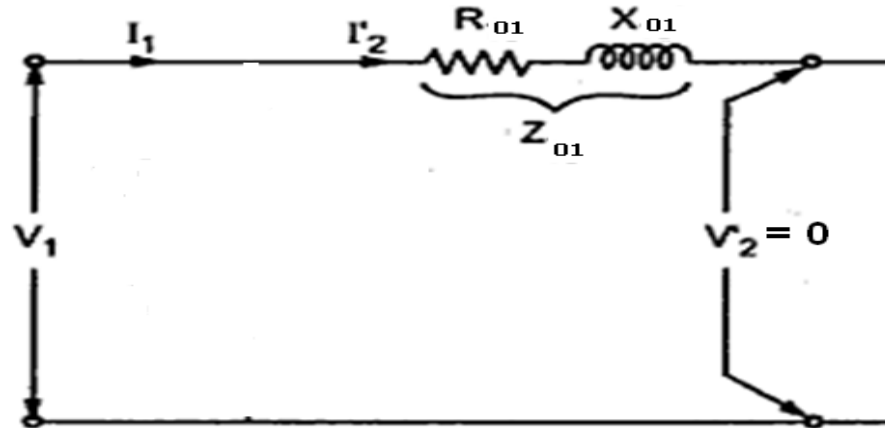

$$\text{Full load cu loss} = W_{sc} = I_{sc}^2 R_{01}$$

$$R_{01} = \frac{W_{sc}}{I_{sc}^2}$$

$$Z_{01} = \frac{V_{sc}}{I_{sc}}$$

$$\therefore X_{01} = \sqrt{Z_{01}^2 - R_{01}^2}$$



# Voltage Regulation of a Transformer


- **Voltage regulation** of a transformer is defined as the change in secondary terminal voltage from no- load to full-load expressed as a secondary rated voltage with primary applied voltage held constant.

$$\text{Voltage regulation} = \frac{\text{no - load voltage} - \text{full - load voltage}}{\text{no - load voltage}}$$


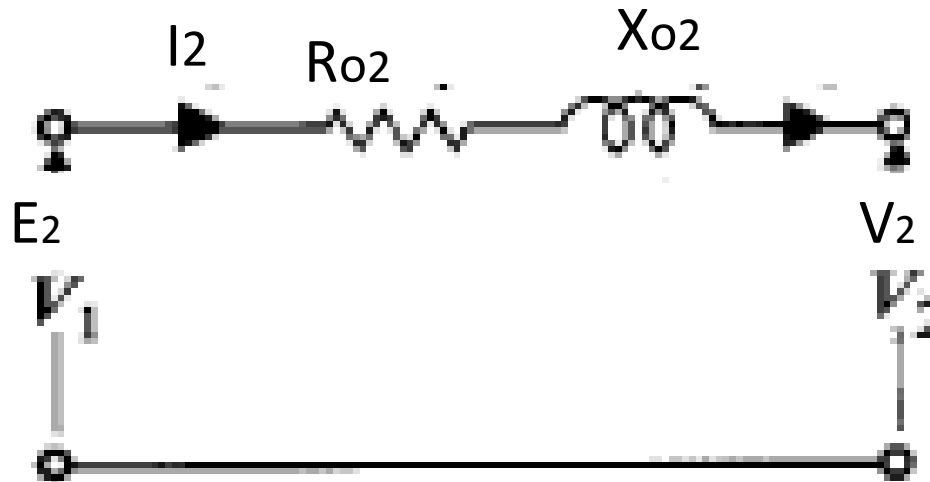
# Voltage Regulation of a Transformer Cont..


- The voltage regulation of a transformer can be obtained from its approximate equivalent circuit referred to primary or secondary windings.



Approximate equivalent circuit referred to secondary


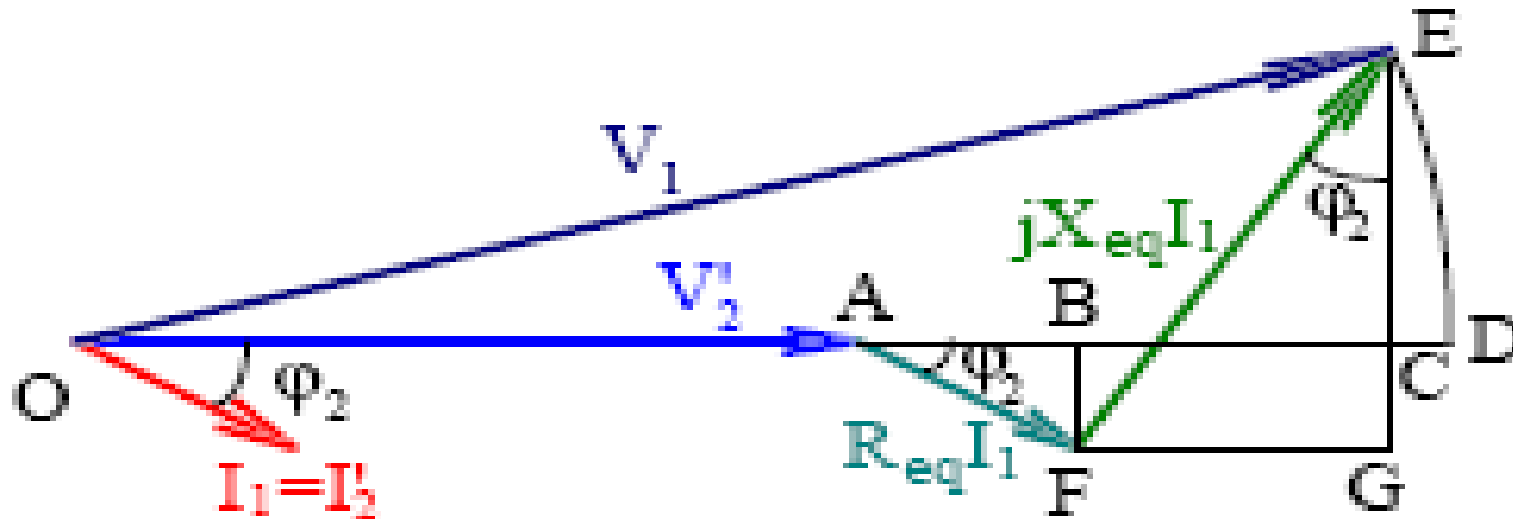
# Voltage Regulation of a Transformer Cont..



Phasor Diagram

$$\begin{aligned}
 E_2 &= OC = OA + AB + BC \text{ (or FG)} \\
 &= OA + AF \cos \phi_2 + EG \sin \phi_2 \\
 &= V_2 + I_2 R_{o2} \cos \phi_2 + I_2 X_{o2} \sin \phi_2
 \end{aligned}$$



# Voltage Regulation of a Transformer Cont..

- Voltage drop in the secondary terminal voltage

$$E_2 - V_2 = I_2 R_{o2} \cos\phi_2 + I_2 X_{o2} \sin\phi_2$$

- Voltage drop in the secondary terminal voltage for any load power factor.

$$E_2 - V_2 = I_2 R_{o2} \cos\phi_2 \pm I_2 X_{o2} \sin\phi_2$$

Where +ve sign for lagging power factor load

-ve sign for leading power factor load

- Similarly the voltage drop as referred to primary is

$$E_1 - V_1 = I_1 R_{o1} \cos\phi_2 \pm I_1 X_{o1} \sin\phi_2$$



# Voltage Regulation Based on Phasor's

In terms of secondary values

$$\% \text{ regulation} = \frac{{}_0V_2 - V_2}{{}_0V_2} = \frac{I_2 R_{02} \cos \phi_2 \pm I_2 X_{02} \sin \phi_2}{{}_0V_2}$$

where '+' for lagging and '-' for leading

In terms of primary values

$$\% \text{ regulation} = \frac{V_1 - V_2'}{V_1} = \frac{I_1 R_{01} \cos \phi_1 \pm I_1 X_{01} \sin \phi_1}{V_1}$$

where '+' for lagging and '-' for leading



# Transformer Efficiency

Transformer efficiency is defined as (applies to motors, generators and transformers):

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\%$$

Types of losses incurred in a transformer:

- Copper  $I^2R$  losses

- Hysteresis losses

- Eddy current losses

Therefore, for a transformer, efficiency may be calculated using the following:

$$\eta = \frac{V_S I_S \cos \theta}{P_{Cu} + P_{core} + V_S I_S \cos \theta} \times 100\%$$



# Summary

- Open-circuit and short-circuit tests are used to determine equivalent circuit parameters. By conducting these tests efficiency and voltage regulation can be predetermined at any load.

