

Circuit Analysis Techniques



Lecture 12

Phasor Relationship for R, L and C Elements

Lecture delivered by:



Topics

- Phasor Relationship for R, L and C Elements
- Resistor Phasor
- Inductor Phasor
- Capacitor Phasor
- Phasor voltage-current relations
- Angular Frequency (ω)



Objectives

At the end of this lecture, student will be able to:


- Analyze phasor Relationship for R, L, and C Elements
- Define phasor voltage-current relations
- Define angular Frequency (ω)



Phasor Relationship for R, L and C Elements

Resistor phasor


Time domain

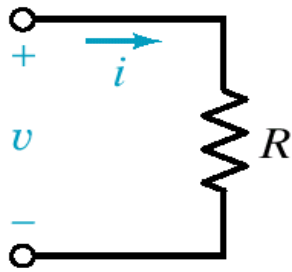

(a)


$$v = Ri$$

Frequency domain

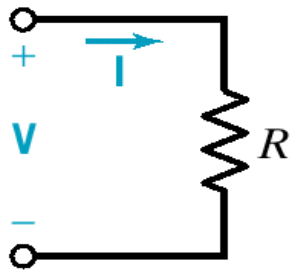


(b)
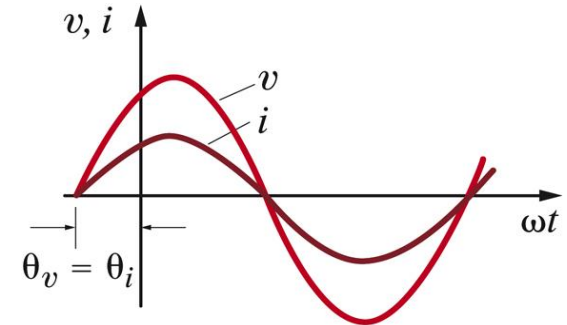
$$\mathbf{V} = R\mathbf{I} \quad \text{or} \quad \mathbf{I} = \frac{\mathbf{V}}{R}$$




Voltage and current are **in phase**


Inductor Phasor

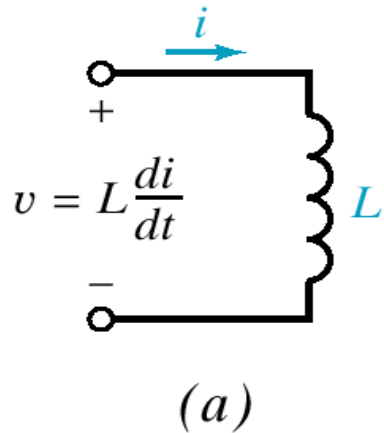

Time domain

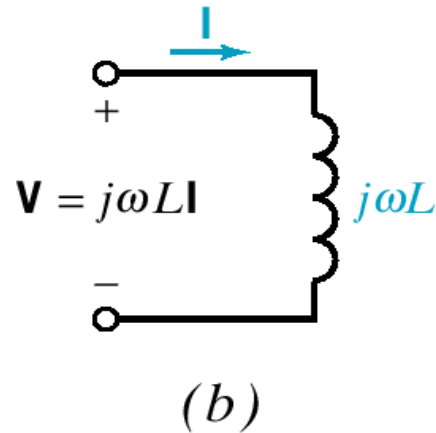

Frequency domain

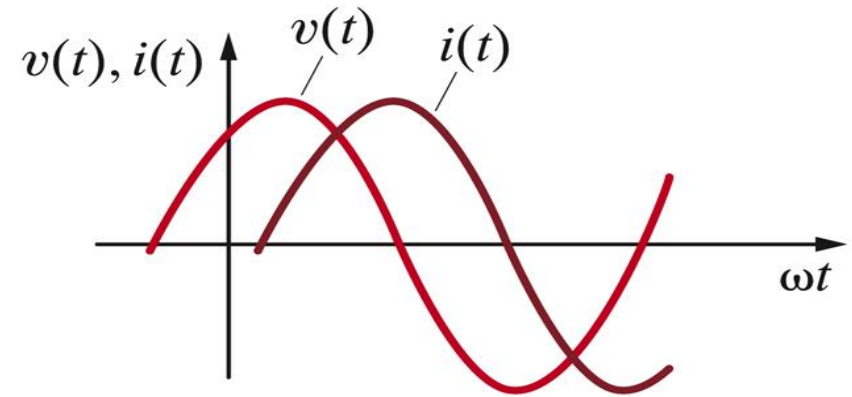


$$v = L \frac{di}{dt}$$

$$\mathbf{V} = j\omega L \mathbf{I} \quad \text{or} \quad \mathbf{I} = \frac{\mathbf{V}}{j\omega L}$$


Voltage **leads** current by **90°**

Capacitor Phasor

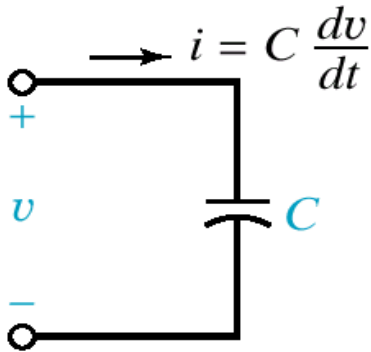


(a)

Time domain

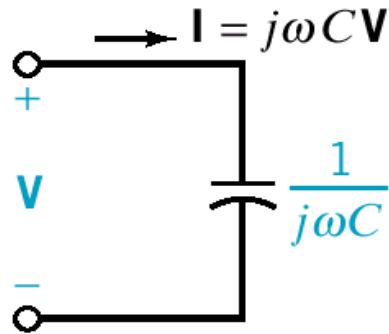

(b)

Frequency domain


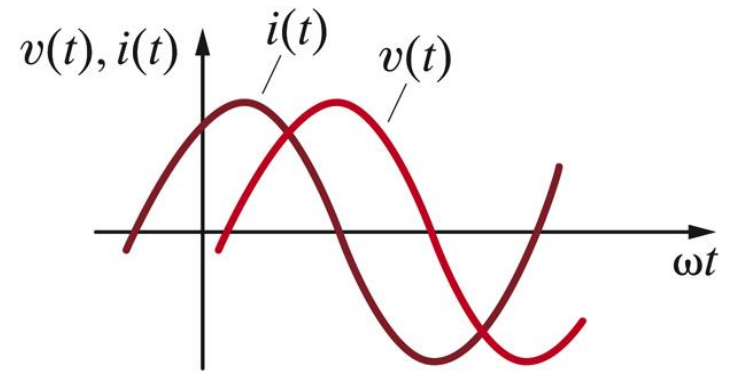


$$i = C \frac{dv}{dt}$$



$$\mathbf{I} = j\omega C \mathbf{V} \quad \text{or} \quad \mathbf{V} = \frac{\mathbf{I}}{j\omega C}$$

Voltage **lags** current by **90°**

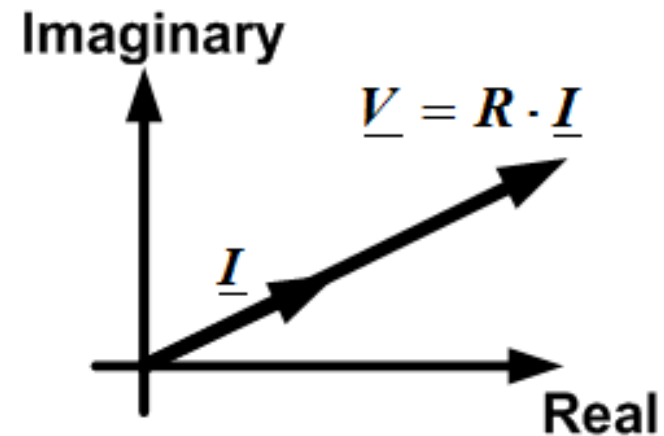
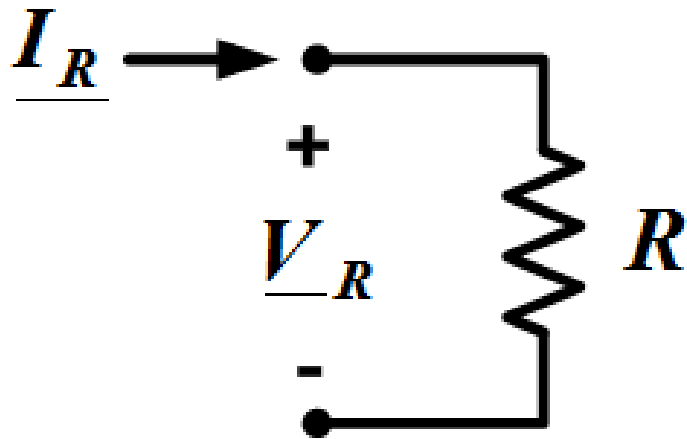
Phasor Voltage-Current Relations of Resistor



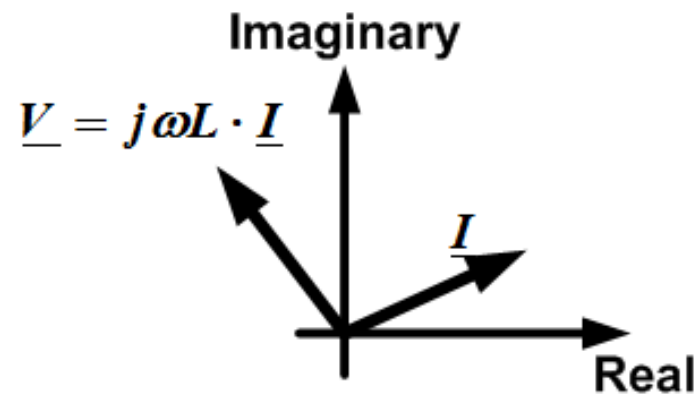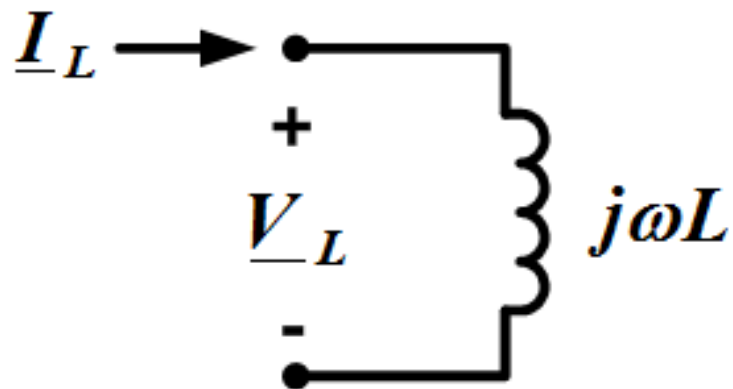Phasor Voltage-current Relations Of Inductor



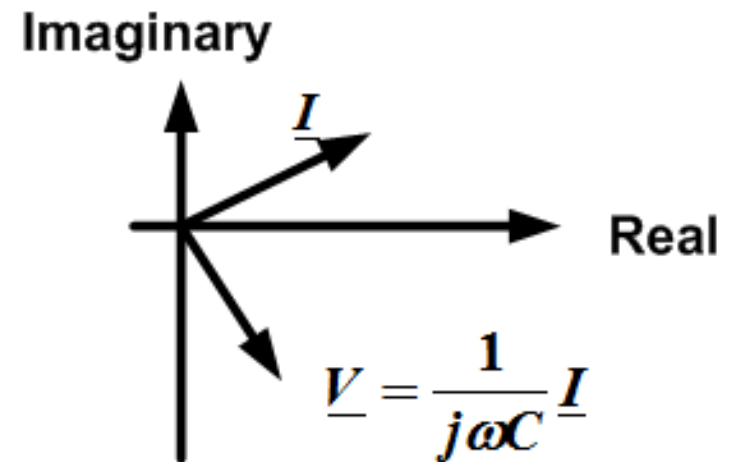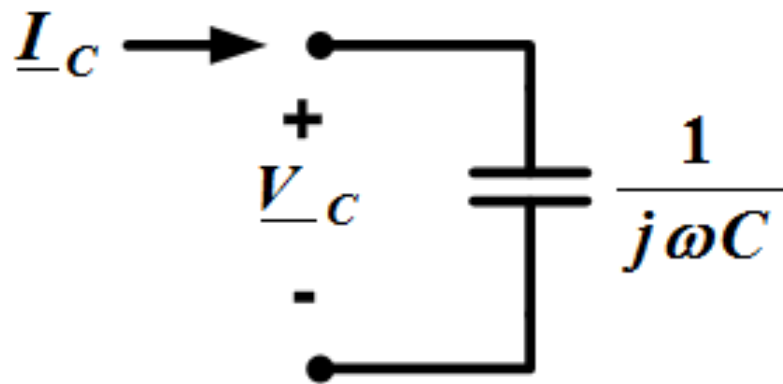Phasor voltage-current relations of capacitor





Circuit Element Phasor Relations

Element	V/I Relation	Phasor Relation	Phase
Capacitor	$I = C \, dV/dt$	$I = j \, \omega \, C \, V$ $= \omega C V \angle 90^\circ$	I leads V by 90°
Inductor	$V = L \, dI/dt$	$V = j \, \omega \, L \, I$ $= \omega L I \angle 90^\circ$	V leads I by 90°
Resistor	$V = I R$	$V = R I$ $= R I \angle 0^\circ$	In-phase



Series RLC Resonance

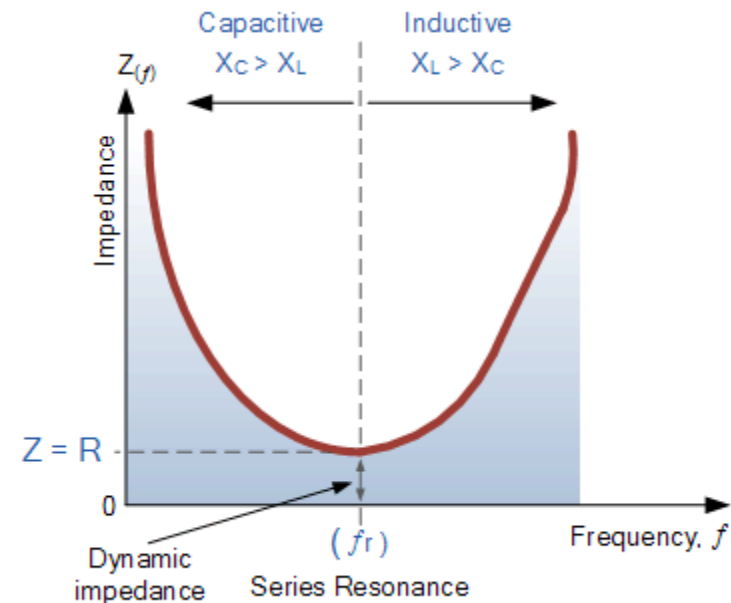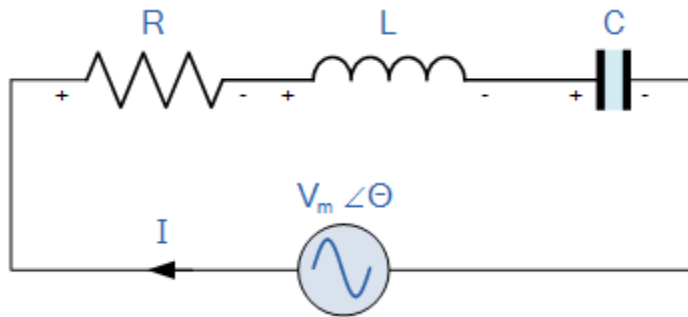- Series RLC circuit there becomes a frequency point where the inductive reactance of the inductor becomes equal in value to the capacitive reactance of the capacitor
- In other words, $X_L = X_C$ The point at which this occurs is called the **Resonant Frequency** point, (f_r) of the circuit



Series RLC Resonance

- Resonant Frequency $F_r = \frac{1}{2\pi\sqrt{LC}}$ Hz
- Lower cut-off Frequency $F_1 = F_r - \frac{R}{4\pi L}$ Hz
- Upper cut-off Frequency $F_2 = F_r + \frac{R}{4\pi L}$ Hz
- Band-width $BW = F_2 - F_1$ Hz
- Quality Factor $Q = \frac{F_r}{F_2 - F_1}$





Parallel RLC Resonance

- In many ways a **parallel resonance** circuit is exactly the same as the series resonance circuit
- Both are 3-element networks that contain two reactive components making them a second-order circuit
- Both are influenced by variations in the supply frequency and have a frequency point where their two reactive components cancel each other



Parallel RLC Resonance

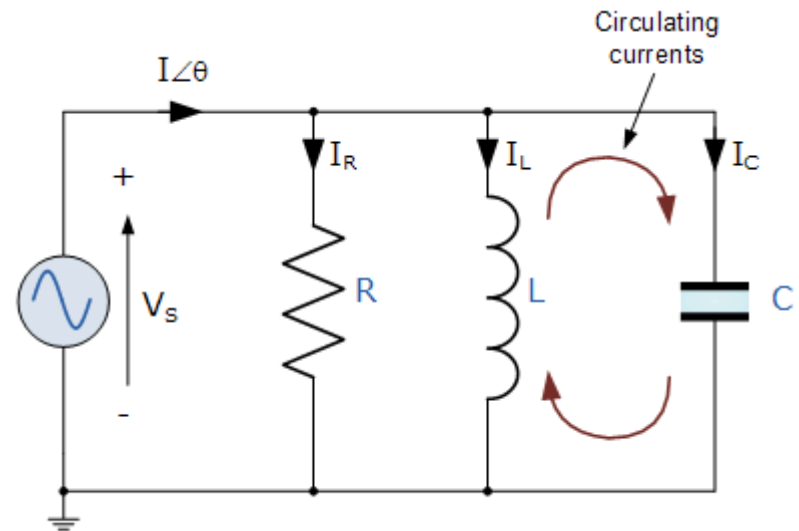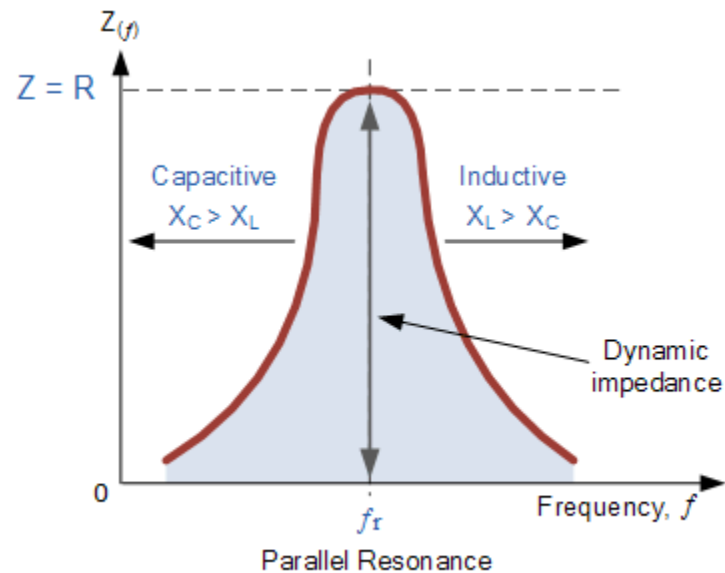- Parallel resonance circuit is influenced by the currents flowing through each parallel branch within the parallel LC tank circuit




Parallel RLC Resonance

- Resonant Frequency $F_r = \frac{1}{2\pi\sqrt{LC}}$ Hz
- Lower cut-off Frequency $F_1 = F_r - \frac{1}{2\pi[(\frac{-1}{2RC}) + \sqrt{(\frac{1}{2RC})^2 + (\frac{1}{LC})}]}$ Hz
- Upper cut-off Frequency $F_2 = F_r + \frac{1}{2\pi[(\frac{1}{2RC}) + \sqrt{(\frac{1}{2RC})^2 + (\frac{1}{LC})}]}$ Hz
- Band-width $BW = F_2 - F_1$ Hz
- Quality Factor $Q = \frac{F_r}{F_2 - F_1}$



Angular Frequency(ω)

- **Angular Frequency** is the number of orbits an object makes around another object in a certain time
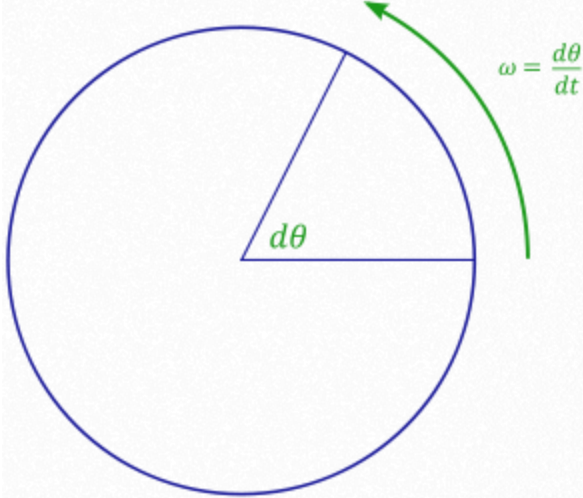
$$\omega = \frac{d\theta}{dt}$$

$$\omega = \frac{2\pi}{T} \quad \omega = 2\pi f$$

- This formula represents angular frequency for an oscillation with period equal T , in this case we deal with one revolution which is equal to 2π radians

Summary

- Phasor Relationship for R, L and C Elements is been discussed
- Phasor voltage-current relations
 - ✓ Voltage and current are in **phase** for **resistive** circuit
 - ✓ Voltage **leads** current by 90° for **inductive** circuit
 - ✓ Voltage **lags** current by 90° for **capacitive** circuit
- Angular Frequency is the number of orbits an object makes around another object is a certain time

