

Lecture-38

Tutorial

Lecture delivered by:



Objectives

At the end of this lecture, student will be able to:

- Solve the problems on the voltage regulation
- Solve the problems on the transformer efficiency



Problem 1:

A 20KVA, 2000/200V, single-phase transformer has the following parameters

HV winding $R_1=3$ ohms $X_1=5.3$ ohms

LV winding $R_2=0.05$ ohms $X_2=0.05$ ohm

Find the voltage regulation at 0.8 power factor lagging and 0.707 Pf leading.



Problem 2:

The Parameters of the equivalent circuit of a 100kVA, 2000/ 200 volts 1-phase transformer are as follows

Primary resistance = 0.2 ohms

Secondary Resistance = 2 milli ohms

Primary leakage reactance = 0.45 ohms

Secondary leakage reactance = 4.5 milli ohms

Core loss resistance = 10 kilo ohms

Magnetizing reactance = 1.55 kilo ohms

Using the circuit referred to primary, determine the

1) Voltage regulation

2) Efficiency of the transformer operating at rated load with 0.8 lagging power factor



Problem 3:

A 25 kVA 2200/220 V, 50 Hz distribution transformer is tested for efficiency and regulation as follows:

O.C. test (l.v side) : 220V, 4 A, 150W

S.C test (h.v. side) : 90 V, 10A, 350W

Determine

- 1) Core loss
- 2) Equivalent resistance referred to primary and secondary
- 3) Equivalent Reactance referred to primary and secondary
- 4) Regulation of transformer at 0.8 power factor lagging current and
- 5) Efficiency at full –load and half load at 0.8 power factor lagging current

