

# Circuit Analysis Techniques



# Lecture 4

## Tutorial

Lecture delivered by:



# Objectives

At the end of this lecture, student will be able to:

- Solve problems on KCL
- Solve problems on KVL,
- Solve problems on Mesh and Nodal analysis



# Problems

## Problem 1

The current and voltage characteristic of a semiconductor diode in the forward direction is measured and recorded in the following table:

$v$ (V)	0.5	0.6	0.65	0.66	0.67	0.68	0.69	0.70	0.71	0.72	0.73	0.74	0.75
$i$ (mA)	$2 \times 10^{-4}$	0.11	0.78	1.2	1.7	2.6	3.9	5.8	8.6	12.9	19.2	28.7	42.7

- In the reverse direction (i.e., when  $v < 0$ ),  $i = 4 \times 10^{-15}$  A.
- Using the values given in the table, calculate the static and dynamic resistances ( $R$  and  $r$ ) of the diode when it operates at 30 mA, and
- Find its power consumption  $p$ .



# Problems


## Problem 2

An inductance of  $3.0\text{mH}$  has a voltage that is described as follows:

- For  $0 < t < 2\text{ ms}$ ,  $V = 15.0\text{V}$  and, for  $2 < t < 4\text{ ms}$ ,  $V = 30.0\text{ V}$ .
- Obtain the corresponding current and sketch  $V_L$  and  $I$  for the given intervals.
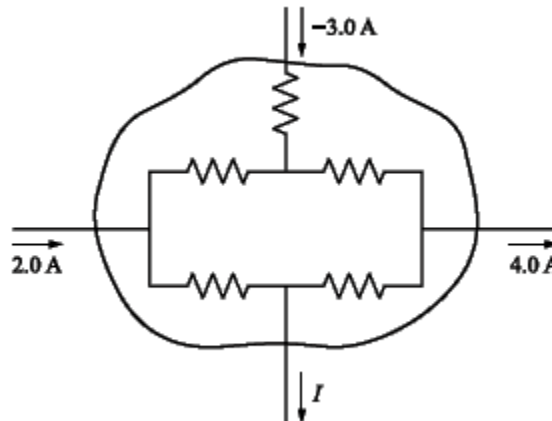
## Problem 3


Find the current  $I$  for the circuit shown in Fig



# Problems


## Problem 4

Find all branch currents in the network

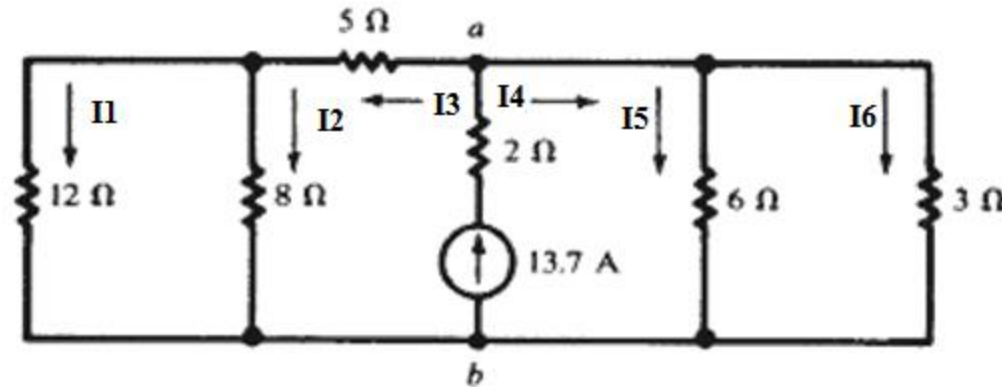

## Problem 5


Solve by the mesh current method

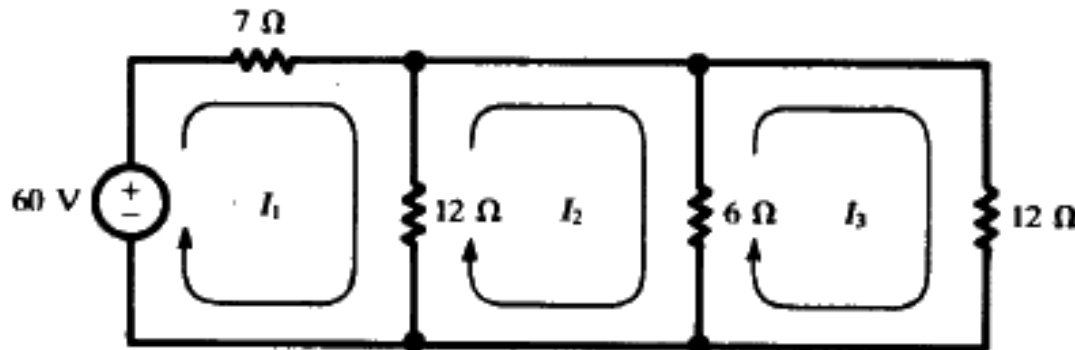

# Problems

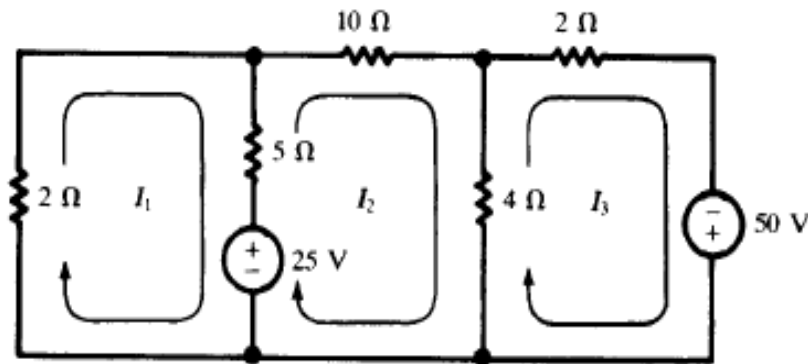
## Problem 6

Write the mesh current matrix equation for the network of Fig by inspection, and solve for Currents.



## Problem 7

Solve Problem by the node voltage method

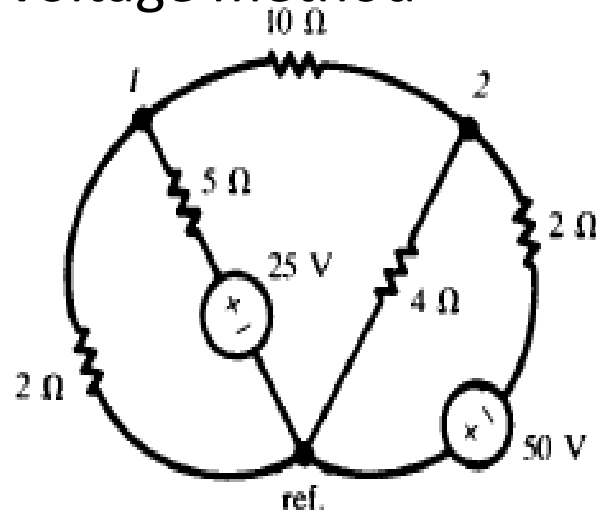

# Summary

- Problems are solved on KCL
- Problems are solved on KVL
- Problems are solved on mesh and node analysis

