

Lecture No. 50

DC Motor (Types & Characteristics)

Lecture delivered by:




Objectives

At the end of this lecture, student will be able to:

- Classify DC Motors based upon methods of excitation
- Derive an expression for torque developed in a DC Motor
- Discuss Speed-Torque characteristics of DC Motors
- Explain methods of Speed Control



Methods of Excitation of DC

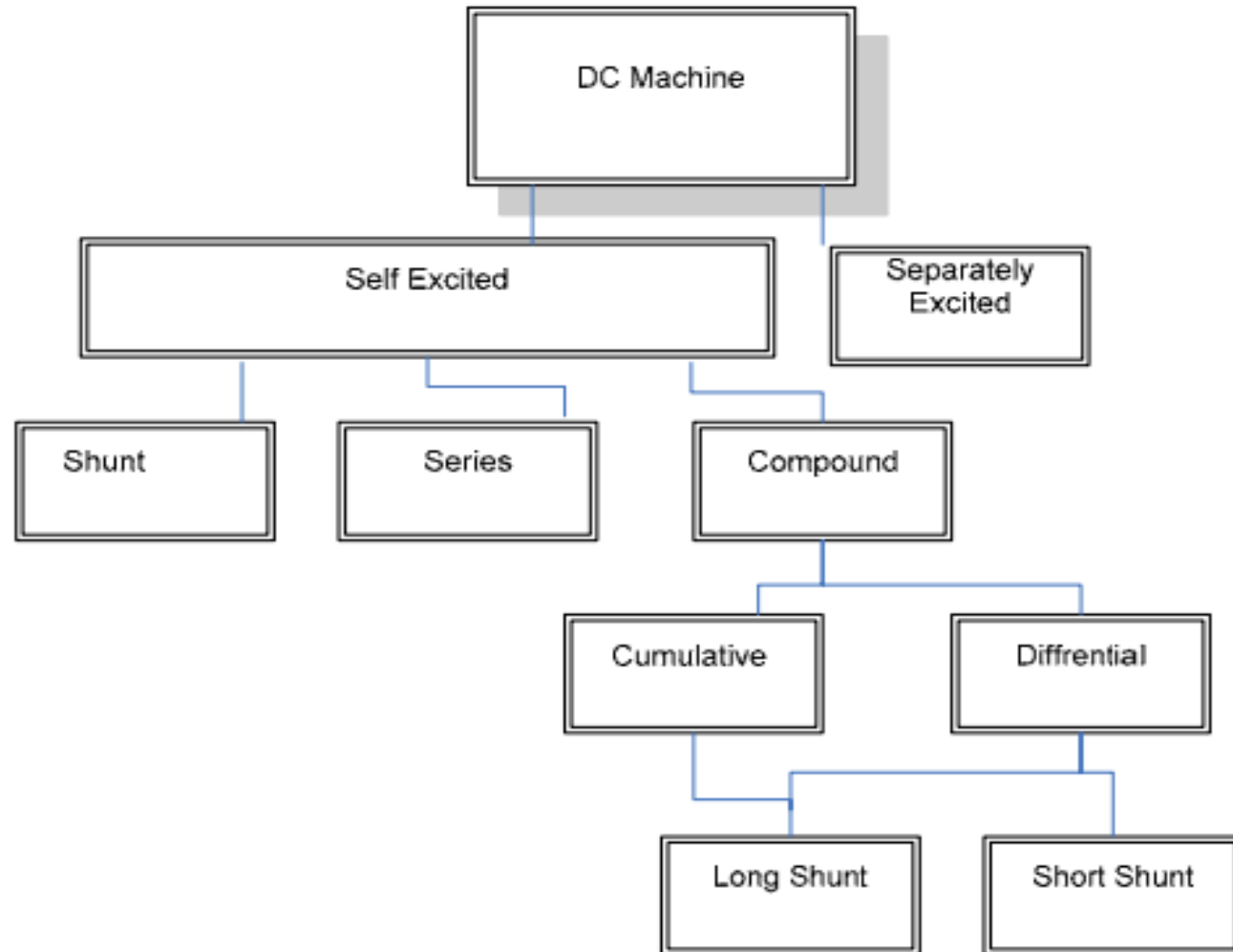


Methods of Excitation of DC Machines

- In DC machine current carrying conductors rotate inside static magnetic field.
- DC machine can be termed as an electro mechanical energy converter which only works in the presence of a field excitation.
- Two types of excitation present for dc machine
 1. Separate excitation
 2. Self excitation



Separate Excitation

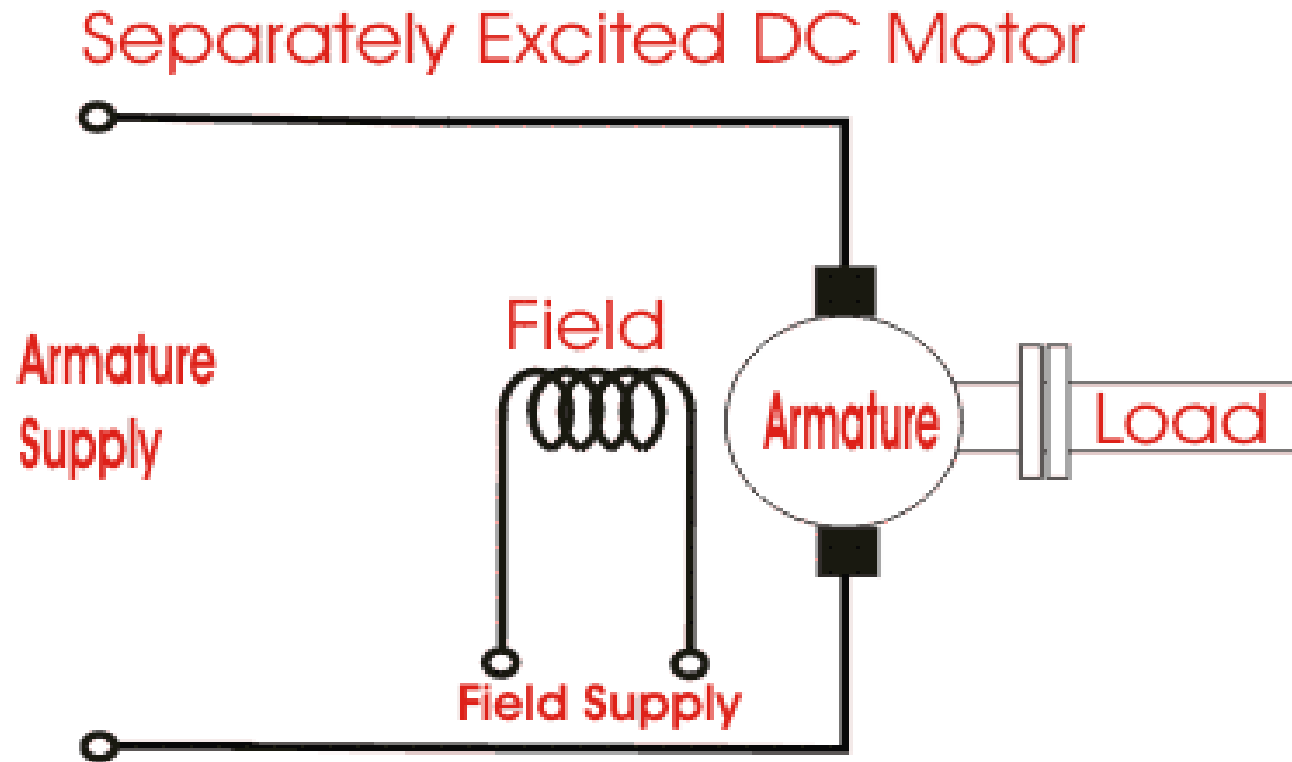
- Field excitation is only possible by dc supply



Self Excitation


A self excited dc machine can be divided into:

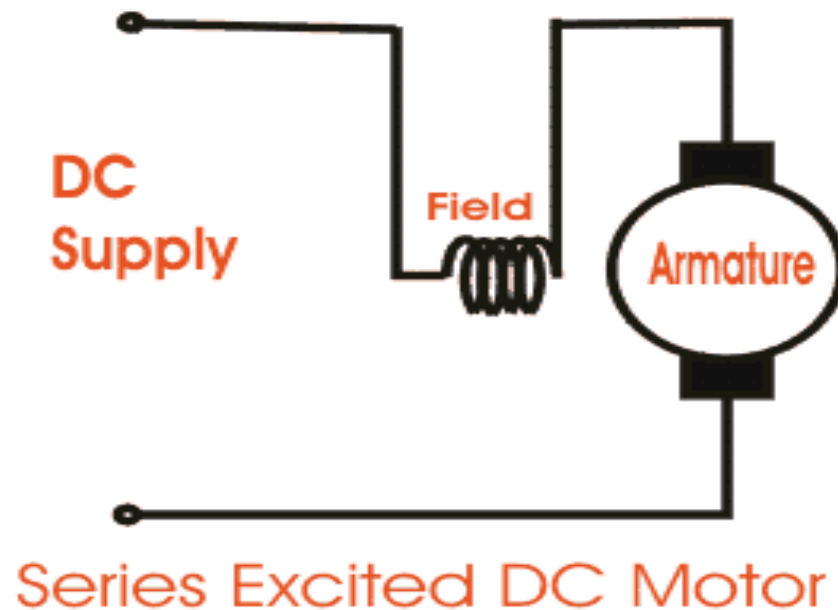- 1. Series excitation** – in this case the field is in series with the rotor and the armature current itself acts as the field current




Self Excitation

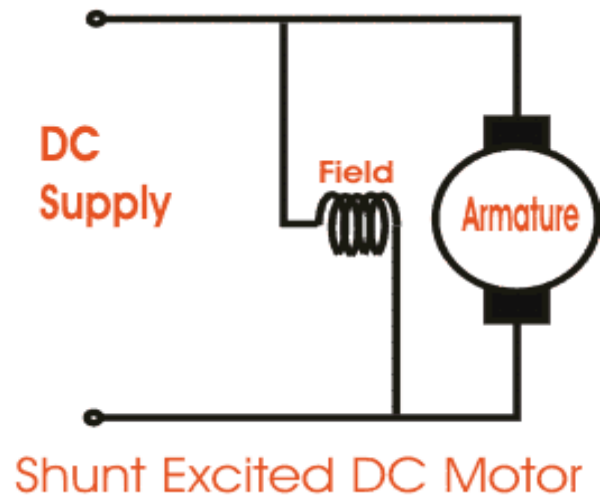2. Shunt excitation- when the field is in the parallel with the armature, then that excitation is called shunt excitation.




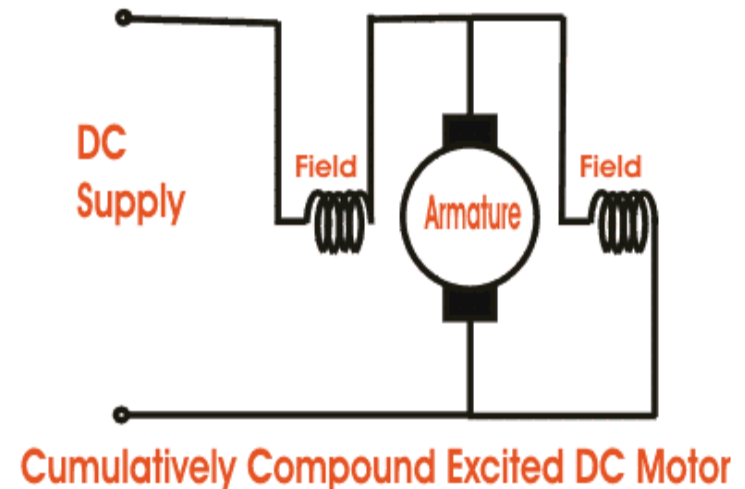3. Compound excitation- both series and shunt excitation winding is present in the circuit then this is called compound excitation.




Self Excitation

Short Shunt DC Motor

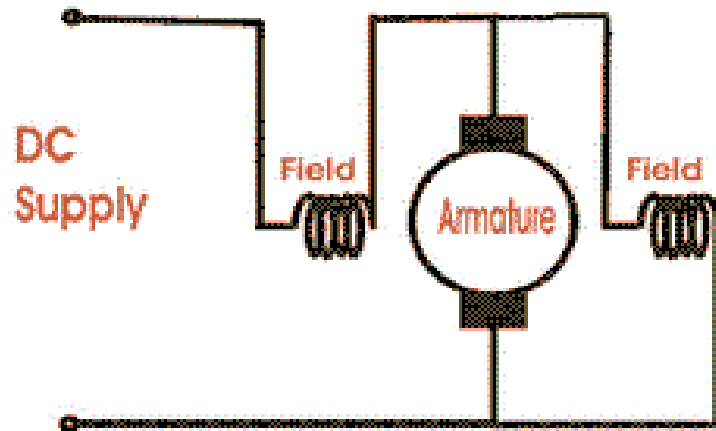

Long Shunt DC Motor

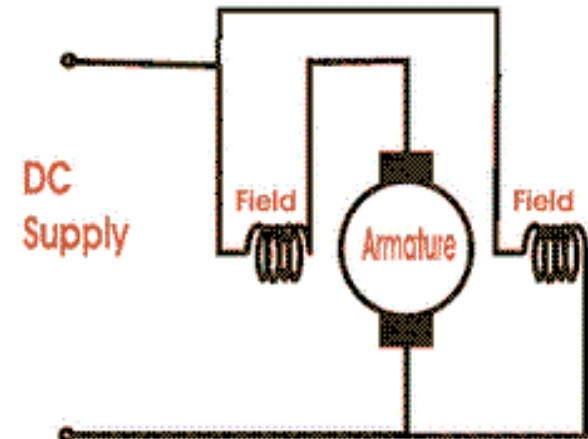

Torque of a D.C. Machine

- For a D.C. Motor, the supply voltage V is given by

$$V = E + I_a R_a$$

- Multiplying each term by current I_a gives:

$$VI_a = EI_a + I_a^2 R_a$$

- The term VI_a is the total electrical power supplied to the armature, the term $I_a^2 R_a$ is the loss due to armature resistance, and the term EI_a is the mechanical power developed by the armature
- If T is the torque, in newton metres, then the mechanical power developed is given by $T\omega$ watts

Hence $T\omega = 2\pi nT = EI_a$ from which,

$$\text{torque } T = \frac{EI_a}{2\pi n} \text{ newton metres}$$



Torque of a D.C. Machine

- The e.m.f. E generated is given by:

$$E = \frac{2p\Phi nZ}{c}$$

$$\text{Hence } 2\pi nT = EI_a = \left(\frac{2p\Phi nZ}{c} \right) I_a$$

$$\text{and torque } T = \frac{\left(\frac{2p\Phi nZ}{c} \right) I_a}{2\pi n}$$

$$\text{i.e., } T = \frac{p\Phi Z I_a}{\pi c} \text{ newton metres}$$

For a given machine, Z , c and p are fixed values

$$\text{Hence torque } T \propto \Phi I_a$$



Problem

- **Problem 14.** An 8-pole D.C. motor has a wave-wound armature with 900 conductors. The useful flux per pole is 25 mWb. Determine the torque exerted when a current of 30 A flows in each armature conductor.

Solⁿ

$$p = 4, c = 2 \text{ for a wave winding, } \phi = 25 \times 10^{-3} \text{ Wb, } Z = 900$$


$$I_a = 30 \text{ A}$$

$$\begin{aligned} \text{torque } T &= \frac{p\Phi Z I_a}{\pi c} \\ &= \frac{(4)(25 \times 10^{-3})(900)(30)}{\pi(2)} = 429.7 \text{ Nm} \end{aligned}$$



Speed Torque Characteristics (Shunt)

$$n = \frac{V - I_a R_a}{k\phi}$$

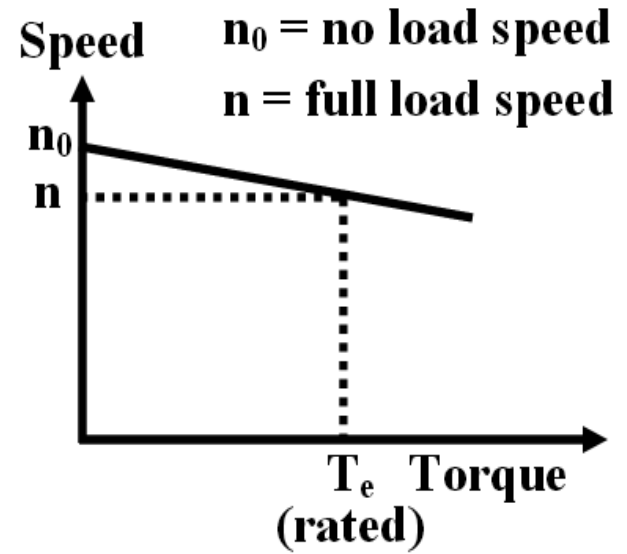

- The graph above shows a torque/speed curve of a D.C. shunt motor.
- For shunt motors Φ will be constant, and Torque is proportional to ΦI_a , hence the curve will be straight line with –ve slope



Speed Torque Characteristics (Series)

$$T \propto \phi I_a$$

$$n = \frac{V - I_a R_a}{k\phi}$$

In linear region,

$$T \propto I_a^2$$

$$n = \frac{V}{k' I_a} - \frac{R_a}{k'}$$


In saturation region,

$$T \propto \phi_{sat} I_a$$


$$n = \frac{V - I_a R_a}{k' \phi_{sat}}$$



Speed Torque Characteristics (Series)

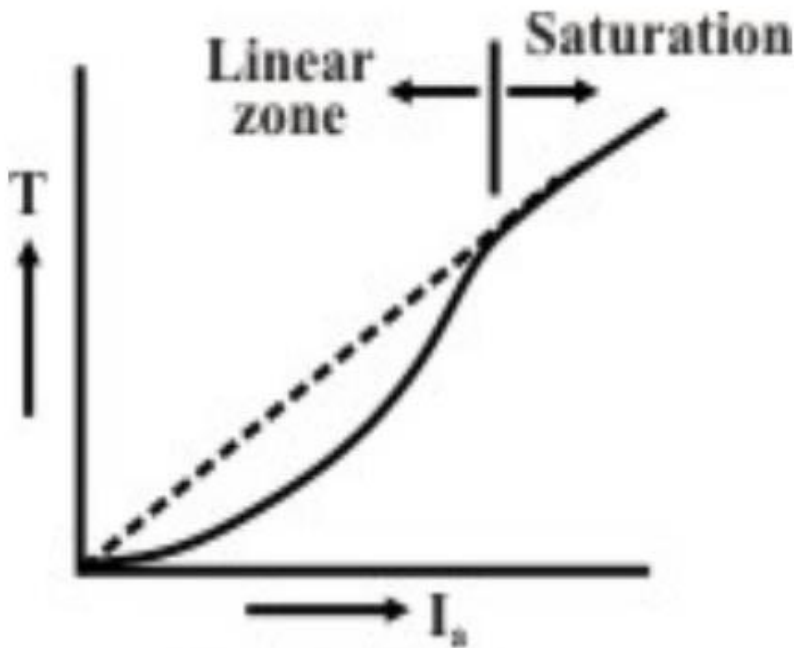


Torque Vs. Current

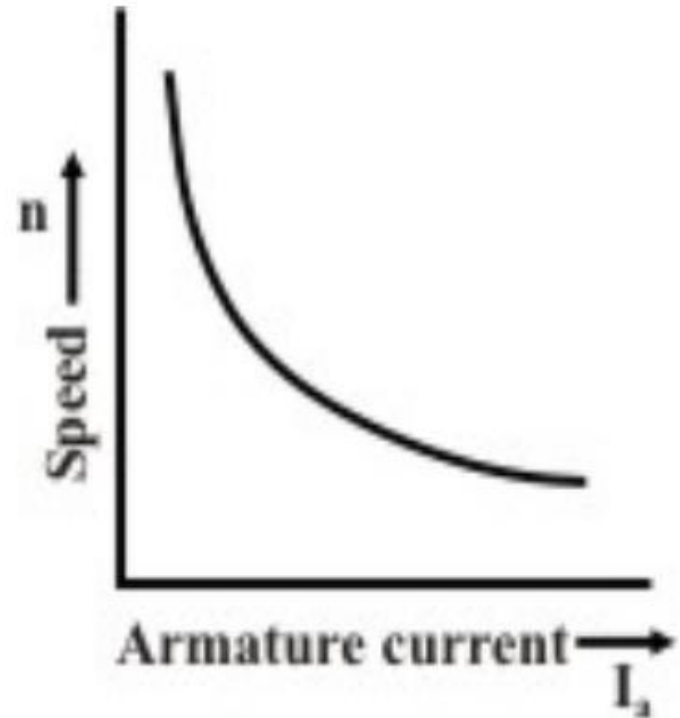

Speed Vs. Current



Speed Torque Characteristics

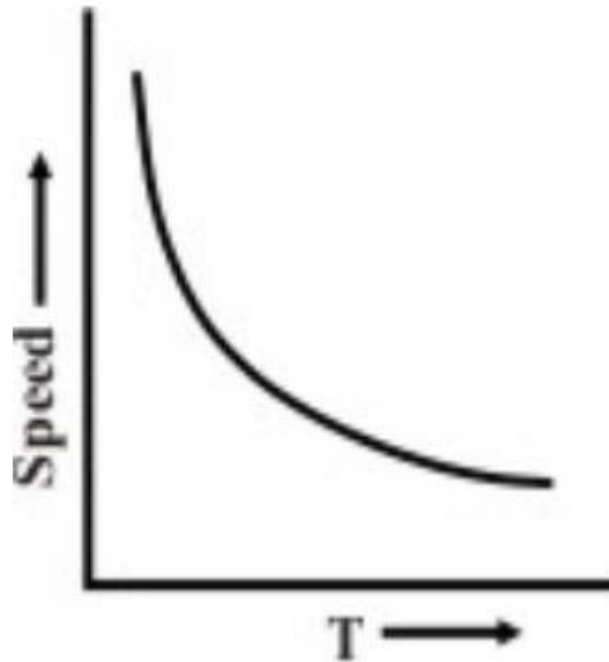

Speed Vs.


Torque

- Series motor should never be started with no load
- It is not suitable for constant speed applications




Speed Torque Characteristics

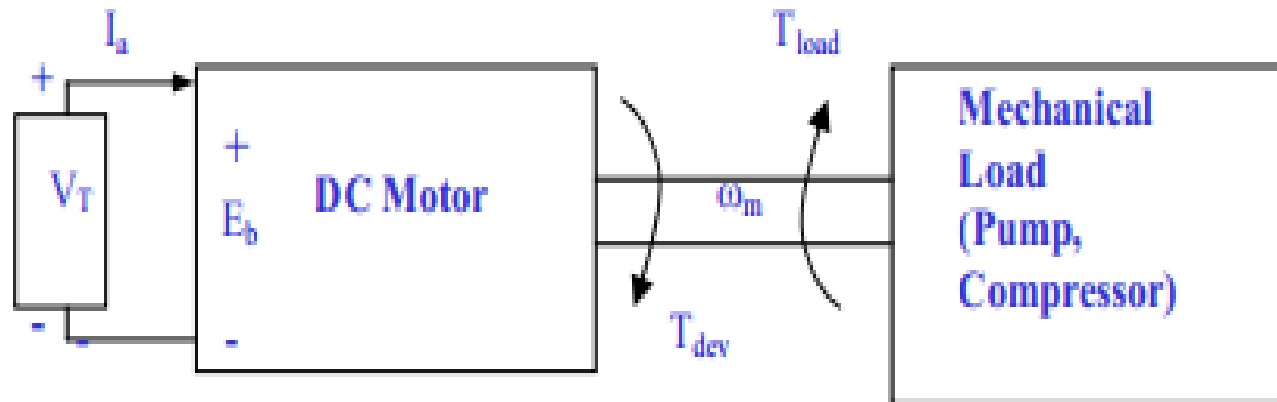- Motor characteristics are frequently given as two points on this graph:
 - The stall torque, represents the point on the graph at which the torque is a maximum, but the shaft is not rotating
 - The no load speed, is the maximum output speed of the motor (when no torque is applied to the output shaft)




Speed Torque Characteristics

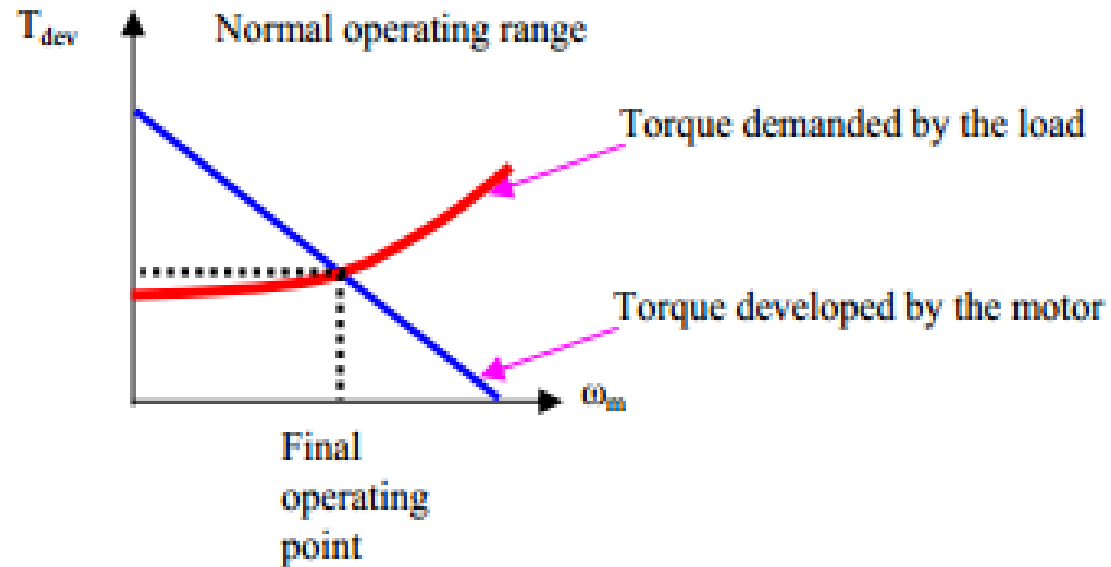- As the motor starts to rotate and picks up speed, the developed torque decreases. The motor finally comes to a stable operating point when the two torques balance each other



Speed Control of DC Motors

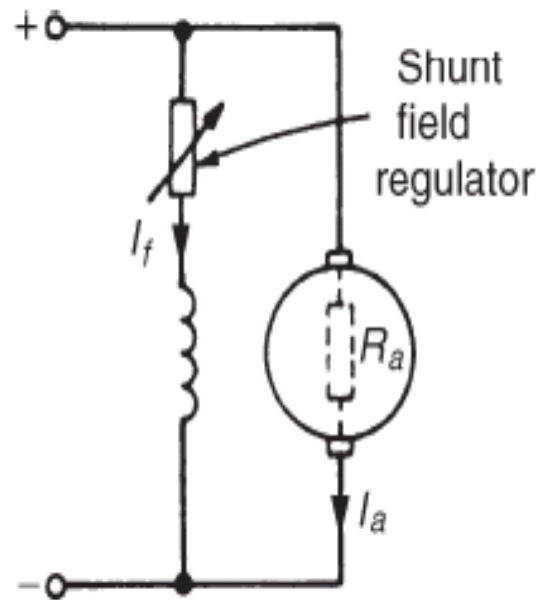- **Shunt-wound Motors:** - The speed of a shunt-wound D.C. motor, n , is proportional to $(V - I_a R_a) / \phi$
- The former is achieved by using a variable resistor in series with the field winding, such a resistor is called the **shunt field regulator**



$$n \propto \frac{V - I_a (R_a + R)}{\Phi}$$

Shunt Wound Motors



Problem

- **Problem 16.** A 500 V shunt motor runs at its normal speed of 10 rev/s when the armature current is 120 A. The armature resistance is 0.2
 - (a) Determine the speed when the current is 60 A and a resistance of 0.5 Ω is connected in series with the armature, the shunt field remaining constant
 - (b) Determine the speed when the current is 60 A and the shunt field is reduced to 80% of its normal value by increasing resistance in the field circuit

Solⁿ

$$\begin{aligned}(a) \text{ back e.m.f at } 120\text{A, } E_1 &= V - I_a R_a \\ &= 500 - (120)(0.2) \\ &= 500 - 24 = 476 \text{ volts}\end{aligned}$$



$$\text{When } I_a = 60\text{A}, E_2 = 500 - (60)(0.2 + 0.5) \\ = 458 \text{ volts}$$

$$\text{Now } \frac{E_1}{E_2} = \frac{\Phi_1 n_1}{\Phi_2 n_2}$$

$$\text{i.e., } \frac{476}{458} = \frac{\Phi_1 (10)}{\Phi_2 n_2} \quad \text{since } \Phi_2 = \Phi_1$$

$$\text{from which, speed } n_2 = \frac{(10)(458)}{(476)} = 9.62 \text{ rev / s}$$

$$(b) \text{ Back e.m.f when } I_a = 60\text{A}, E_2 = 500 - (60)(0.2) \\ = 488 \text{ volts}$$

$$\text{Now } \frac{E_1}{E_2} = \frac{\Phi_1 n_1}{\Phi_2 n_2}$$

$$\text{i.e., } \frac{476}{458} = \frac{\Phi_1 (10)}{(0.8\Phi_1) n_3} \quad \text{since } \Phi_2 = 0.8\Phi_1$$

$$\text{from which, speed } n_3 = \frac{(10)(458)}{(0.8)(476)} = 12.82 \text{ rev / s}$$




Speed Control of DC Motors

- **Series-wound motors:** -The speed control of series-wound motors is achieved using either (a) field resistance, or (b) armature resistance techniques

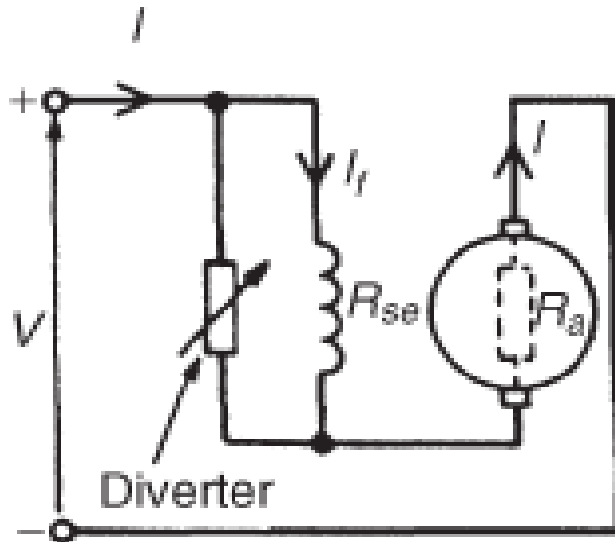a) Field resistance series wound motor: The speed of a D.C. series-wound motor is given by:

$$n = k \left(\frac{V - IR}{\Phi} \right)$$



- **Problem 17.** On full-load a 300 V series motor takes 90 A and runs at 15 rev/s. The armature resistance is 0.1Ω and the series winding resistance is $50\text{ m}\Omega$. Determine the speed when developing full load torque but with a 0.2Ω diverter in parallel with the field winding. (Assume that the flux is proportional to the field current.)

So/ⁿ

$$\begin{aligned}
 \text{At } 300\text{ V, e.m.f. } E_1 &= V - IR \\
 &= V - I(R_a + R_{se}) \\
 &= 300 - (90)(0.1 + 0.05) = 286.5\text{volts}
 \end{aligned}$$

with the 0.2Ω diverter in parallel with R_{se}

$$\text{the equivalent resistance, } R = \frac{(0.2)(0.05)}{(0.2) + (0.05)} = 0.04\Omega$$

$$\text{By current division, current } I_1 = \left(\frac{0.2}{0.2 + 0.05} \right) I = 0.8I$$



Torque, $T \propto I_a \Phi$ and for full load torque, $I_{a1} \Phi_1 = I_{a2} \Phi_2$

Since flux is proportional to field current $\Phi_1 \propto I_{a1}$ and $\Phi_2 \propto 0.8 I_{a2}$
then $(90)(90) = (I_{a2})(0.8 I_{a2})$

from which, $I_{a2}^2 = \frac{(90)^2}{0.8}$ and $I_{a2} = \frac{90}{\sqrt{0.8}} = 100.62 \text{ A}$

Hence e.m.f $E_2 = V - I_{a2}(R_a + R)$
 $= 300 - (100.62)(0.1 + 0.04) = 285.9 \text{ volts}$

Now e.m.f., $E \propto \Phi n$ from which, $\frac{E_1}{E_2} = \frac{\Phi_1 n_1}{\Phi_2 n_2} = \frac{I_{a1} n_1}{0.8 I_{a2} n_2}$

Hence $\frac{(286.5)}{285.9} = \frac{(90)(15)}{(0.8)(100.62)n_2}$

and new speed, $n_2 = 16.74 \text{ rev/s}$


Thus the speed of the motor has increased from 15 rev/s (i.e., 900 rev/min) to 16.74 rev/s (i.e., 1004 rev/min) by inserting a 0.2 diverter resistance in parallel with the series winding.



Speed Control of DC Motors

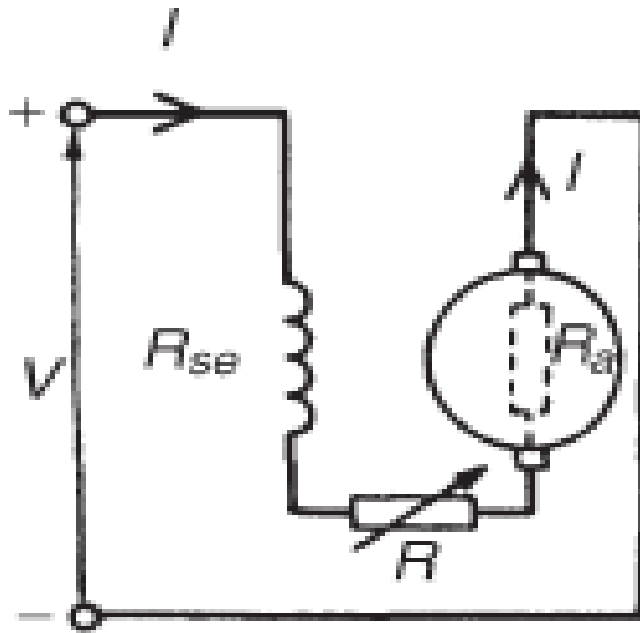(b) Armature resistance technique

- Speeds below normal are obtained by connecting a variable resistor in series with the field winding
- reduces the speed
- large power loss



$$n = k \left(\frac{V - IR}{\Phi} \right)$$



Armature Resistance Technique

- **Problem 18.** A series motor runs at 800 rev/min when the voltage is 400 V and the current is 25 A. The armature resistance is 0.4Ω and the series field resistance is 0.2Ω . Determine the resistance to be connected in series to reduce the speed to 600 rev/min with the same current.

- *So/n e.m.f.* $E_1 = V - I(R_a + R_{se})$
 $= 400 - (25)(0.4 + 0.2) = 385\text{volts}$

At 600 rev/min, since the current is unchanged, the flux is unchanged.

Thus $E \propto \Phi n$ from which, $\frac{E_1}{E_2} = \frac{\Phi_1 n_1}{\Phi_2 n_2} \implies \frac{385}{E_2} = \frac{800}{600} = 288.75\text{volts}$

and $E_2 = V - I(R_a + R_{se} + R)$

Hence $288.75 = 400 - 25(0.4 + 0.2 + R)$

$$R = 3.85\Omega$$

Thus the addition of a series resistance of 3.85Ω has reduced the speed from 800 rev/min to 600 rev/min



Summary

- Torque developed by a DC motor is proportional to flux and armature current
- Shunt motors run at almost constant speed
- Series motors are used for high torque applications
- Series motors should never be operated without load

